



UNIVERSITY OF
LIVERPOOL

Digital Systems Design

ELEC373/473

Assignment/Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs


Behavioural Modelling and Synthesis (Modelling Repetitive Algorithms)

Extracted from: Verilog HDL by M.D. Ciletti and
IEEE Std 1364-2001 Version C

Prof J.S. Smith
Room A515;
E-mail: j.s.smith@liv.ac.uk

Dataflow Models of a Linear Feedback Shift Register (LFSR)

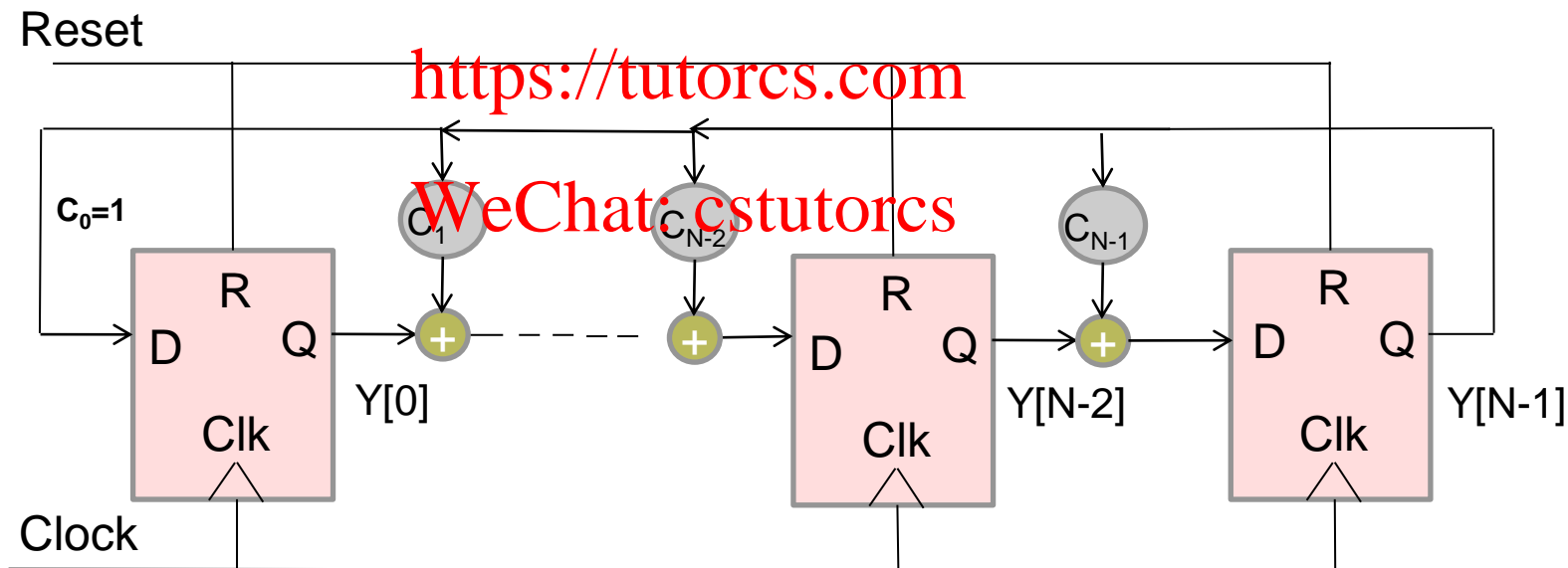
- LFSRs are commonly used in generating pseudo-random binary numbers and have many other applications like cyclic redundancy check (CRC).



$C_x = 1$ means $Y[x]$ is connected to the XOR gate (except for LSB).

$C_x = 0$ means there is no connection.

Data Movement in an LFSR

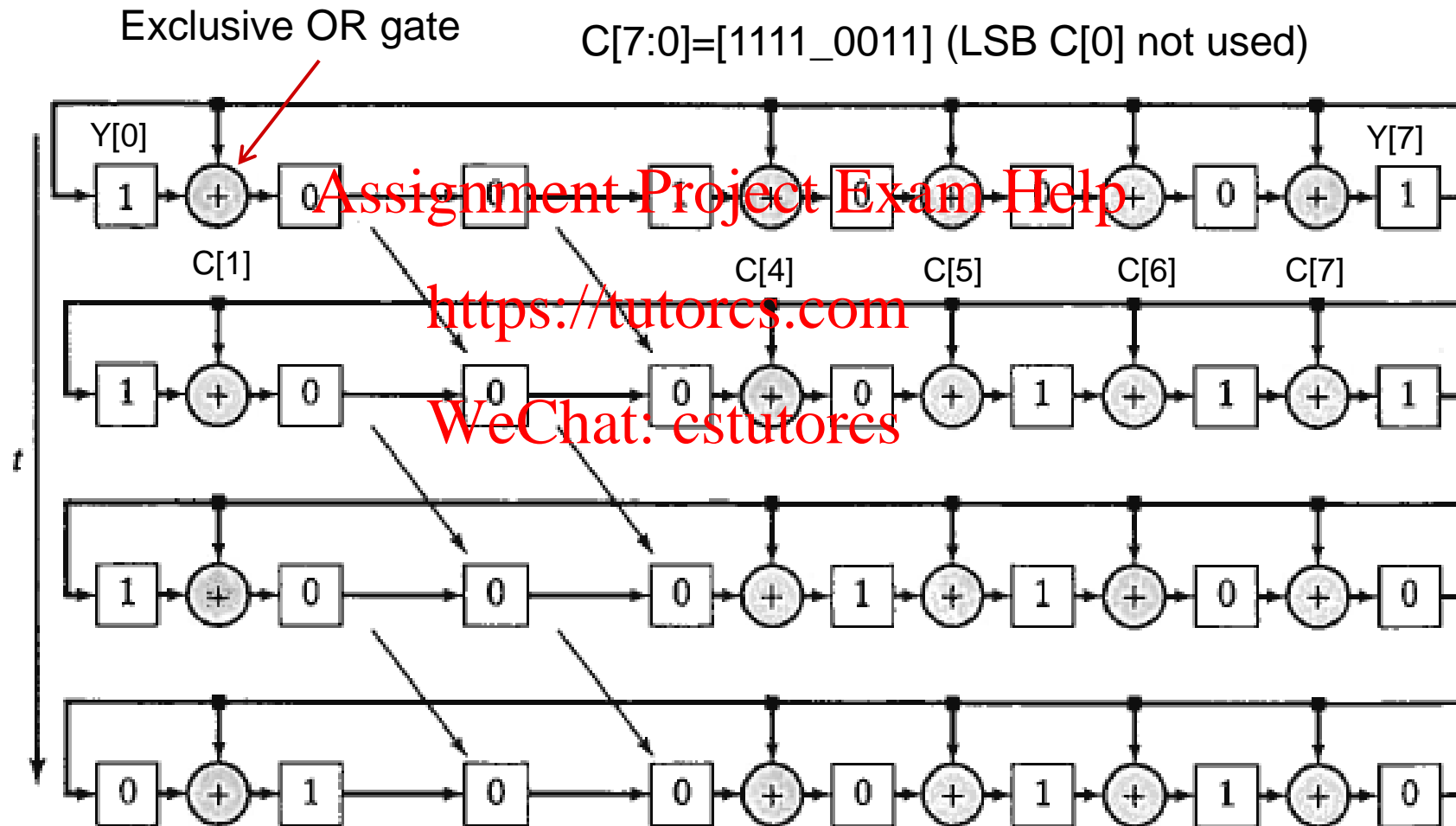

8-Cell LFSR using Nonblocking Assignments

```
1 module LFSR_RTL (Y, Clock, Reset);
2     parameter          Length = 8;
3     parameter          initial_state = 8'b1000_1001;
4     parameter [Length-1:0] Tap_Coefficient = 8'b1111_0011;
5
6     input               Clock, Reset;
7     output [Length-1:0] Y;
8     reg [Length-1:0] Y;
9
10
11     always @ (posedge Clock)
12         if (Reset==0) Y <= initial_state;
13         else
14             begin
15                 Y[0] <= Y[7];
16                 Y[1] <= Tap_Coefficient[1] ? Y[0] ^ Y[7] : Y[0];
17                 Y[2] <= Tap_Coefficient[2] ? Y[1] ^ Y[7] : Y[1];
18                 Y[3] <= Tap_Coefficient[3] ? Y[2] ^ Y[7] : Y[2];
19                 Y[4] <= Tap_Coefficient[4] ? Y[3] ^ Y[7] : Y[3];
20                 Y[5] <= Tap_Coefficient[5] ? Y[4] ^ Y[7] : Y[4];
21                 Y[6] <= Tap_Coefficient[6] ? Y[5] ^ Y[7] : Y[5];
22                 Y[7] <= Tap_Coefficient[7] ? Y[6] ^ Y[7] : Y[6];
23             end
24 endmodule
```


Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs

Note in this code everything is in the always@(posedge) block as the only output is the register value you can do this if there are only register outputs

Synthesised circuit

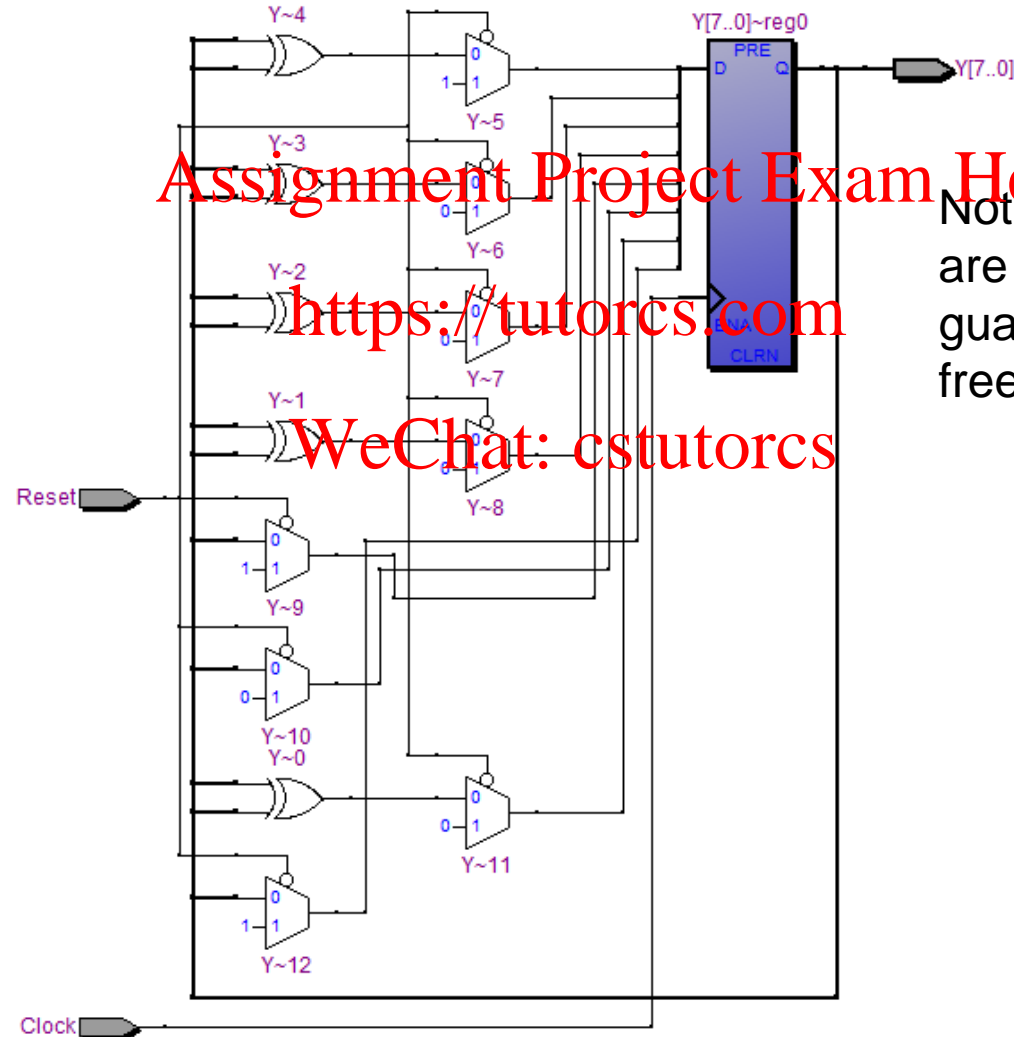


Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs

Note only register values are output. These are guaranteed to be glitch free.

Simulation Result

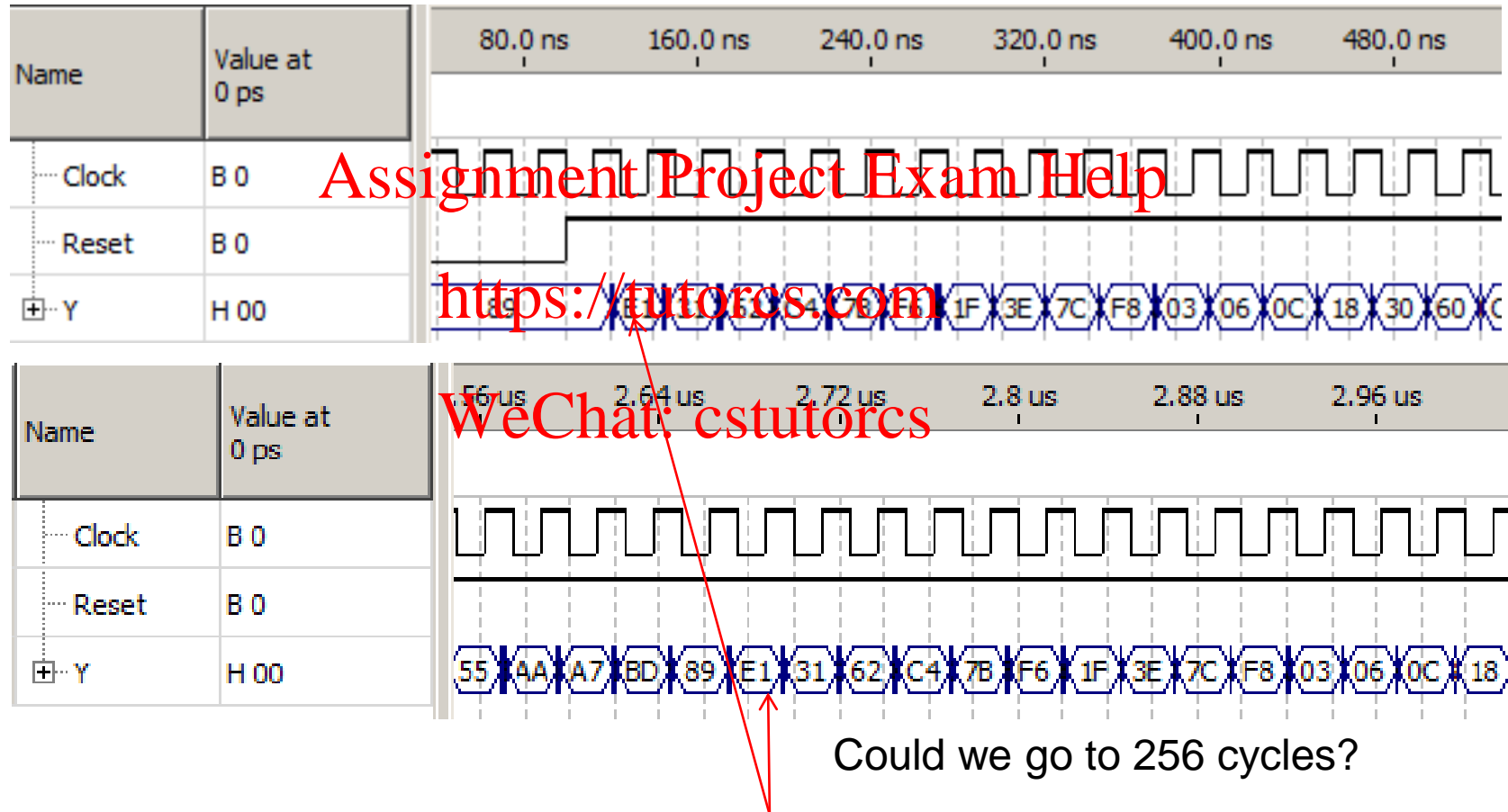

The pattern is repeated after 2550 ns = 51 cycles X 50ns
This period can be increased to 255 cycles by changing the coefficients.

Looping Statements IEEE Std 1364-2001

■ *forever*

- *Continuously* executes a statement.

■ *repeat*

- Executes a statement *a fixed number of times*. If the expression evaluates to unknown or high impedance, it shall be treated as zero, and no statement shall be executed.

■ *while*

- Executes a statement *until an expression becomes false*. If the expression starts out false, the statement shall not be executed at all.

Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs

Looping Statements IEEE Std 1364-2001

■ *for*

- Controls execution of its associated statement(s) by a three-step process, as follows:
 - a) Executes an assignment normally used to initialize a variable that controls the number of loops executed.
 - b) Evaluates an expression—if the result is zero, the for-loop shall exit, and if it is not zero, the for-loop shall execute its associated statement(s) and then perform step c. If the expression evaluates to an unknown or high-impedance value, it shall be treated as zero.
 - c) Executes an assignment normally used to modify the value of the loop-control variable, then repeats step b.

8-cell LFSR using For loop

For loop can be used for describing repetitive algorithms.

```
1 module LFSR_RTL_for (Y, Clock, Reset);
2     parameter          Length = 8;
3     parameter          initial_state = 8'b1000_1001;
4     parameter [Length-1:0] Tap_Coefficient = 8'b1111_0011;
5
6     input               Clock, Reset;
7     output [Length-1:0] Y;
8     reg [Length-1:0] Y;
9     integer            Cell_ptr;
10
11
12     always @ (posedge Clock)
13     begin
14         if (Reset==0) Y <= initial_state;
15         else
16         begin
17             Y[0] <= Y[Length-1];
18             for (Cell_ptr = 1; Cell_ptr <= (Length-1); Cell_ptr = Cell_ptr + 1)
19                 if (Tap_Coefficient[Cell_ptr] == 1)
20                     Y[Cell_ptr] <= Y[Cell_ptr-1] ^ Y[Length-1];
21                 else
22                     Y[Cell_ptr] <= Y[Cell_ptr-1];
23         end
24     end
25 endmodule
```

Assignment Project Exam Help
<https://tutorcs.com>
WeChat: cstutorcs

initial_statement executes once

If the control expression is true the following statement(s) will be executed.

If the control expression is false the loop terminates.

index_statement

Repeat Example: Combinational Multiplier

```
1 module Multiplier (Result, Operanda, Operandb);
2
3     parameter    SIZE = 4;
4     parameter    LONGSIZE = 8;
5
6     output    [LONGSIZE-1:0] Result;
7     input     [SIZE-1:0] Operanda, Operandb;
8
9     reg       [LONGSIZE-1:0] shift_opa, shift_opb, Result;
10
11     always @ (Operanda, Operandb)
12     begin
13         /* The left 4 bits of shift_opa and shift_opb are assigned to 0
14            while their right 4 bits are assigned to Operanda and Operandb */
15         shift_opa = Operanda;
16         shift_opb = Operandb;
17         Result = 0;
18
19         repeat (SIZE)
20         begin
21             if (shift_opb[0])
22                 Result = Result + shift_opa;
23             shift_opa = shift_opa << 1;
24             shift_opb = shift_opb >> 1;
25         end
26     end
27 endmodule
```

Will this produce a
combinational or
sequential design?


Assignment Project Exam Help

<https://tutorcs.com>


WeChat: cstutorcs

Operanda	1010	X
Operandb	1101	
Shift_opa	00001010	+
	00000000	
	00101000	
	01010000	
Result	10000010	

Simulation and Synthesis

 

WeChat: cstutorcs

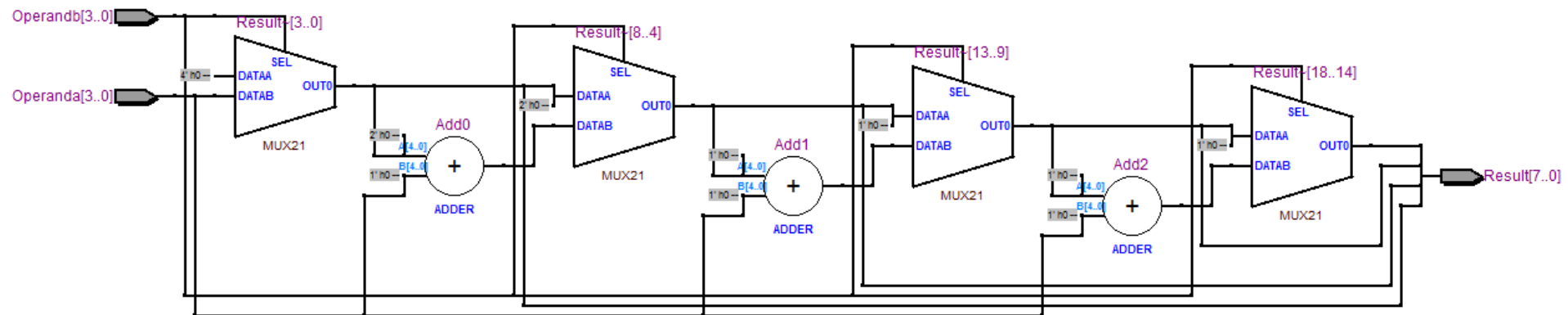

No latches were synthesized. Combinational circuit with Adders and Multiplexers.

Counting 1's in a 7 bit value

The next few examples are going to count the number of 1's in an 7 bit value:

i.e. 1010101B = 4 1's

Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs

“While” Example: Counting the Number of Ones in an Input Register

```
1 module Count_ones (ones, rega);  
2  
3     output    [2:0] ones;  
4     input     [6:0] rega;  
5  
6     reg       [6:0] temp_reg;  
7     reg       [2:0] ones;  
8  
9     always @ (rega)  
10    begin  
11        ones = 0;  
12        temp_reg = rega;  
13        while (temp_reg)  
14        begin  
15            if (temp_reg[0]) ones = ones + 1;  
16            temp_reg = temp_reg >> 1;  
17        end;  
18    end  
19 endmodule
```


Assignment Project Exam Help

Will this produce a combinational or sequential design?

<https://tutorcs.com>

WeChat: cstutorcs

Synthesised Circuit

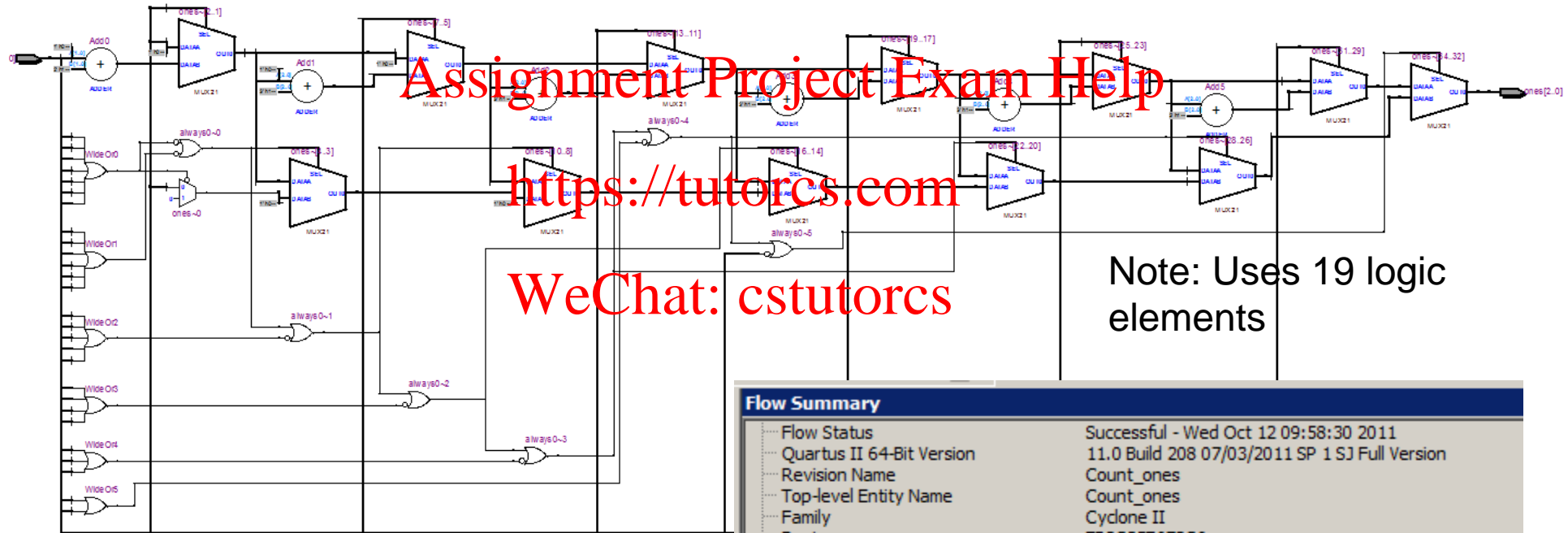


Note: Uses 19 logic elements

No latches synthesised, all combinational logic.

Flow Summary	
Flow Status	Successful - Wed Oct 12 09:58:30 2011
Quartus II 64-Bit Version	11.0 Build 208 07/03/2011 SP 1 SJ Full Version
Revision Name	Count_ones
Top-level Entity Name	Count_ones
Family	Cyclone II
Device	EP2C35F672C6
Timing Models	Final
Total logic elements	19 / 33,216 (< 1 %)
Total combinational functions	19 / 33,216 (< 1 %)
Dedicated logic registers	0 / 33,216 (0 %)
Total registers	0
Total pins	10 / 475 (2 %)
Total virtual pins	0
Total memory bits	0 / 483,840 (0 %)
Embedded Multiplier 9-bit elements	0 / 70 (0 %)
Total PLLs	0 / 4 (0 %)

Simulation Results

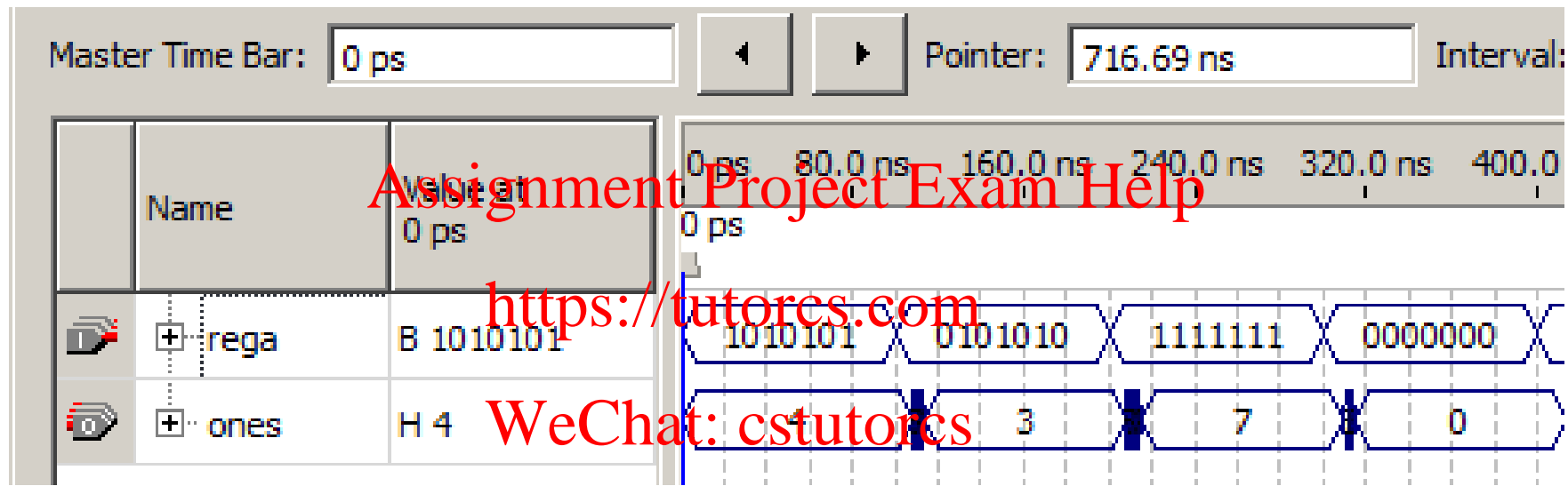


Counting the Number of Ones (more efficient approach)

```
1 module NumberOfOnes ( Out, Input);  
2     output    [2:0] Out;  
3     input     [6:0] Input;  
4  
5     assign Out = Input[0]+Input[1]+Input[2]+  
6               Input[3]+Input[4]+Input[5]+Input[6];  
7 endmodule
```


Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs

 

Synthesised Design

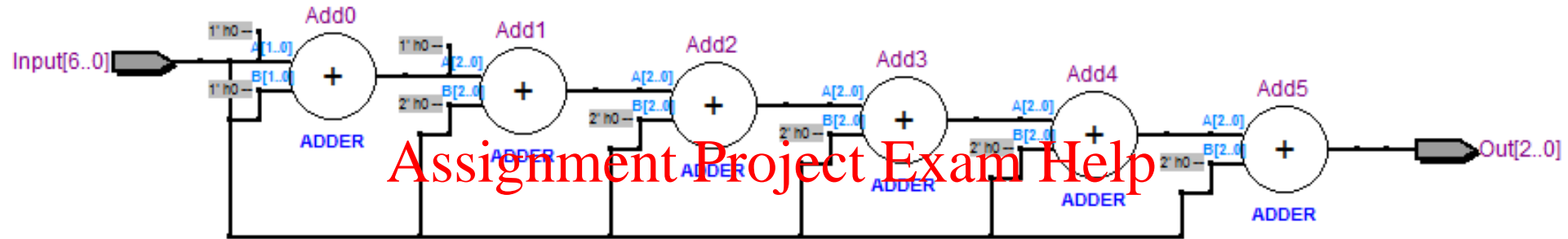

<https://tutorcs.com>

Flow Summary	
Flow Status	Successful - Wed Oct 12 11:44:32 2011
Quartus II 64-bit Version	11.0 Build 208.07.02.2011 SP 1 SJ Full Version
Revision Name	NumberOfOnes
Top-level Entity Name	NumberOfOnes
Family	Cyclone II
Total logic elements	8 / 33,216 (< 1 %)
Total combinational functions	8 / 33,216 (< 1 %)
Dedicated logic registers	0 / 33,216 (0 %)
Total registers	0
Total pins	10 / 475 (2 %)
Total virtual pins	0
Total memory bits	0 / 483,840 (0 %)
Embedded Multiplier 9-bit elements	0 / 70 (0 %)
Total PLLs	0 / 4 (0 %)
Device	EP2K35F672C6
Timing Models	Final

Note: 8 logic elements


Counting the Number of Ones (using a for loop)

```
1 module NumberOfOnes_for( Out, Input);
2     parameter    size = 7;
3
4     output    [2:0] Out;
5     input     [size-1:0] Input;
6
7     reg       [2:0] Out;
8     integer   Count;
9
10    always @ (Input)
11    begin
12        Out = 0;
13        for (Count = 0; Count < size; Count = Count + 1)
14            if (Input[Count])
15                Out = Out + 1;
16    end
17 endmodule
```


Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs

 

Synthesised Design

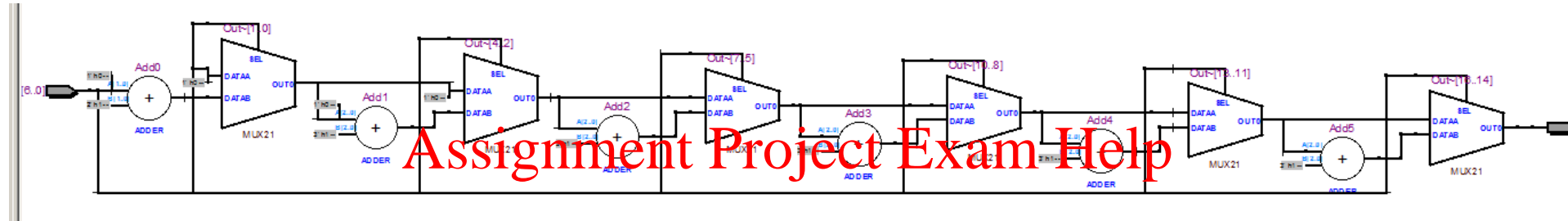

<https://tutorcs.com>

WeChat: cstutorcs

Flow Summary	
Flow Status	Successful - Wed Oct 12 11:46:42 2011
Quartus II 64-Bit Version	11.0 Build 208 07/03/2011 SP 1 SJ Full Version
Revision Name	NumberOfOnes_for
Top-level Entity Name	NumberOfOnes_for
Family	Cyclone II
Device	EP2C35F672C6
Timing Models	Final
Total logic elements	9 / 33,216 (< 1 %)
Total combinational functions	9 / 33,216 (< 1 %)
Dedicated logic registers	0 / 33,216 (0 %)
Total registers	0
Total pins	10 / 475 (2 %)
Total virtual pins	0
Total memory bits	0 / 483,840 (0 %)
Embedded Multiplier 9-bit elements	0 / 70 (0 %)
Total PLLs	0 / 4 (0 %)


Note: 9 Logic Elements

Disable Statement

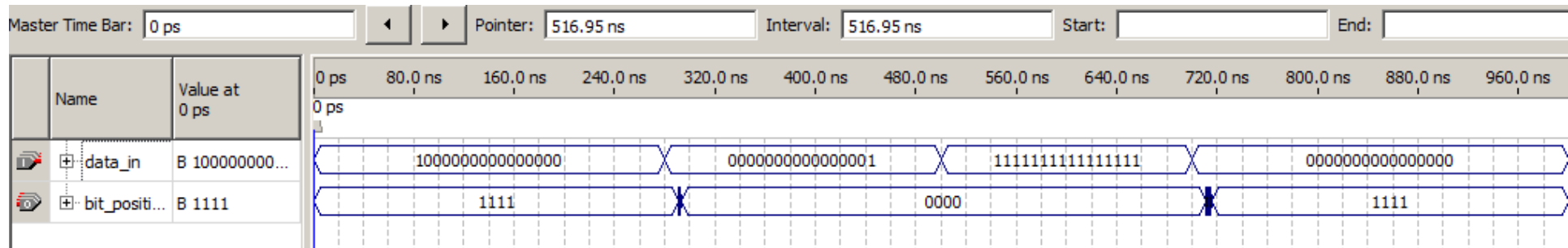
Example: Position of the First '1'

The *disable* statement is used to prematurely terminate a named block of procedural statements.

```
1 module find_first_one( bit_position, data_in);
2
3     output [3:0] bit_position; // four bits will identify
4     input  [15:0] data_in;      // the position
5
6     reg [3:0] bit_position;
7
8     always @ (data_in)          // rerun when input data changes
9     begin: search_for_1         // named Block
10         for (bit_position = 0; bit_position < 15; bit_position = bit_position + 1)
11             if (data_in[bit_position]==1)
12                 disable search_for_1;
13     end
14 endmodule
```



Synthesised Circuit

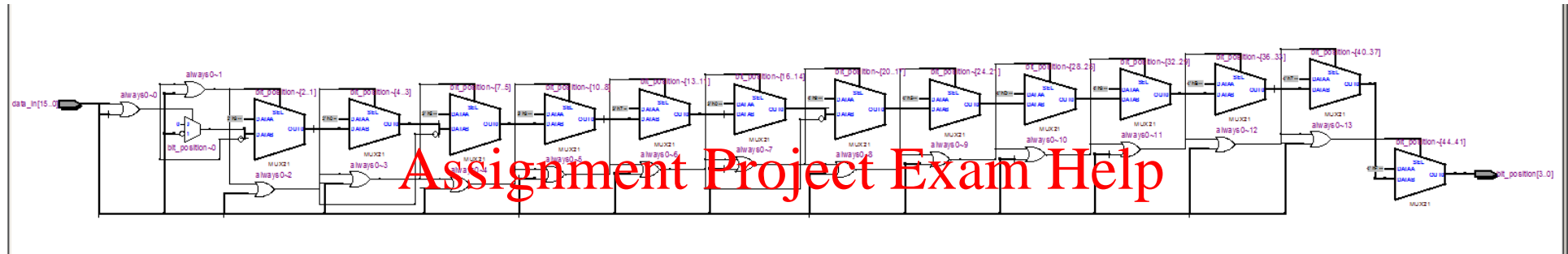


<https://tutorcs.com>

WeChat: estutorcs


Flow Summary	
Flow Status	Successful Wed Oct 12 16:17:37 2011
Quartus II 64-Bit Version	11.0 Build 208 07/03/2011 SP 1 SJ Full Version
Revision Name	find_first_one
Top-level Entity Name	find_first_one
Family	Cyclone II
Device	EP2C35F672C6
Timing Models	Final
Total logic elements	14 / 33,216 (< 1 %)
Total combinational functions	14 / 33,216 (< 1 %)
Dedicated logic registers	0 / 33,216 (0 %)
Total registers	0
Total pins	20 / 475 (4 %)
Total virtual pins	0
Total memory bits	0 / 483,840 (0 %)
Embedded Multiplier 9-bit elements	0 / 70 (0 %)
Total PLLs	0 / 4 (0 %)

Position of the First '1' with Valid

```
1 module find_first_one_valid( bit_position, valid, data_in);
2
3     output    [3:0]    bit_position; // four bits will identify
4     input     [15:0]   data_in;      // the position
5     output    valid;
6
7     reg       [3:0]    bit_position;
8
9     assign    valid = |data_in;
10
11     always @ (data_in) // rerun when input data changes
12     begin: search_for_1 // named Block
13         for (bit_position = 0; bit_position < 16; bit_position = bit_position + 1)
14             if (data_in[bit_position] == 1)
15                 disable search_for_1;
16     end
17 endmodule
```

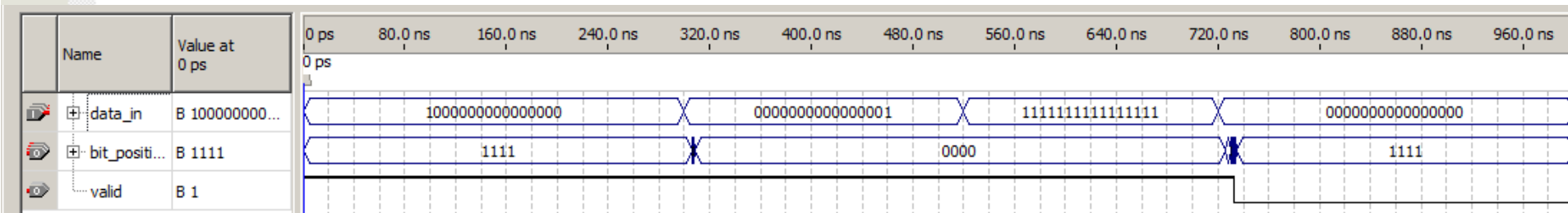

Synthesised Circuit

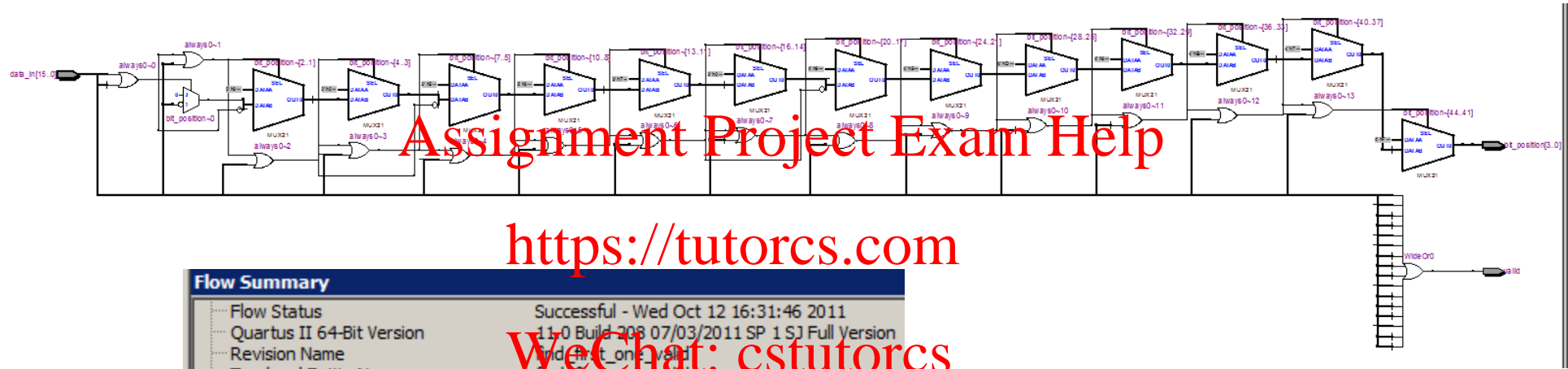

<https://tutorcs.com>

WeChat: cstutorcs