

# Digital System Design

## ELEC373/473

Assignment Project Exam Help



<https://tutorcs.com>

WeChat: cstutorcs

Hardware Description Languages (HDLs)  
and coding styles

# Overview of HDLs (Hardware Description Languages)

- Designers use HDLs

- 1) To model circuits
- 2) To compile the model to synthesize it into physical circuits.
- 3) To simulate the model to verify the functionality and timing of the circuit. Designers need to write a testbench containing descriptions of the stimulus waveforms that are applied to the circuit.

- Today HDLs are widely used to design circuits of enormous size and complexity. HDLs use design hierarchy to support the top-down methodology.

# Overview of HDLs

- Provides many descriptive styles
  - Structural
  - Register Transfer Level (RTL)
  - Behavioral
- HDL based designs are highly portable and independent of technology.
- HDLs are not like procedural software and cannot run on processors.
- HDLs are a convenient medium for integrating intellectual property (IP) from a variety of sources with a proprietary design.

Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs


# Overview of HDLs

- HDLs reduces the time for the design cycle.
- Synthesis tools (e.g. Quartus) take a HDL model and generate the technology-specific netlist.
- Two main HDLs are used by industry:
  - Verilog (Verify Logic)
    - C-based
    - Driven by industry/academia
  - VHDL (Very High Speed Integrated Circuit HDL)
    - Ada based. Originally developed by an order of the USA DoD for documentation of digital systems.
    - Driven by defence/industry/academia

 
# HDL vs. Software

- In software programmes just one of the expressions is calculated depending on the values of **a** and **b**.
- In HDL all hardware for computing the logic are created during synthesis.
- Multiplexers are used to select the correct output.
- Learn to understand how descriptions are translated to hardware. “**think hardware**”

```
if(a) then f = c AND d;  
elseif(b) then f = d;  
else f = d OR e;  
end if;
```



# ASM for previous example

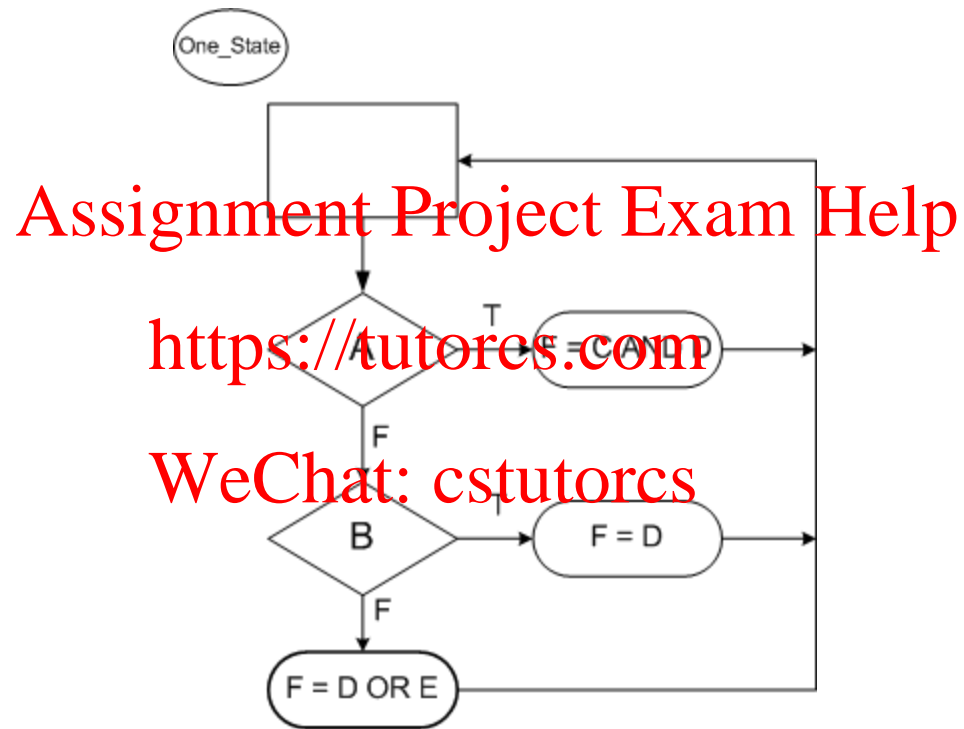

- Only combinational logic so just has a single state

# Verilog Module

- In Verilog, a circuit is a **module**.
- Three types of ports: **input**, **output**, **inout** (bidirectional)
- A signal is attached to every port.
- Specify multiple bits using range, e.g. **a[7:0]** or **b[3:7]**
- Single bit if range is not specified.


Assignment Project Exam Help

<https://tutorcs.com>


WeChat: cstutorcs

*module name*  
*ports names*  
*Ports types*
 
```
module Add_half ( sum, c_out, a ,b);  
    input  
    output  
    xor  
    and  
endmodule
```



# ASM for half\_adder

 

Alternative module declaration (introduced in the Verilog 2001 standard)

```
module Add_half ( output sum, output c_out, input a, input b);  
    xor          (sum, a, b);  
    and          (c_out, a, b);  
endmodule
```



# Module Styles

- Modules can be specified in different ways
  - 1) **Structural**: connect primitives and modules
  - 2) **RTL** (Register Transfer Level) :
    - use continuous assignments
  - 3) **Behavioral**: use **initial** and **always** blocks
    - Note that “initial” is primarily for simulation rather than for synthesis.
- A single module can use more than one method.