

Digital System Design

ELEC373/473

Assignment Project Exam Help



<https://tutorcs.com>

WeChat: cstutorcs


Counters in Verilog

Prof J.S. Smith
Room A515;
E-mail: j.s.smith@liv.ac.uk

Counters

- Counters are probably one of the most heavily used components in digital systems.
- When circuits were built using the 74-series devices the common “synchronous” counters used were:
 - 74x160 - synchronous presettable 4-bit decade counter, asynchronous clear
 - 74x161 - synchronous presettable 4-bit binary counter, asynchronous clear
 - 74x162 - synchronous presettable 4-bit decade counter, synchronous clear
 - 74x163 - synchronous presettable 4-bit binary counter, synchronous clear
 - 74x190 - synchronous presettable up/down 4-bit decade counter
 - 74x191 - synchronous presettable up/down 4-bit binary counter

74x161- Schematic

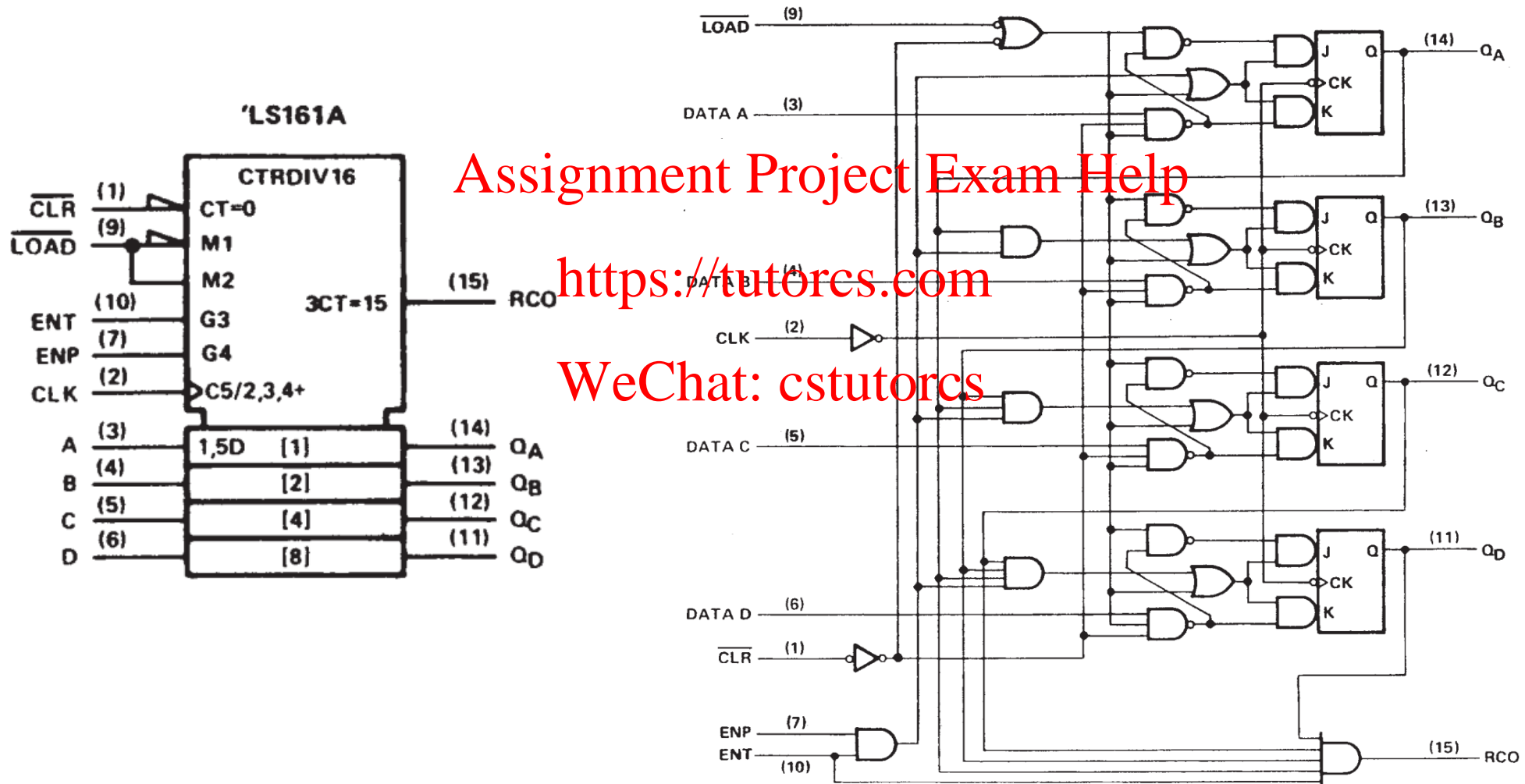


74x161- Timing Diagrams

'161, 'LS161A, '163, 'LS163A, 'S163 BINARY COUNTERS

typical clear, preset, count, and inhibit sequences

Illustrated below is the following sequence:

 1. Clear outputs to zero ('161 and 'LS161A are asynchronous; '163, 'LS163A, and 'S163 are synchronous)
2. Preset to binary twelve
3. Count to thirteen, fourteen fifteen, zero, one, and two
4. Inhibit




- 74x161 has asynchronous active low clear
- Active low synchronous Preset
- Synchronously counts when the Enables P & T are both true (ENT & ENP)
- Generates a Ripple Carry Out (RCO) when Count = 15 and ENT is TRUE.
- When cascaded to form larger counters i.e. 8 bit, 12 bit etc. the RCO of the lower bits is connected to the ENT of the next stage and ENP is treated as a global enable for all stages.

4 Bit Counter System Block Diagram



4 Bit counter ASM - 1

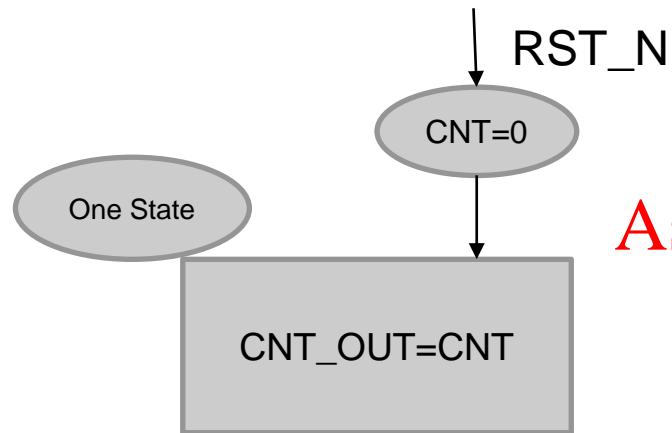


Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs

4 Bit counter ASM - 2

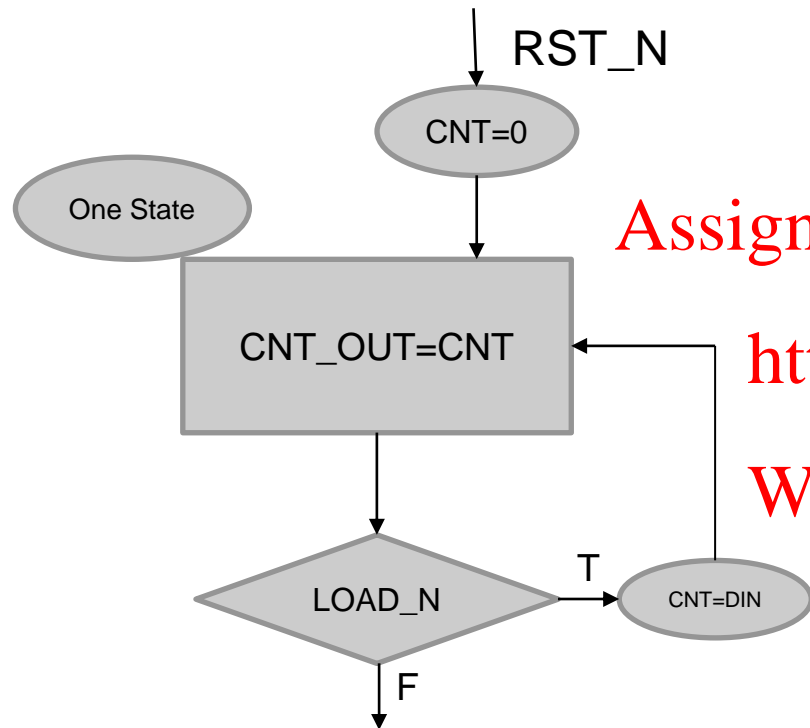


Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs

4 Bit counter ASM - 3

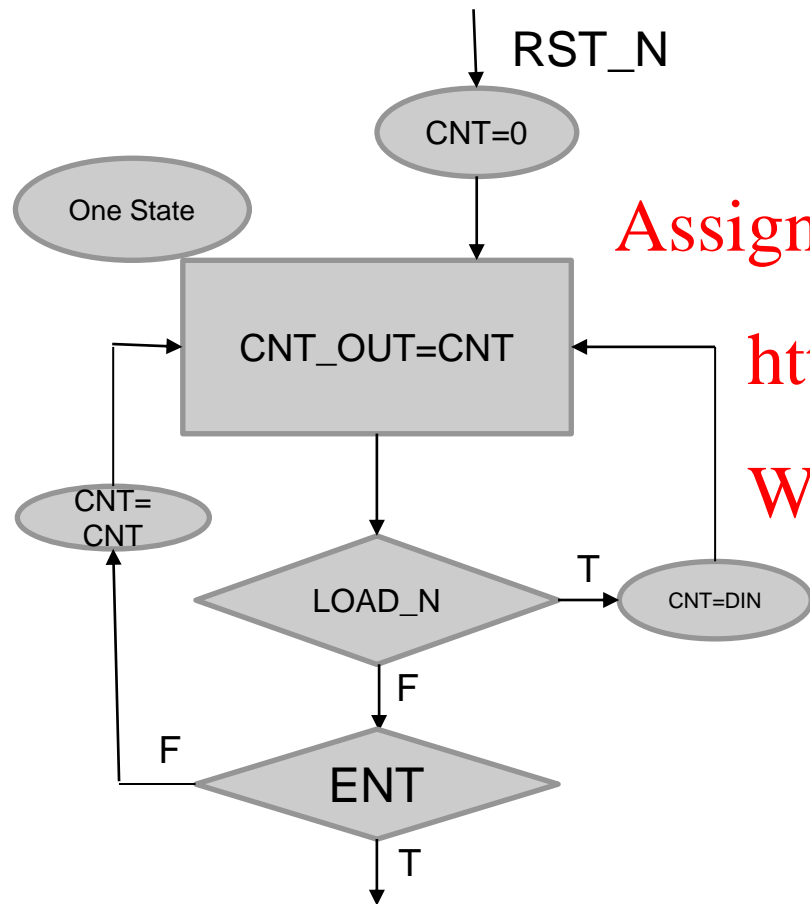


Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs

4 Bit counter ASM - 4

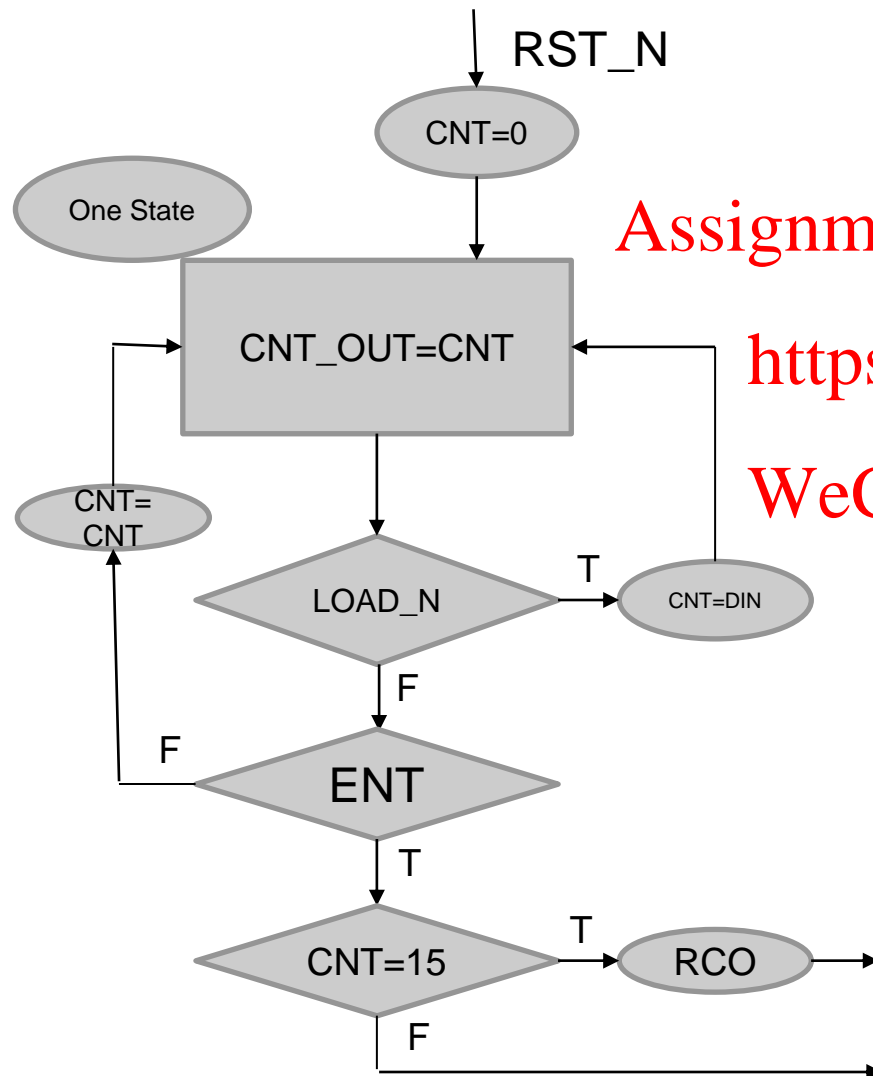


Assignment Project Exam Help


<https://tutorcs.com>

WeChat: cstutorcs

4 Bit counter ASM - 5

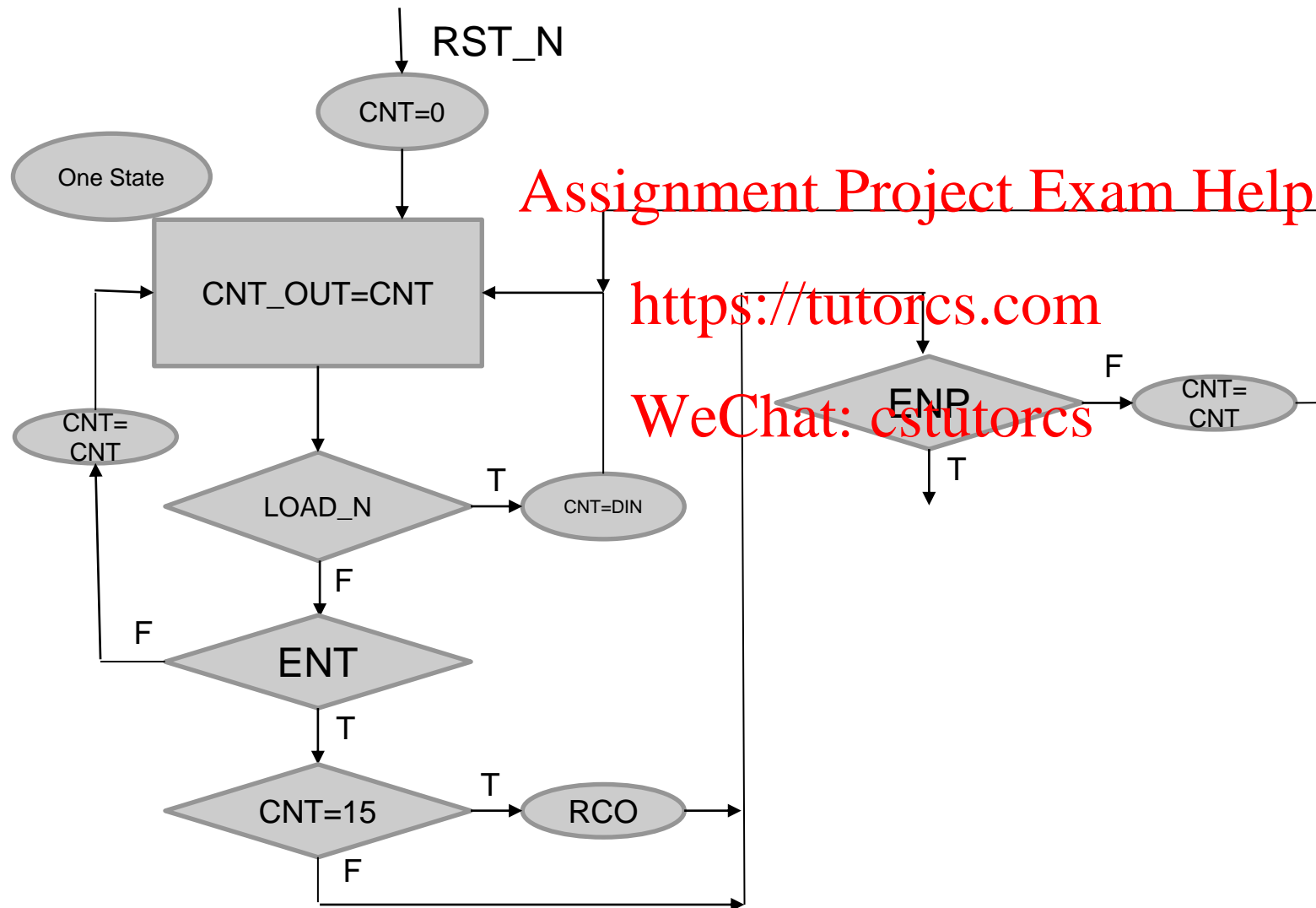

4 Bit counter ASM - 6

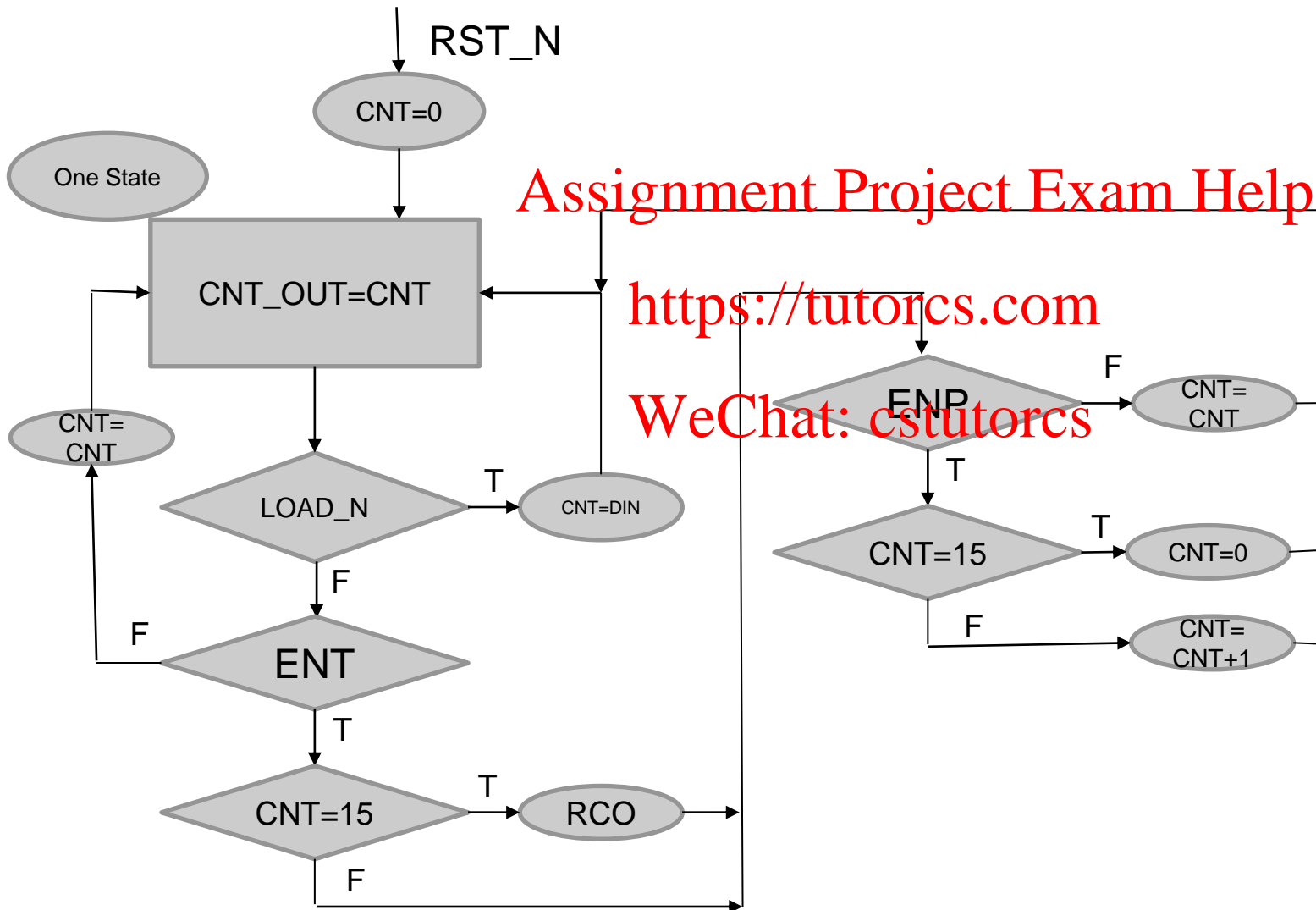

Verilog Code


```
1 module count_74161(output [3:0] cnt_out, output rco, input rst_n, load_n, clk, enp, ent, input [3:0] din);
2
3 // local reg vars to hold present and next cnt
4 reg [3:0] p_cnt, n_cnt;
5 // assign p_cnt to the output cnt_out
6 assign cnt_out = p_cnt;
7 // generate rco with assign when p_cnt = 15 & ent = 1
8 assign rco = (p_cnt == 4'd15) & ent;
9 //sequential block to synthesise flip flops
10 // note non-blocking assignments
11 always @ (posedge clk)
12 begin
13     //synchronous reset done here
14     if (rst_n == 1'b0)
15         p_cnt <= 4'b0;
16     else
17         p_cnt <= n_cnt;
18 end
19 // combinational block to generate n_cnt
20 // note using blocking assignments
21 always @ (load_n, enp, ent, din, p_cnt)
22 begin
23     // default to prevent latches
24     n_cnt = p_cnt;
25     if (load_n == 1'b0)
26         n_cnt = din;
27     else if (ent & enp)
28     begin
29         if (p_cnt == 4'd15)
30             n_cnt = 4'd0;
31         else
32             n_cnt = p_cnt + 1'b1;
33     end
34 end
35 endmodule
36
```

Assignment Project Exam Help


<https://tutorcs.com>

WeChat: cstutorcs

RTL View

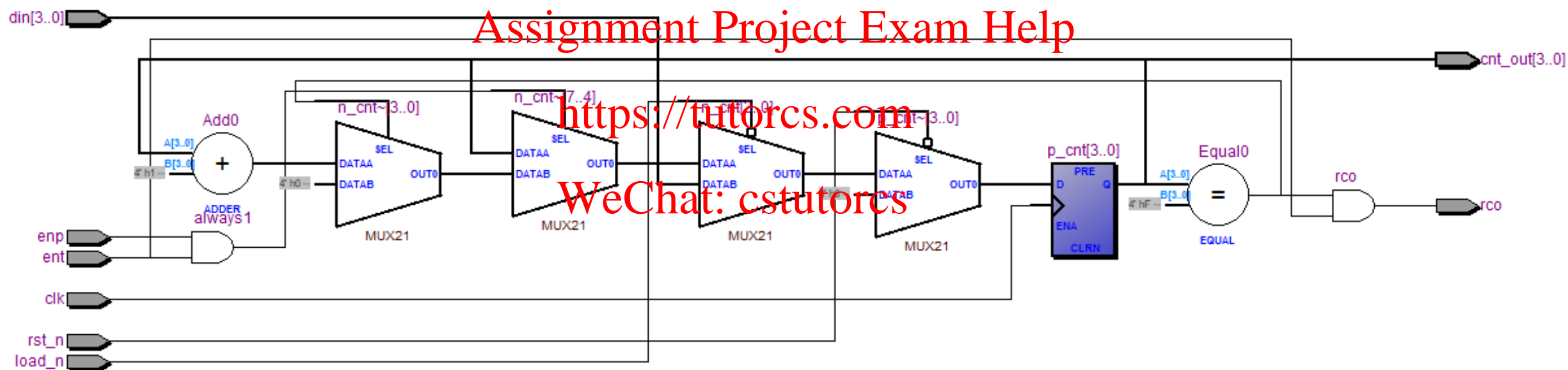

Timing Simulation – input

 

Timing Simulation – output

