

# Digital System Design

## ELEC373/473

Assignment Project Exam Help



<https://tutorcs.com>

WeChat: cstutorcs

Structural Verilog

# Module Styles

- Modules can be specified in different ways
  - 1) **Structural**: connect primitives and modules
  - 2) **RTL** (Register Transfer Level) :
    - use continuous assignments
  - 3) **Behavioral**: use **initial** and **always** blocks
    - Note that “initial” is primarily for simulation rather than for synthesis.
- A single module can use more than one method.

# Verilog Structural Model

- A schematic in text form
- Build up a circuit from gates/flip-flops
  - Gates are primitives (part of the language)
  - Flip-flops are User Defined Primitives (UDP)
- Structural design
  - 1) Create module interface (inputs and outputs)
  - 2) Instantiate the gates in the circuit
  - 3) Declare the internal wires needed to connect the gates
  - 4) Put the names of the wires in the correct port locations of the gates (For primitives, **outputs always come first**)

# Structural Example (Majority Circuit)

```
module Majority (major, V1, V2, V3);
```

```
/* start your comments with a forward  
slash and star and finish it with  
a star and forward slash. */
```

```
output major;
```

```
input V1, V2, V3;
```

```
wire N1, N2, N3;
```

```
and A0 (N1, V1, V2);
```


```
and A1 (N2, V2, V3);
```

```
and A2 (N3, V3, V1);
```

```
or Or0 (major, N1, N2, N3);
```

```
// Use two forward slashes for one line comments
```
 
```
endmodule /* Each statement in Verilog must terminate with  
a semicolon except endmodule.*/
```



All **identifiers** (names) in Verilog have a scope (i.e., domain of definition) that is local to the module, function, task or named block in which they are declared.

# Identifiers

- Identifiers (names) are composed of a sequence of
  - case sensitive alphabetic characters
  - digits (0 to 9)
  - underscore ( \_ ) and ( \$ ) symbol
- Identifiers cannot start with a digit or the ( \$ ) symbol
- Spaces are not allowed in an identifier
- An identifier can be up to 1024 characters long.

## Legal Identifier

Full\_Adder

Decoder2

\_\$Multiplier1

Half\_Adder

## Illegal Identifier

Full-Adder

2Decoder

\$Multiplier1

Half Adder

- Use the same rules for module names in Quartus II or you may get errors during the simulation

# Representing Numbers

- Representation: `<size>'<base><number>`
  - `size` => number of **BITS** (regardless of base used)
  - `base` => base the given number is specified in
  - `number` => the actual value in the given base
- Can use different bases
  - Decimal (d or D) – default if no base specified!
  - Hex (h or H)
  - Octal (o or O)
  - Binary (b or B)
- Size defaults to at least 32...
  - You should specify the size explicitly!
  - Why create 32-bit register if you only need 5 bits?
  - May cause compilation errors on some compilers

Assignment Project Exam Help

<https://tutorcs.com>


WeChat: cstutorcs

# Number Examples

Number	Decimal Equivalent	Actual Binary
4'd3	3	0011
8'ha	10	00001010
8'o26	22	00010110
5'b111	7	00111
8'b0101_1101	93	01011101
8'bx1101	-	xxxx1101
-8'd6	-6	11111010

*Numbers with MSB of x or z are extended with that value*

# Full Adder Example

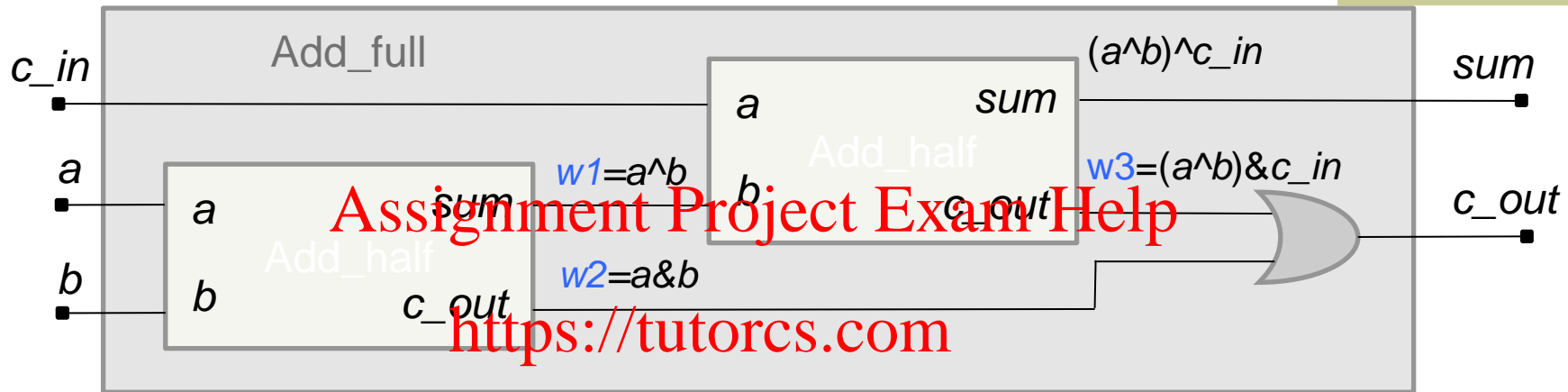

```

module Add_full (sum, c_out, a, b, c_in),
  input      a, b, c_in;
  output    sum, c_out;
  wire      w1, w2, w3;
  Add_half M1 (w1, w2, a, b);
  Add_half M2 (sum, w3, c_in, w1);
  or        (c_out, w2, w3);
endmodule

```

```


module Add_half (sum, c_out, a, b);
  input      a, b;
  output    c_out, sum;
  xor       (sum, a, b);
  and       (c_out, a, b);
endmodule

```




# Functional and Timing Simulations with Quartus II

Functional Simulation

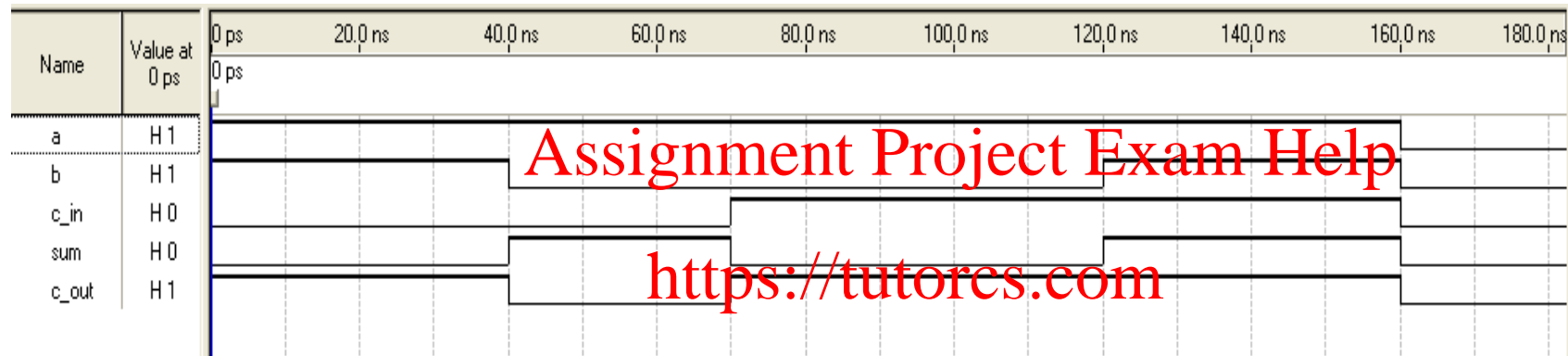

Timing Simulation

 


Propagation delay




# Design Hierarchy
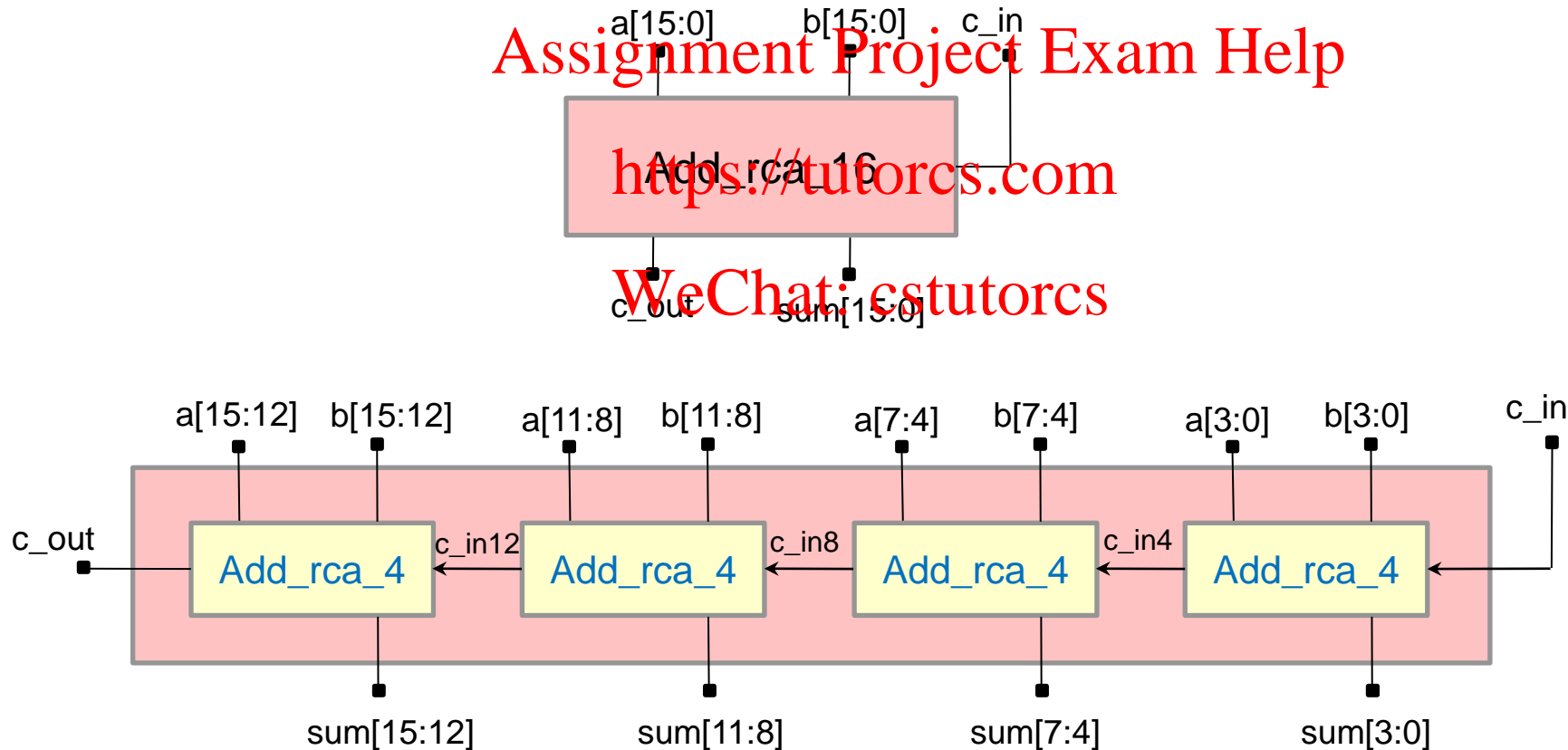
## Example: Ripple Carry Adder

A 16-bit ripple-carry adder can be formed by cascading four 4-bit ripple-carry adders.



# Design Hierarchy

  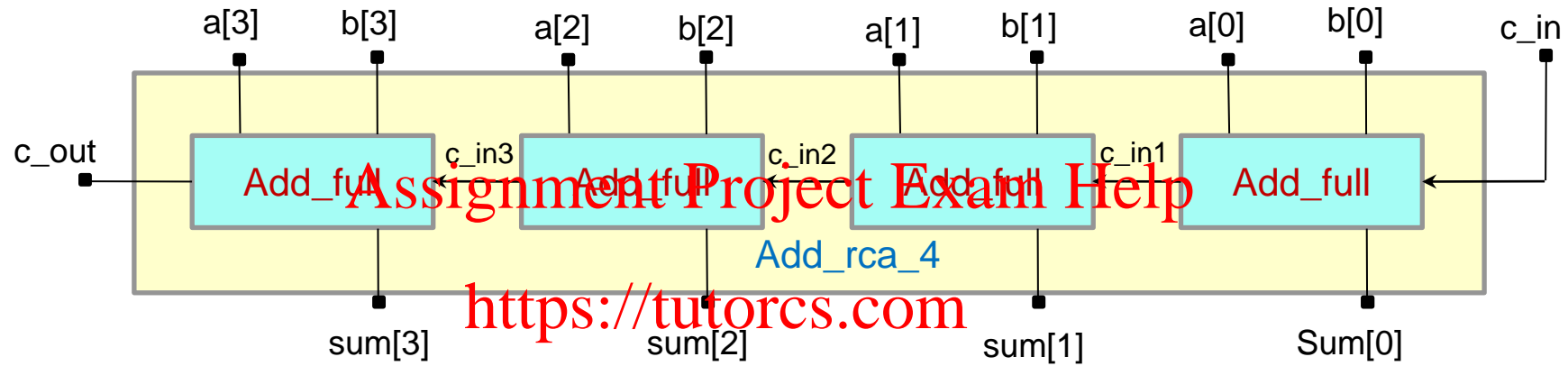

# Structural Verilog Code (1)

```
1  module Add_rca_16 (sum, c_out, a, b, c_in);
2      output[15:0]    sum;
3      output          c_out;
4      input[15:0]     a, b;
5      input           c_in;
6      wire            c_in4, c_in8, c_in12;
7
8      Add_rca_4 M1 (sum[3:0], c_in4, a[3:0], b[3:0], c_in);
9      Add_rca_4 M2 (sum[7:4], c_in8, a[7:4], b[7:4], c_in4);
10     Add_rca_4 M3 (sum[11:8], c_in12, a[11:8], b[11:8], c_in8);
11     Add_rca_4 M4 (sum[15:12], c_out, a[15:12], b[15:12], c_in12);
12 endmodule
13
14 module Add_rca_4 (sum, c_out, a, b, c_in);
15     output[3:0]    sum;
16     output          c_out;
17     input[3:0]     a, b;
18     input           c_in;
19     wire            c_in1, c_in2, c_in3;
20
21     Add_full M1 (sum[0], c_in1, a[0], b[0], c_in);
22     Add_full M2 (sum[1], c_in2, a[1], b[1], c_in1);
23     Add_full M3 (sum[2], c_in3, a[2], b[2], c_in2);
24     Add_full M4 (sum[3], c_out, a[3], b[3], c_in3);
25 endmodule
```

Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs




- Any identifier that is referenced without having a type declaration is by default of type **wire** (The pointed declarations can be removed).

# Structural Verilog Code (2)


```
26
27 module Add_full (sum, c_out, a, b, c_in);
28     output      sum, c_out;
29     input       a, b, c_in;
30     wire        w1, w2, w3;
31     Add_half    M1 (w1, w2, a, b);
32     Add_half    M2 (sum, w3, c_in, w1);
33     or          (c_out, w2, w3);
34 endmodule
35
36 module Add_half (sum, c_out, a, b);
37     output      c_out, sum;
38     input       a, b;
39     xor         (sum, a, b);
40     and         (c_out, a, b);
41 endmodule
42
```

- A **vector** in Verilog is denoted by square brackets, e.g. **Sum[7:0]**
- The leftmost index in the bit range is the most significant bit, and the rightmost is the least significant bit.
- If **Sum** has a value of **4** then: **Sum[3:0]=4** , **Sum[2]=1**, and **Sum[5:1]=2**
- **Wires** in Verilog establish connectivity between design objects.

# Synthesised Design (RTL Viewer)

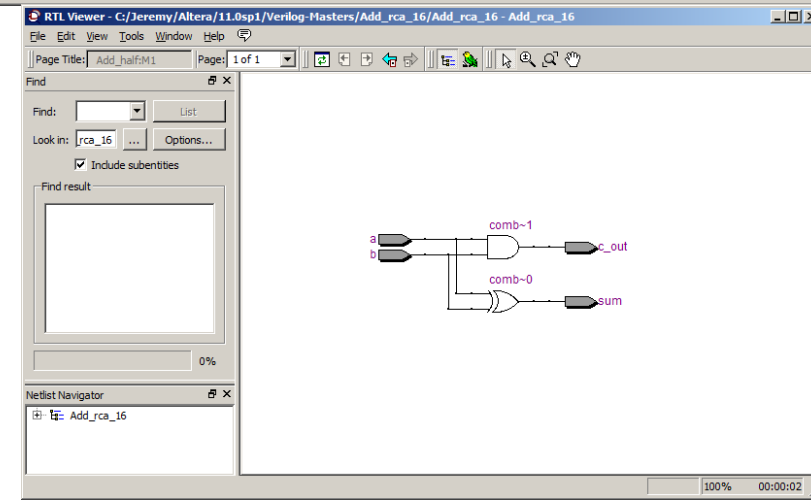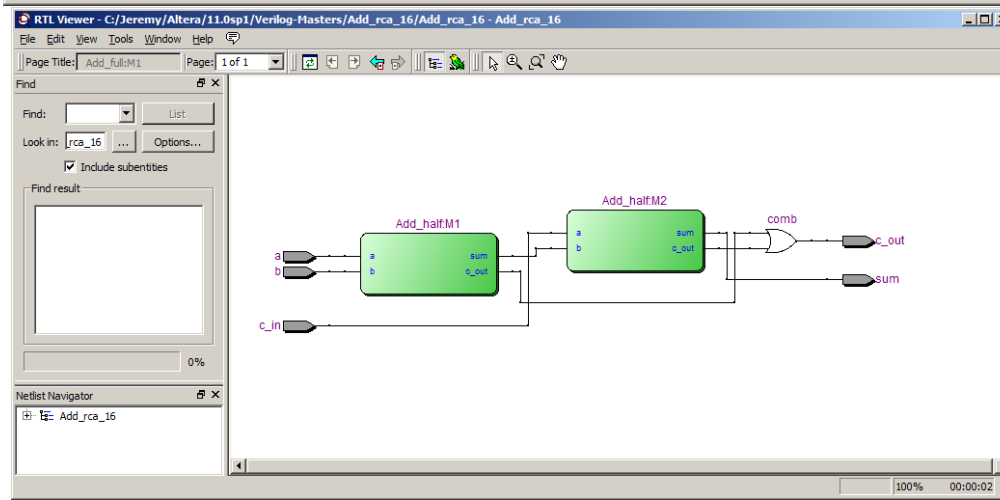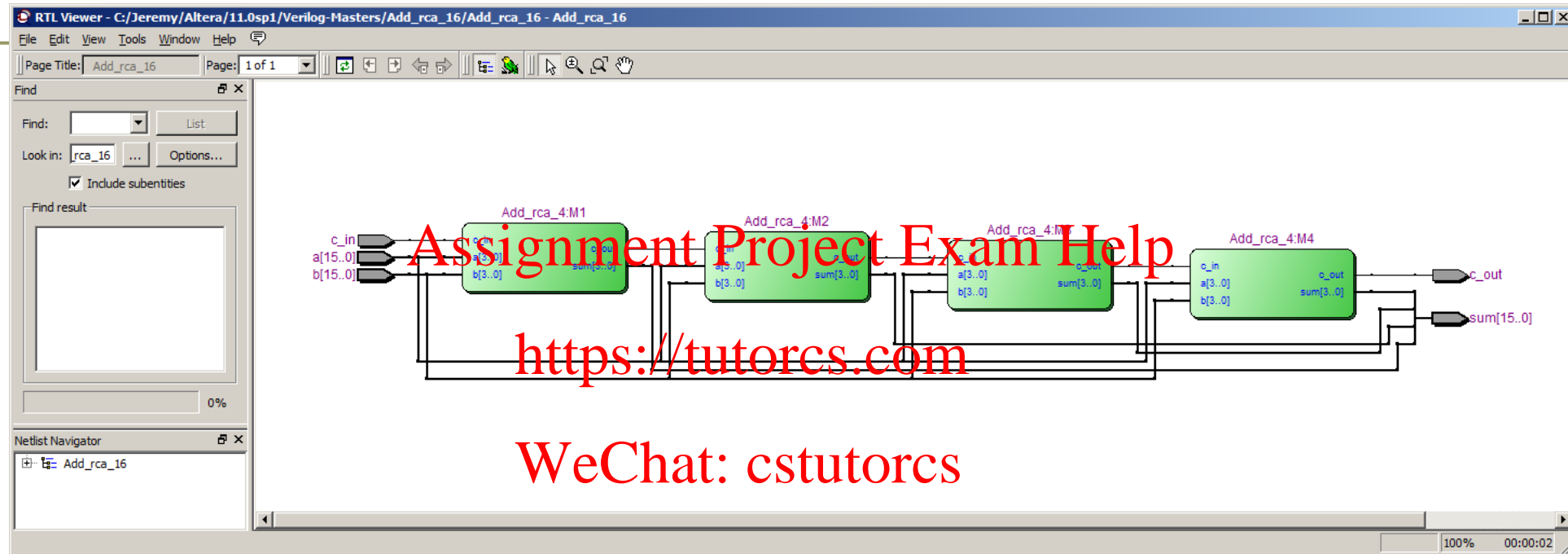

# Simulation

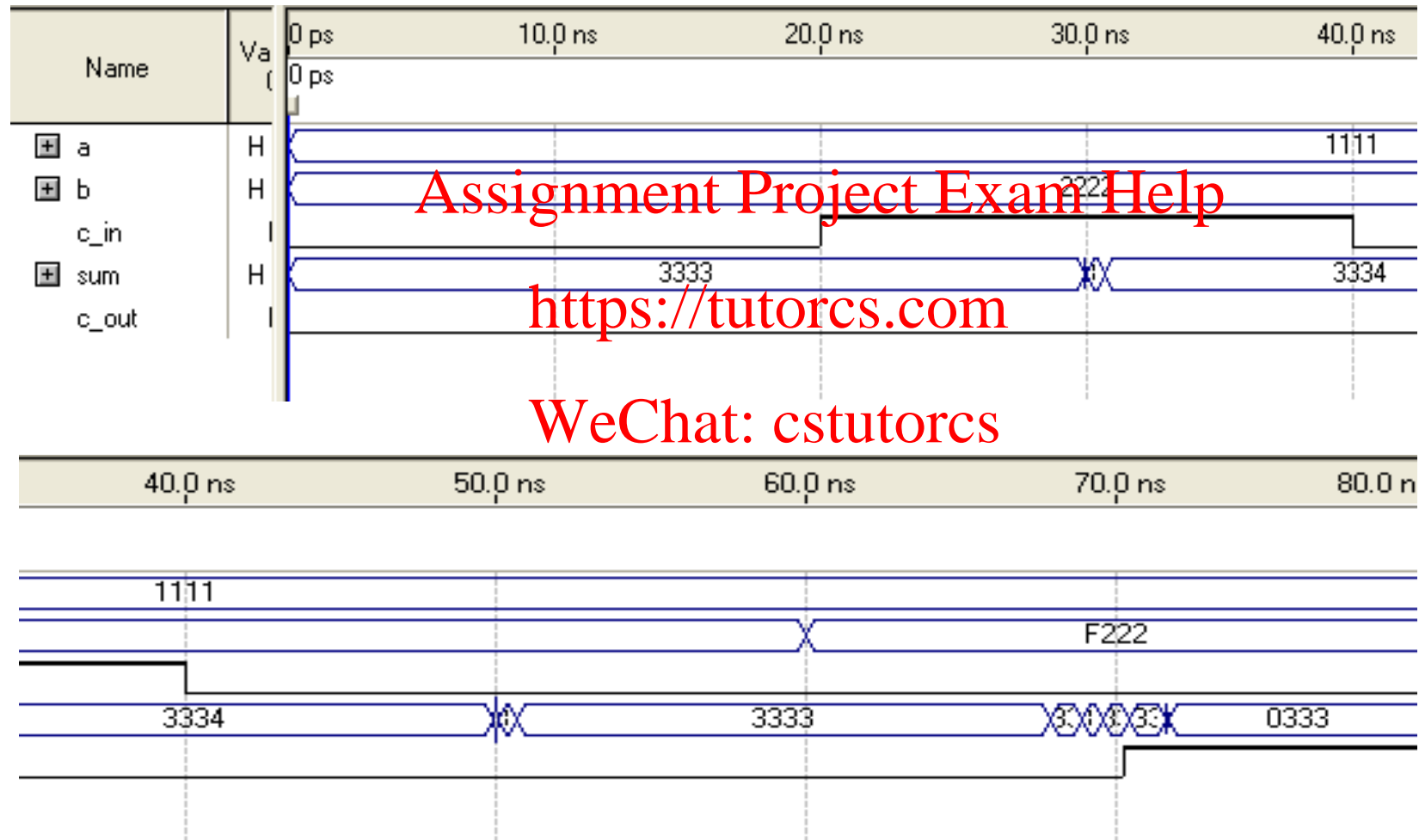

# Associating Ports of Instantiated Modules

## ■ By Position

- The names of the connecting signals can be different but they must be consistent with the module declaration.

■ **module** Add\_half ( sum, c\_out, a, b );

■ Add\_half M1 ( w1, w2, a, b );

Module declaration


Module instantiation

## ■ By Name

- This method is useful for modules with many ports.
- Syntax: *.formal\_name* (*actual\_name*)
- Add\_half M1 (.c\_out (w2), .b(b), .a(a), .sum(w1) );



# Example: 2-bit Comparator

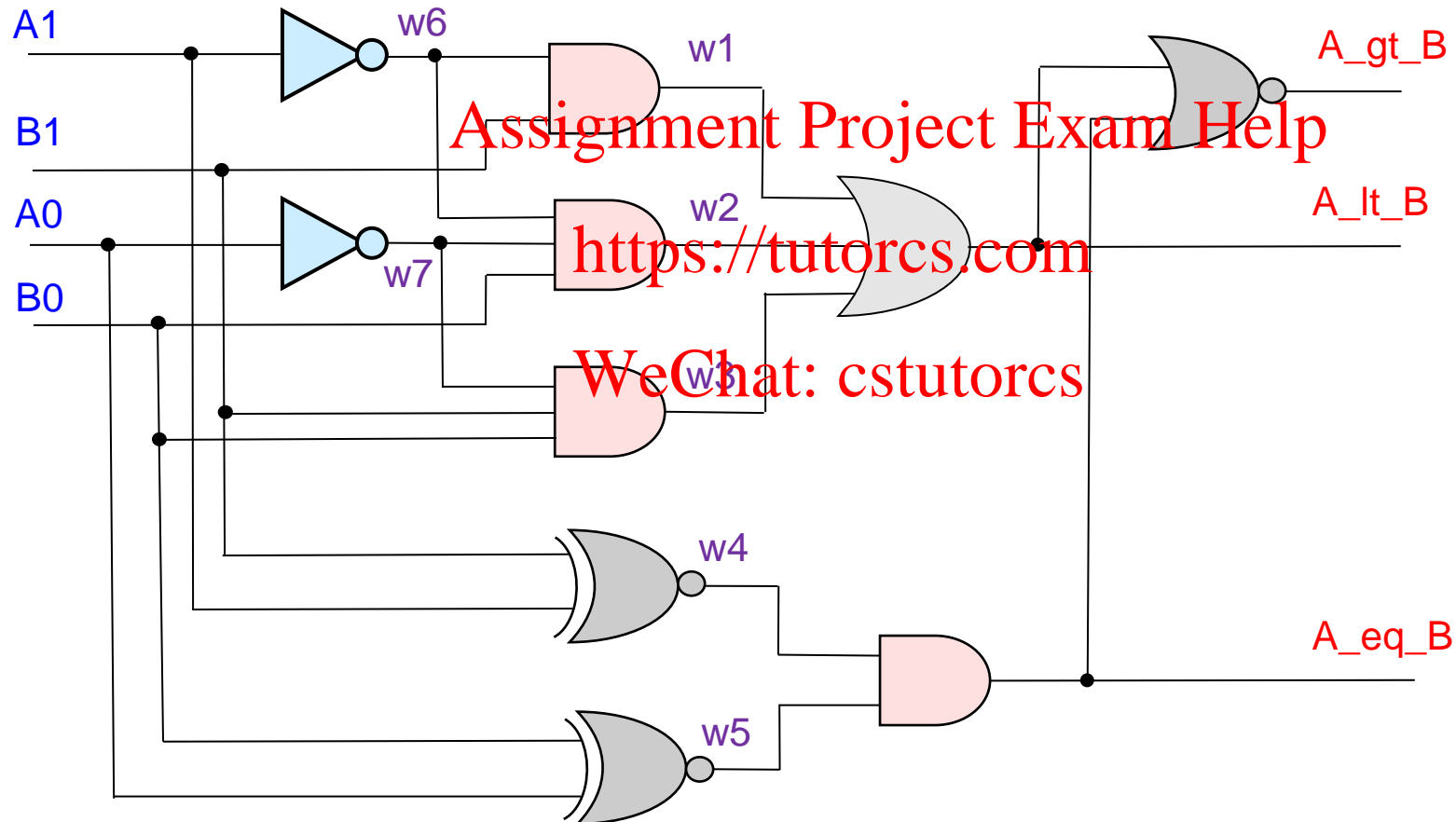

# Structural Verilog Code


```
1  module Compare_2_str(A_gt_B, A_lt_B, A_eq_B, A0, A1,B0, B1);
2      output  A_gt_B, A_lt_B, A_eq_B ;
3      input   A0, A1,B0, B1 ;
4
5      nor     (A_gt_B, A_lt_B, A_eq_B);
6      or      (A_lt_B,w1,A0);
7      and     (w1,w6,B1);
8      and     (w2,w6,w7,B0);
9      and     (w3,w7,B1,B0);
10     and     (A_eq_B,w4,w5);
11     not     (w6,A1);
12     not     (w7,A0);
13     xnor    (w4,A1,B1);
14     xnor    (w5,A0,B0);
15 endmodule
```

Assignment Project Exam Help


<https://tutorcs.com>

WeChat: cstutorcs

# Timing Simulation

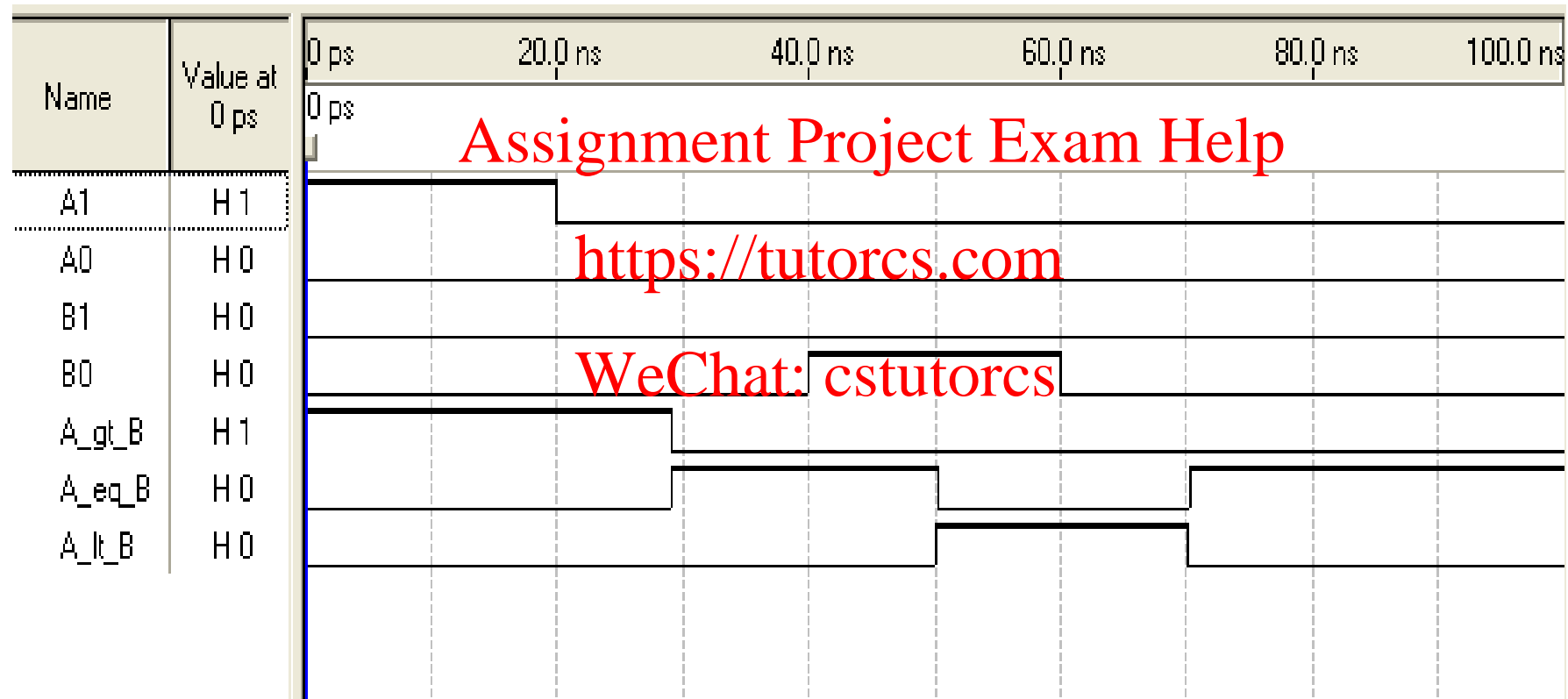

# 4-bit Comparator

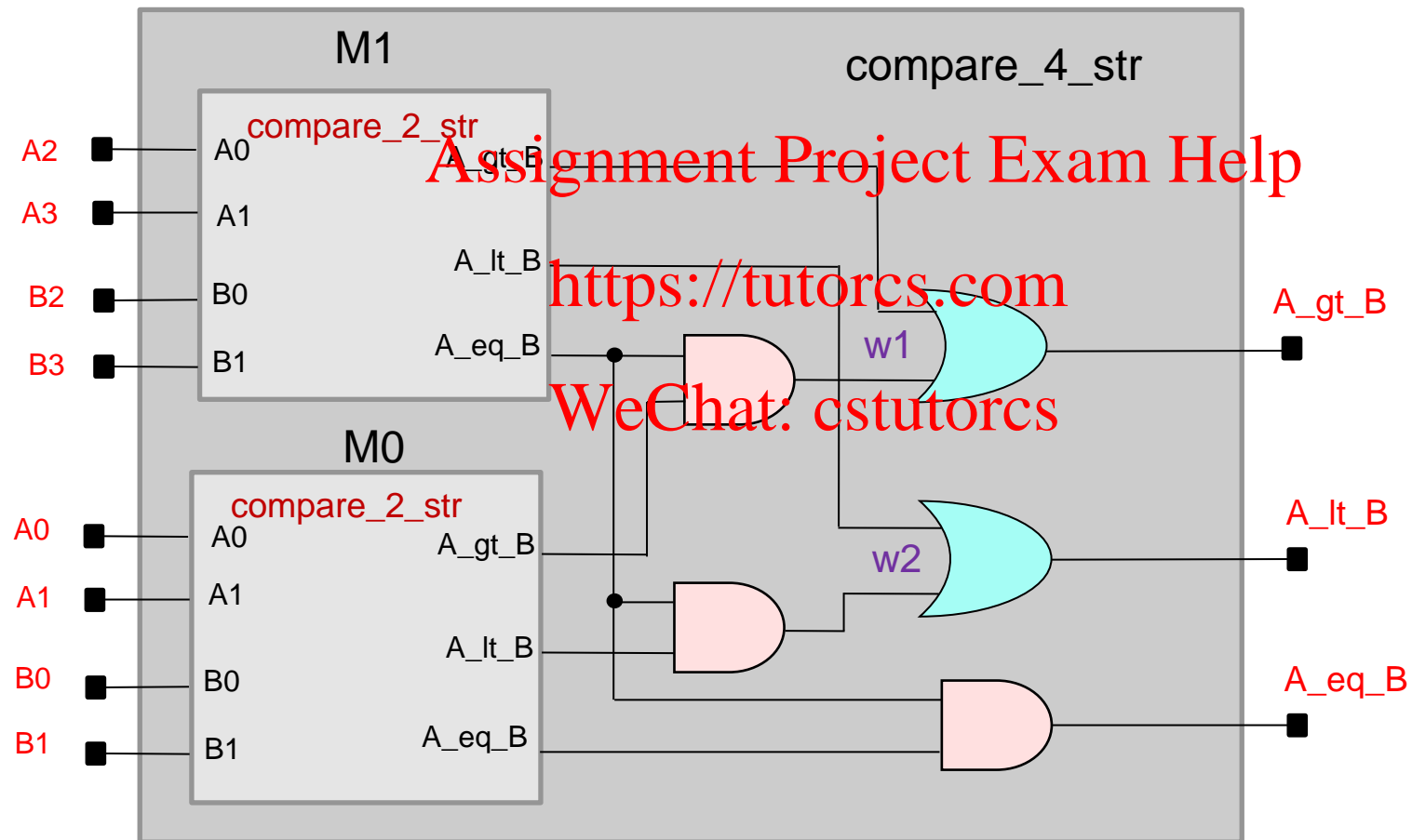

# Verilog Code


```
1 module Compare_4_str(A_gt_B, A_lt_B, A_eq_B, A, B);
2     output A_gt_B, A_lt_B, A_eq_B;
3     input  [3:0] A, B;
4
5     Compare_2_str M1 (A_gt_B_M1, A_lt_B_M1, A_eq_B_M1, A[2], A[3], B[2], B[3]);
6     Compare_2_str M0 (A_gt_B_M0, A_lt_B_M0, A_eq_B_M0, A[0], A[1], B[0], B[1]);
7
8     or      (A_gt_B, A_gt_B_M1, w1);
9     or      (A_lt_B, A_lt_B_M1, w2);
10    and     (A_eq_B, A_eq_B_M1, A_eq_B_M0);
11    and     (w1, A_eq_B_M1, A_gt_B_M0);
12    and     (w2, A_eq_B_M1, A_lt_B_M0);
13
14 endmodule
15
```

Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs

# Synthesised design

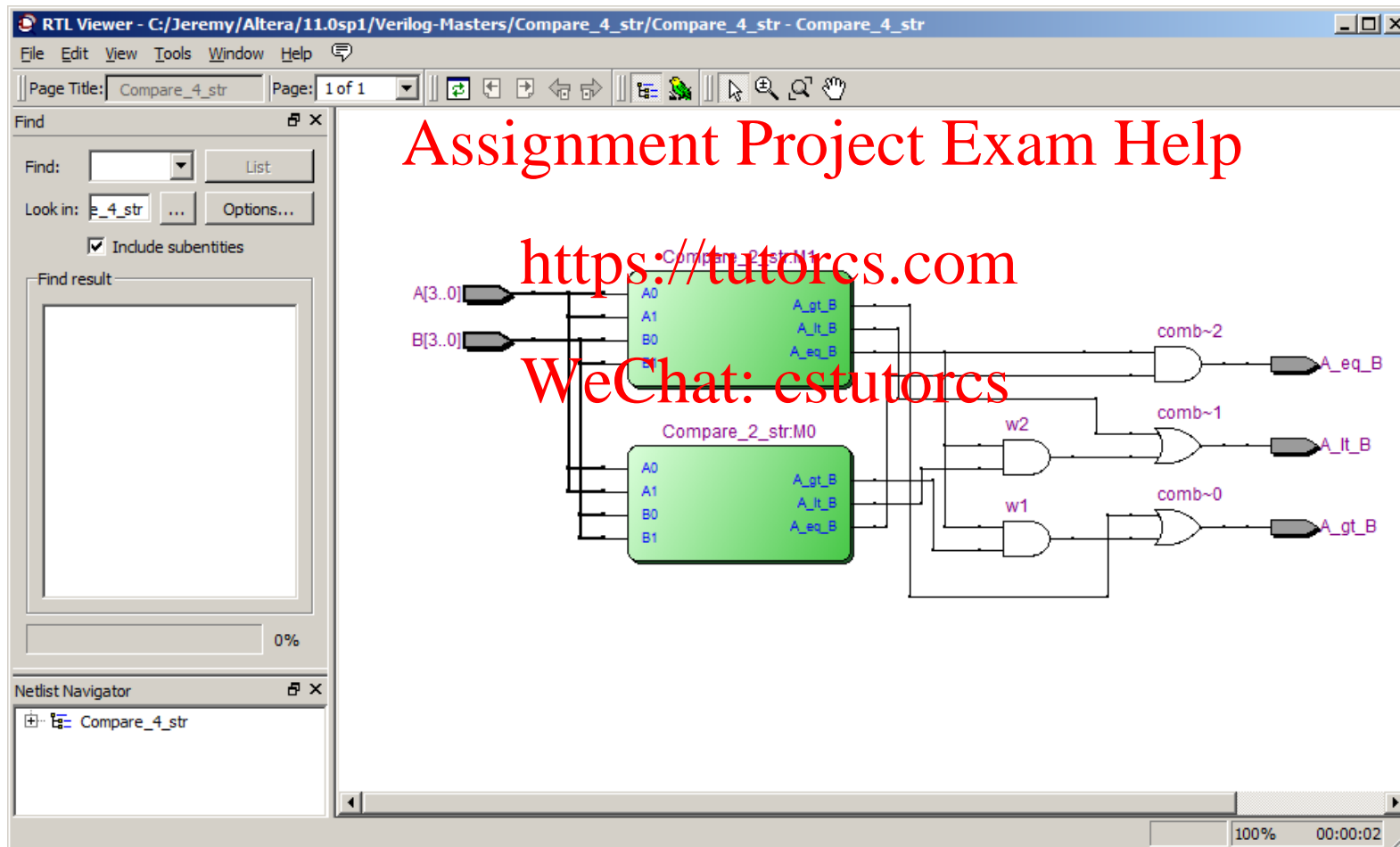

# Functional Simulation

