

Digital System Design

ELEC373/473

Assignment Project Exam Help



<https://tutorcs.com>

WeChat: cstutorcs

Algorithmic State Machines (ASM)

BCD to Excess 3

Verilog Sequential Template

```
module model_name (list of outputs and inputs);  
  external signal declarations  
  internal signal declarations  
  begin  
    -- the state process defines the storage elements  
    always @ (posedge (negedge) clock [optional reset])  
    begin  
      verilog statements for storage elements (normally nonblocking)  
    end  
  
    -- the comb process defines the combinational logic  
    always @ (level sensitivity list – usually includes all inputs and state vars)  
    begin  
      verilog statements which specify combinational logic  
      (normally use a case statement to identify states)  
    end  
  end  
endmodule;
```

BCD to XS-3 Code Converter

- An Excess-3 code is obtained by adding 0011 to the BCD code.
- An Excess-3 code is self complementing. The 9's complement of a number can be obtained by bitwise complementing it.
- The 10's complement of an XS-3 is its 9's complement plus 1.
- Negative numbers are represented by their 10's complement.
- Example:
 - $873 - 218 = 655$
 - $-218 \longrightarrow 781$ (9's complement)
 - $-218 \longrightarrow 782$ (10's complement)
 - $873 + 782 = 1655$ (overflow)
 - $1655 - 1000 = 655$ (correct result)

Decimal	BCD	Excess-3
0	0000	0011
1	0001	0100
2	0010	0101
3	0011	0110
4	0100	0111
5	0101	1000
6	0110	1001
7	0111	1010
8	1000	1011
9	1001	1100


BCD to XS-3 Code Converter

- A Mealy FSM is designed to convert a serial bit stream of a BCD code to Excess-3 bit stream.

Assignment Project Exam Help


<https://tutorcs.com>

WeChat: cstutorcs

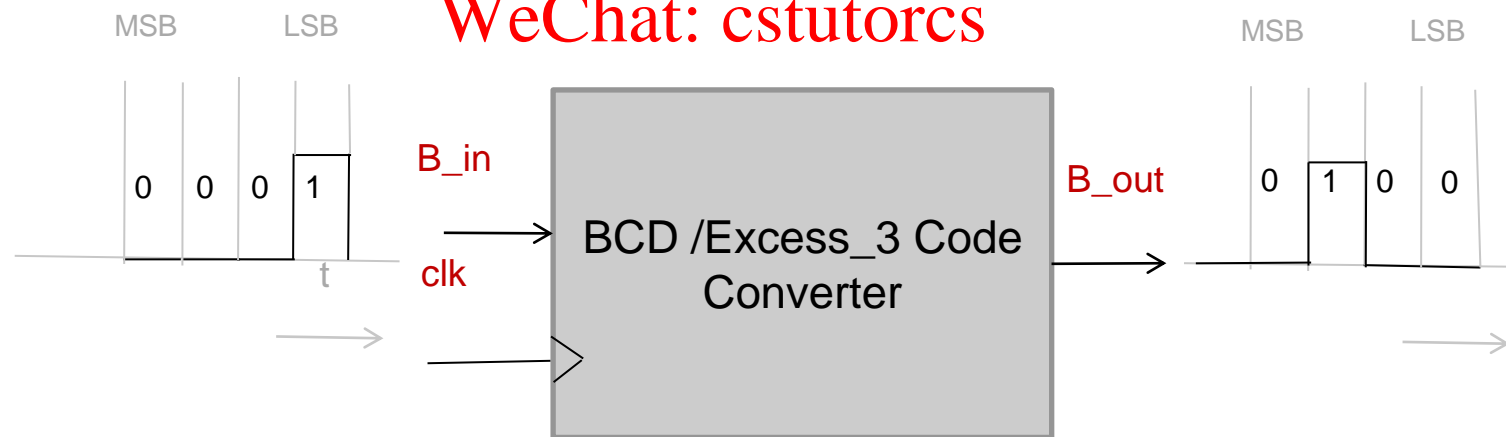

LSB is inserted first.


ASM Chart

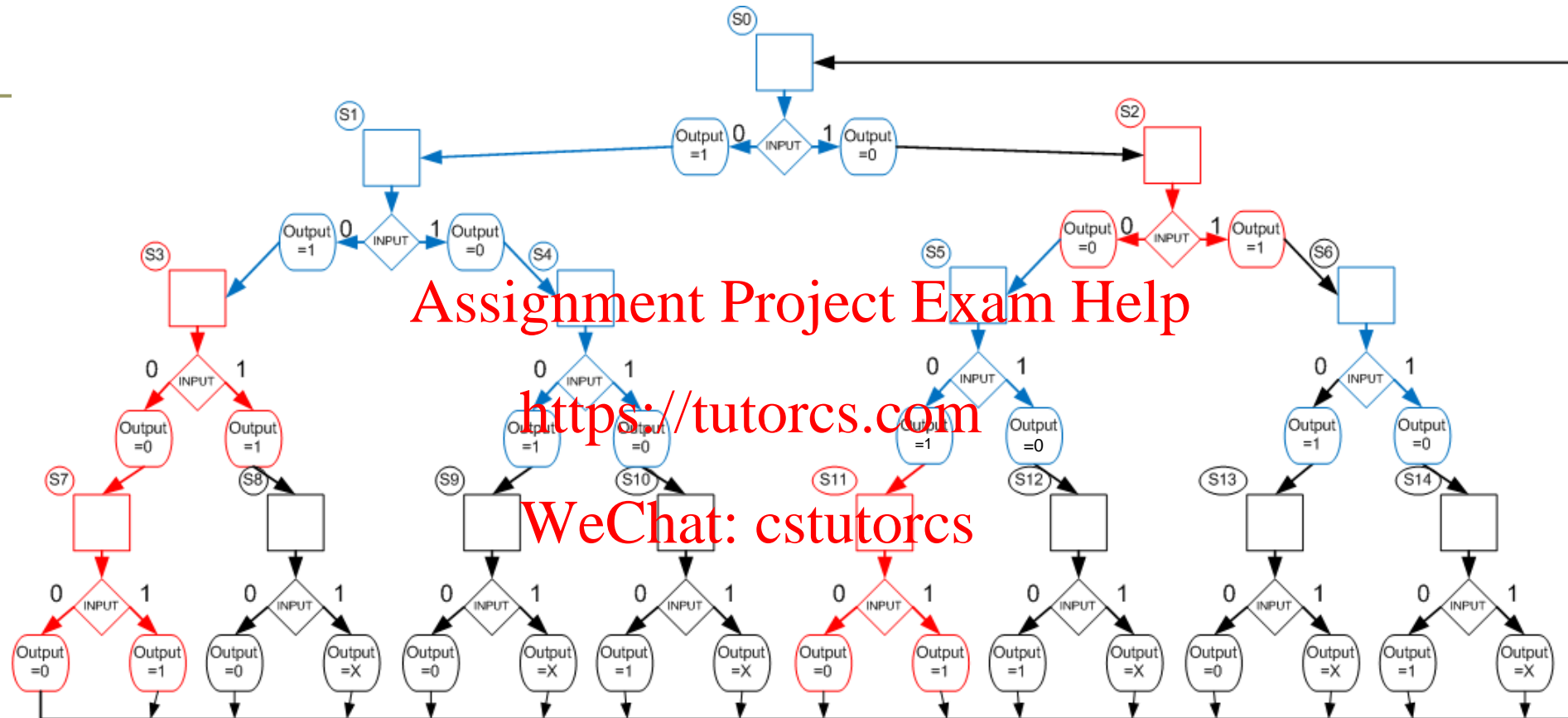

There are 4 possible types of states in each time period.

- 1) The output is the same as the input (red states – S2, S3, S7, S11).
- 2) The output is the inversion of the input (blue states – S0, S1, S4, S5, S6).
- 3) The output is 1 for valid input values (could be S10, S12, or S14).
- 4) The output is 0 for valid input values (could be S8, S9, or S13).


State Reduction (1)

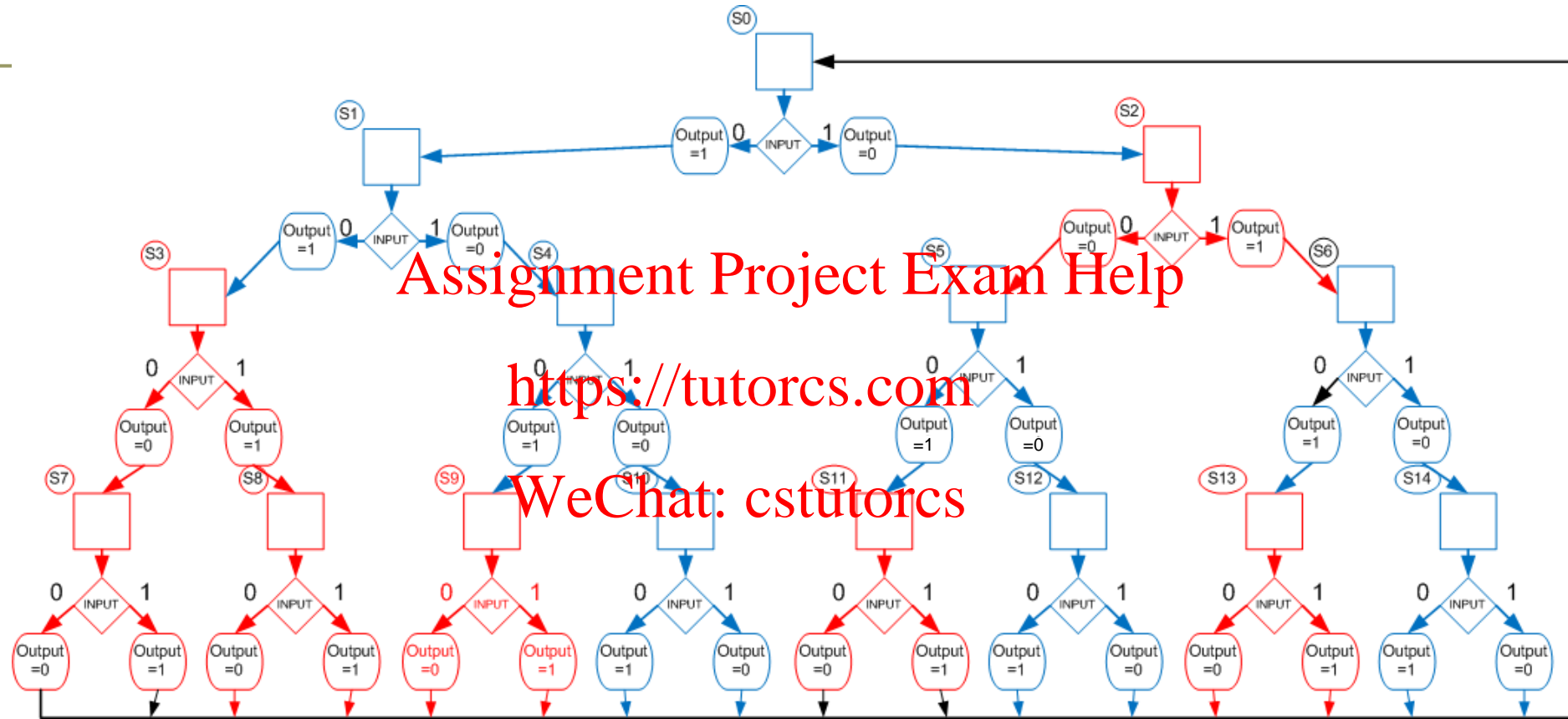

By setting the don't cares the state types can be reduced to 2 types.


- 1) The output is the same as the input (red states – S2, S3, S7, S8, S9, S11, S13).
- 2) The output is the inversion of the input (blue states–S0,S1,S4,S5,S6,S10,S12,S14).

State Reduction (2)

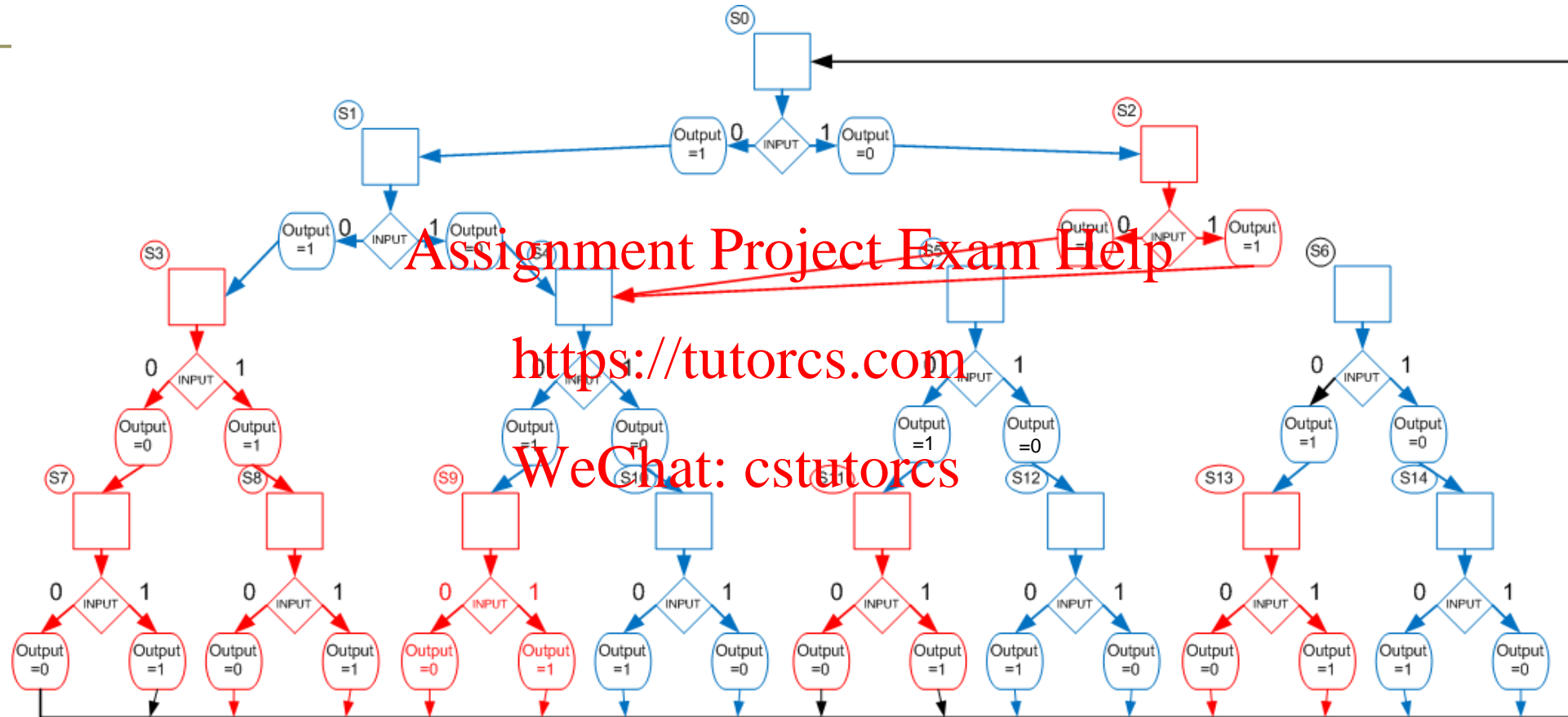


By going from S2 to S4 we get the same functionality but can eliminate six states
S5, S6, S11, S12, S13 & S14


State Reduction (3)

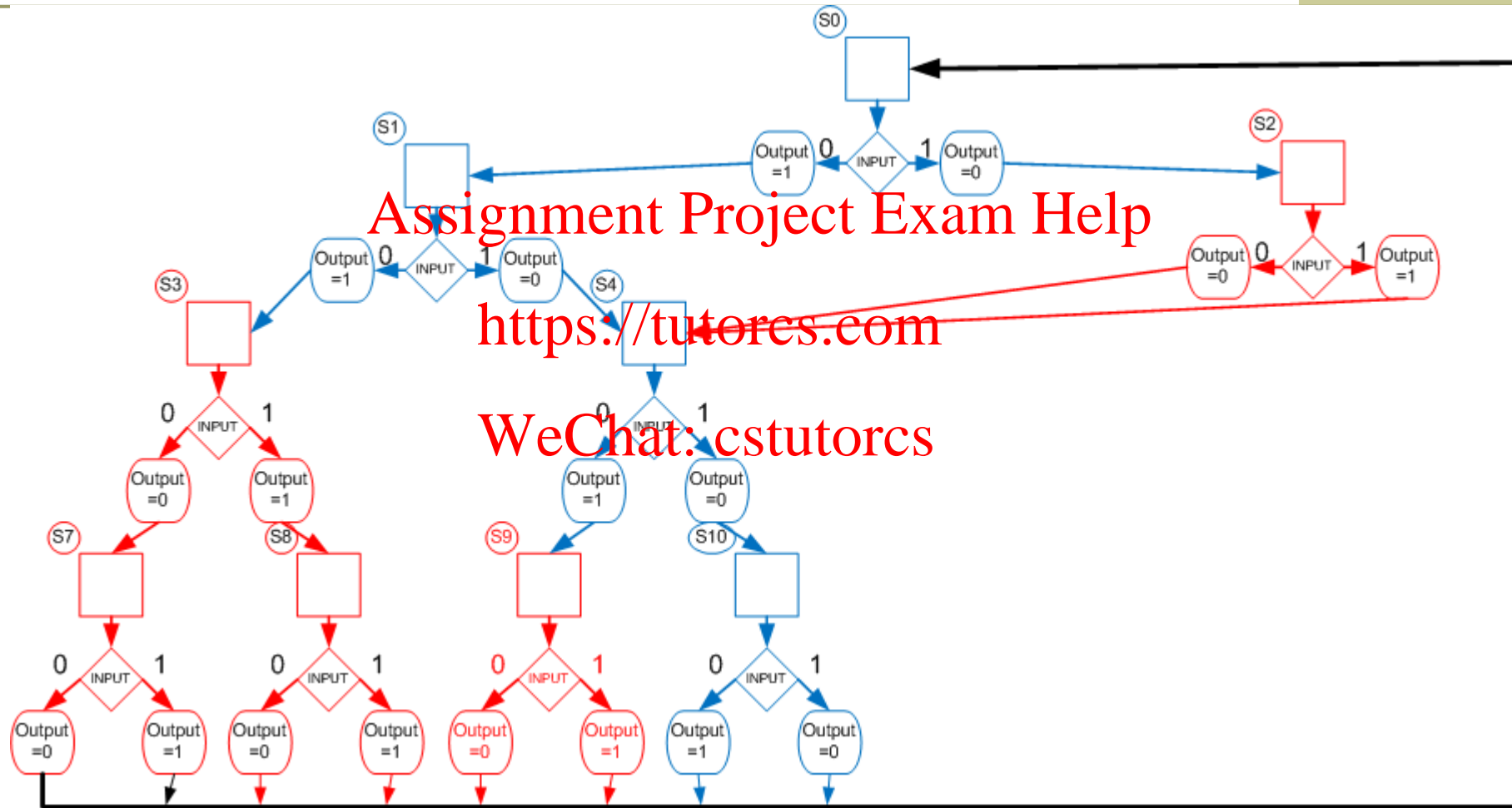


State Reduction (4)

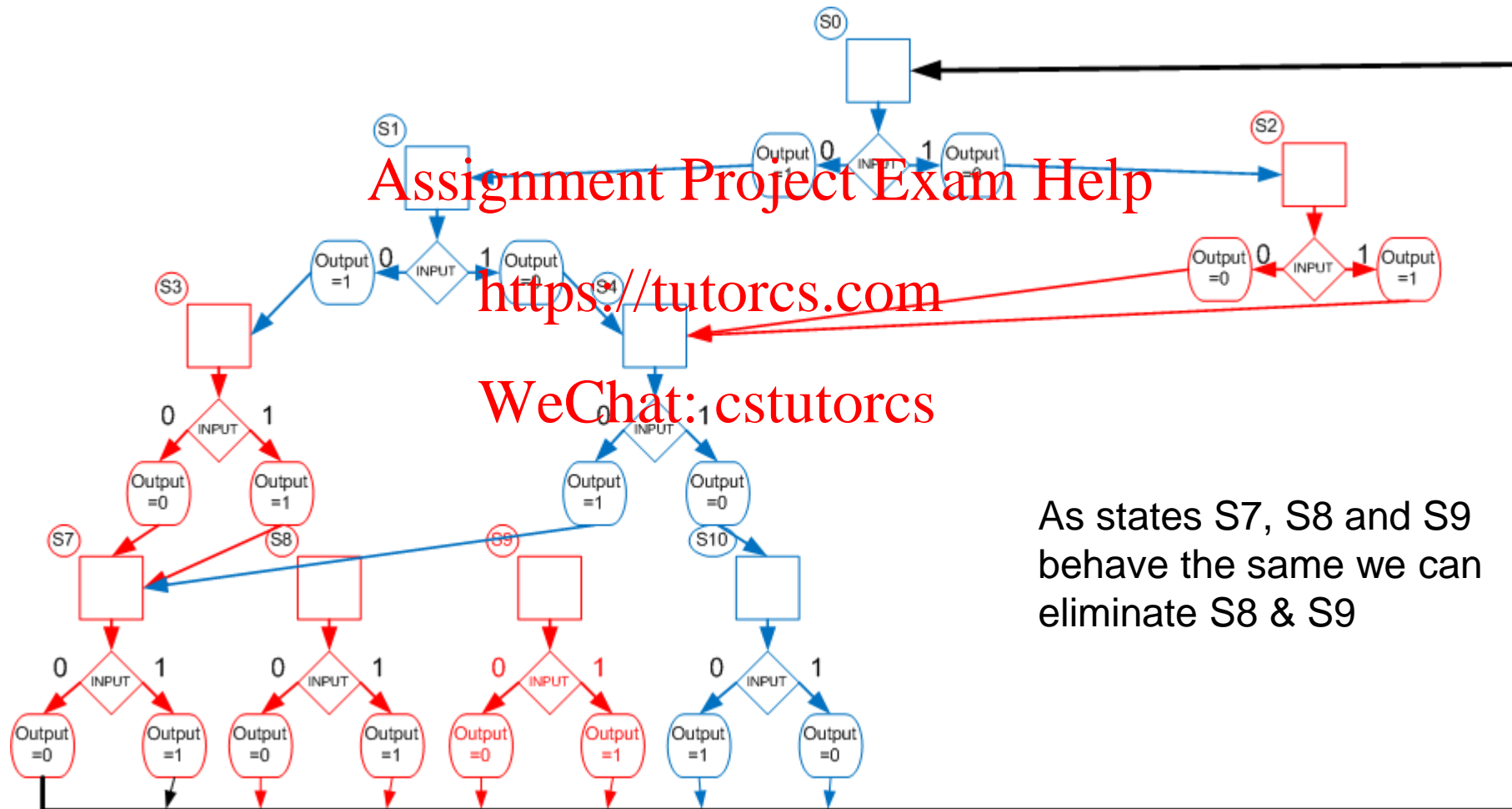


State Reduction (5)

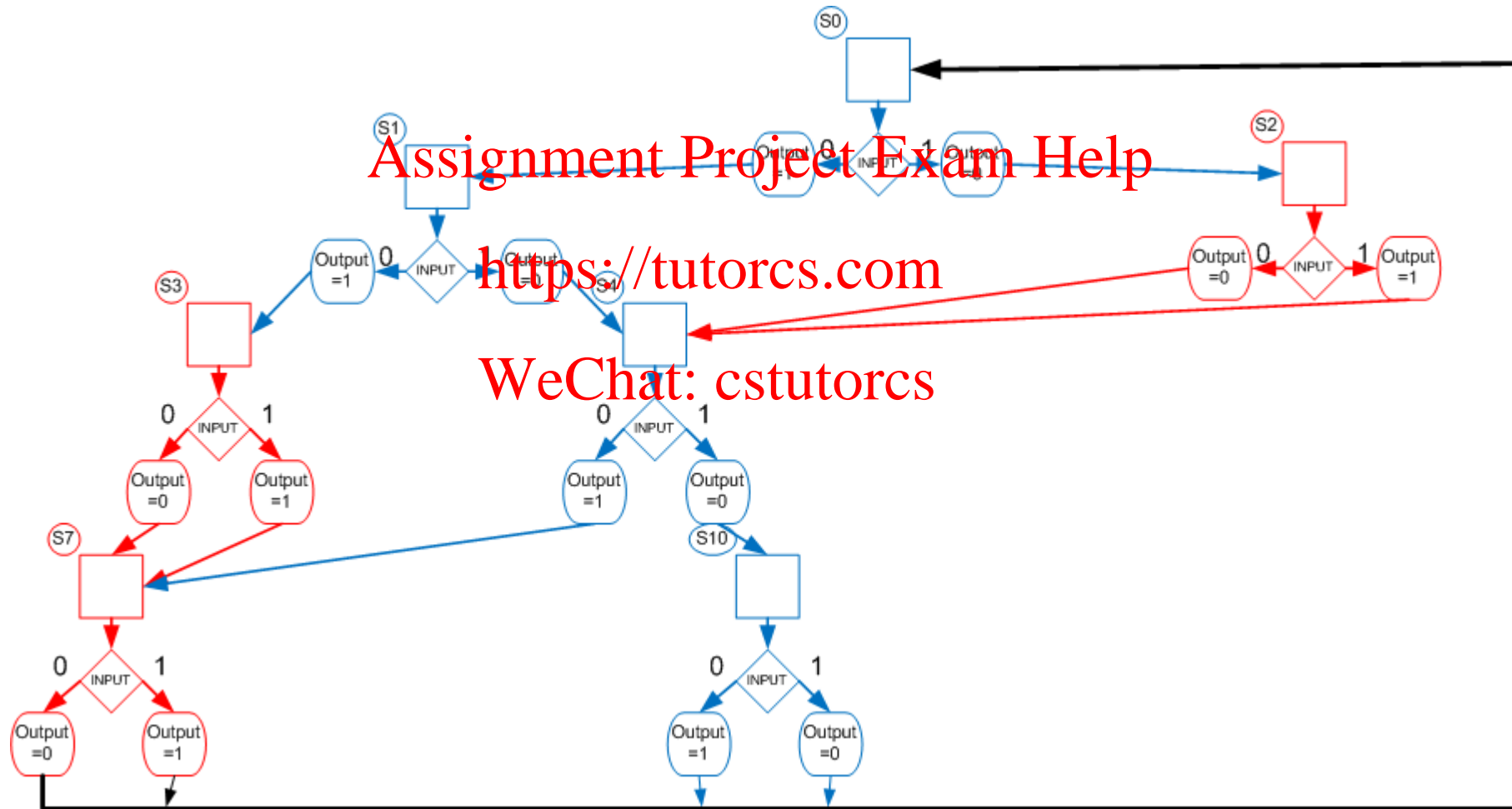

State Reduction (6)

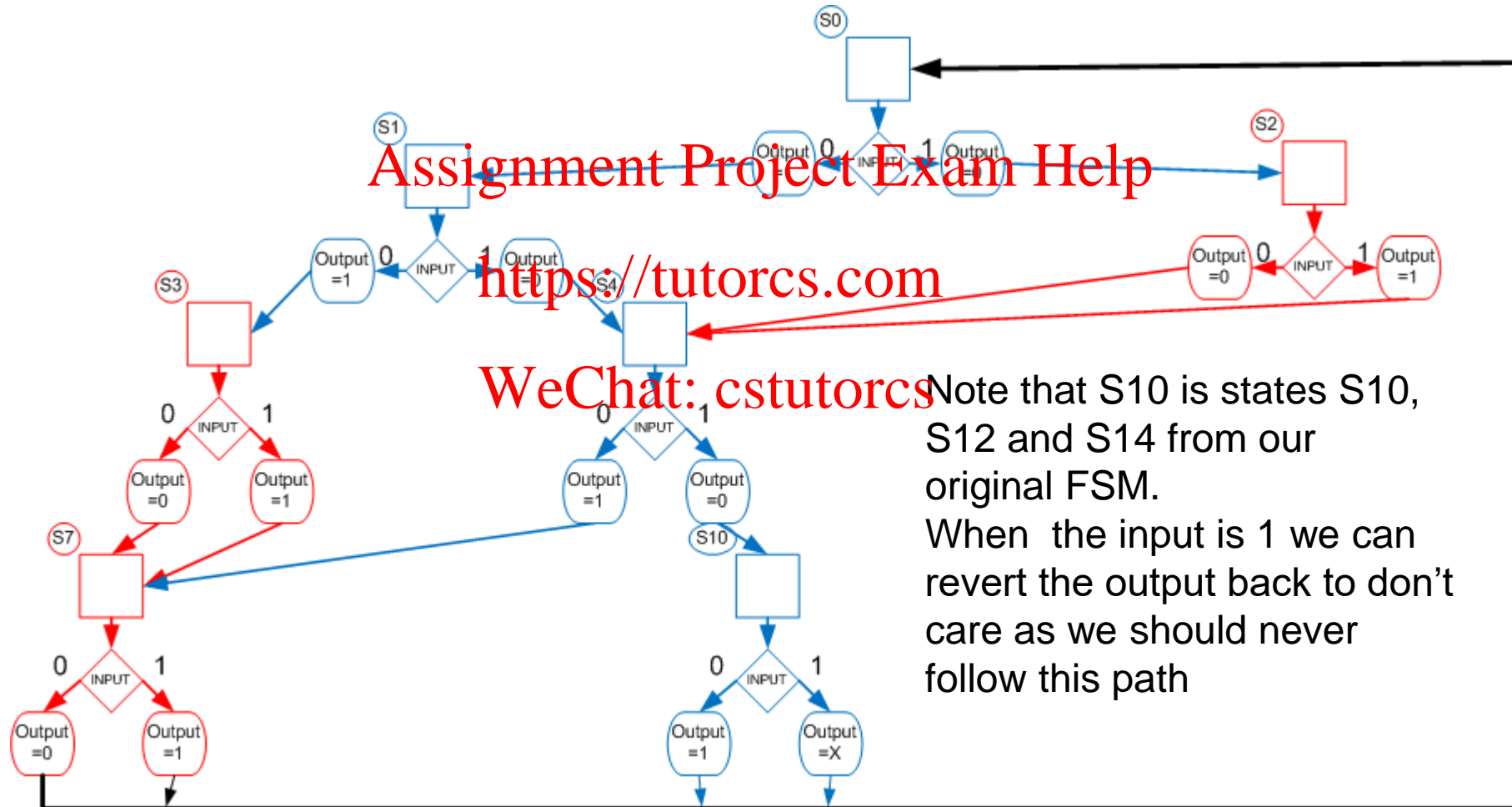

State Diagram with Minimum States

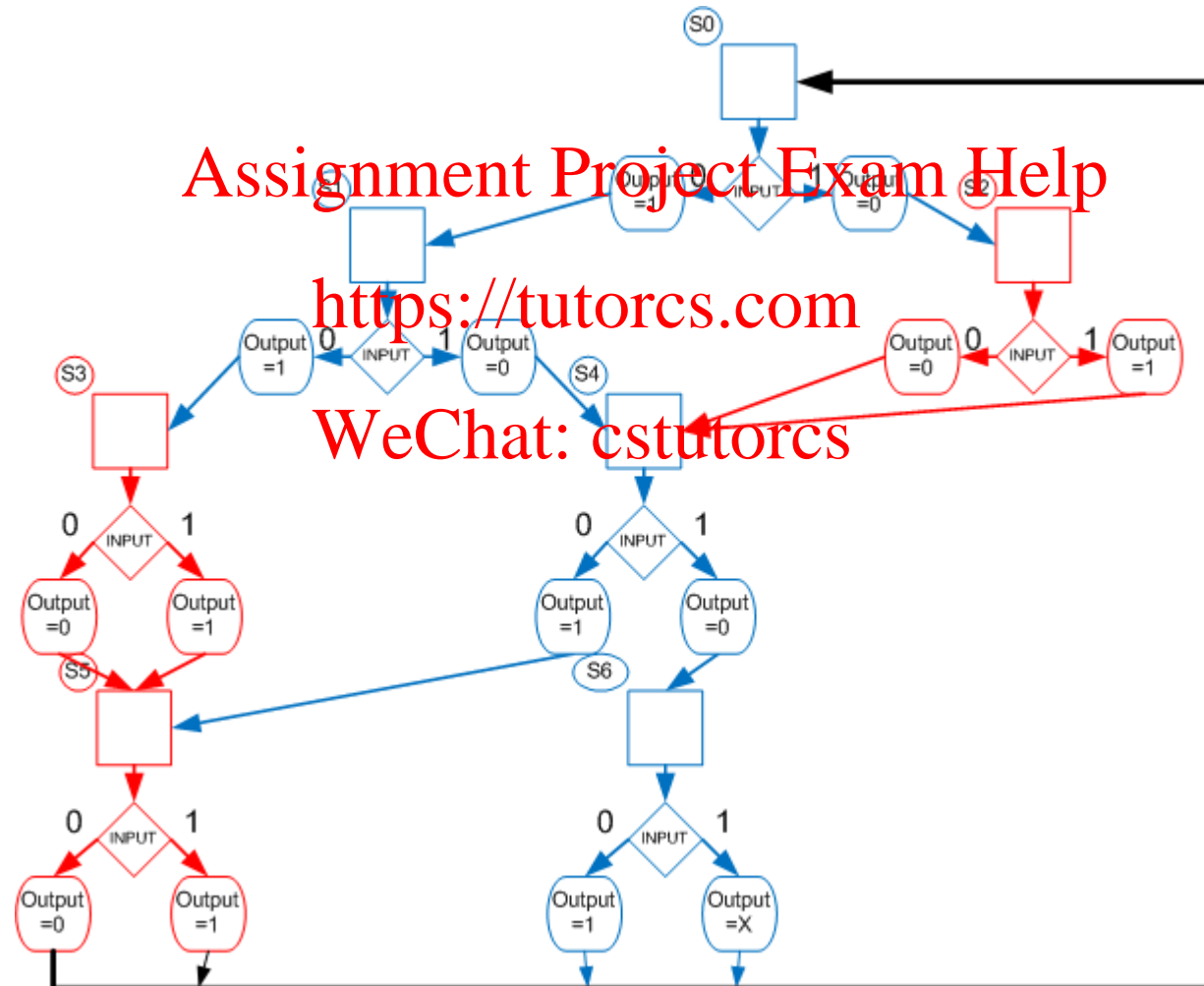

Verilog Model

Edge-sensitive
cyclic behaviour
describes the
state transition.

Level-sensitive
cyclic behaviour
describes the next
state and the
output logic.

```
1 module BCD_to_Excess_3b(B_out, B_in, clk, reset_b);
2     output      B_out;
3     input       B_in, clk, reset_b;
4     parameter   S_0 = 3'b000,
5                 S_1 = 3'b001,
6                 S_2 = 3'b101,
7                 S_3 = 3'b111,
8                 S_4 = 3'b011,
9                 S_5 = 3'b110,
10                S_6 = 3'b010;
11
12     reg [2:0]    state, next_state;
13     reg          B_out;
14
15     always@(posedge clk or negedge reset_b)
16         if (reset_b == 0) state <= S_0; else state <= next_state;
17
18     always @(state or B_in) begin
19         B_out=0;
20         case (state)
21             S_0: if(B_in == 0)begin next_state = S_1; B_out = 1; end
22                 else if (B_in == 1)begin next_state = S_2; end
```

Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs


Nonblocking assignments are used in the edge-sensitive behaviour while **procedural** or **blocked** assignments are used in the level-sensitive behaviours.

Verilog Model

```
17
18 always @(state or B_in) begin
19     B_out=0;
20     case (state)
21         S_0: if(B_in == 0)begin next_state = S_1; B_out = 1; end
22              else if (B_in == 1)begin next_state = S_2; end
23         S_1: if(B_in == 0)begin next_state = S_3; B_out = 1; end
24              else if (B_in == 1)begin next_state = S_4; end
25         S_2: begin next_state = S_4; B_out = B_in; end
26         S_3: begin next_state = S_5; B_out = B_in; end
27         S_4: if(B_in == 0)begin next_state = S_5; B_out = 1; end
28              else if (B_in == 1)begin next_state = S_6; end
29         S_5: begin next_state = S_0; B_out = B_in; end
30         S_6: begin next_state = S_0; B_out = 1; end
31     endcase
32 end
33 endmodule
```


Using don't cares in the state graph
the S_6 output has been designed
to be 1 regardless of its input.

Functional Simulation

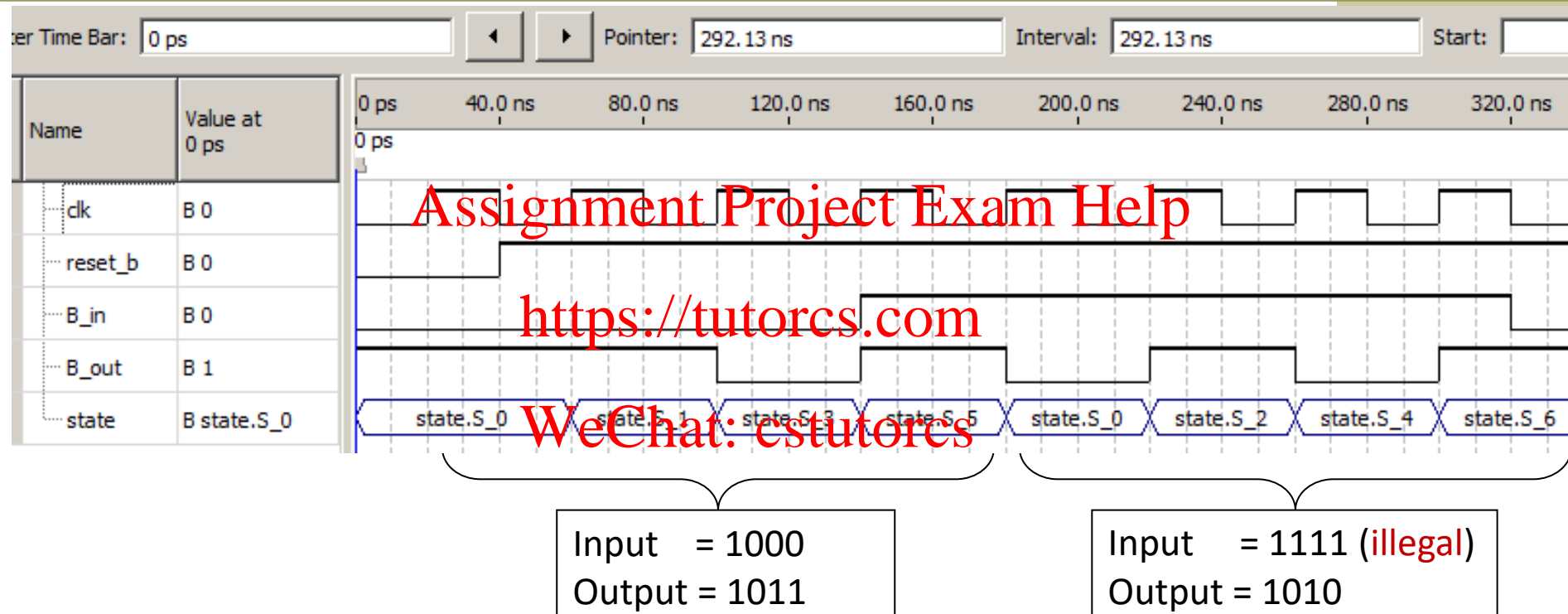


State Machine Editor

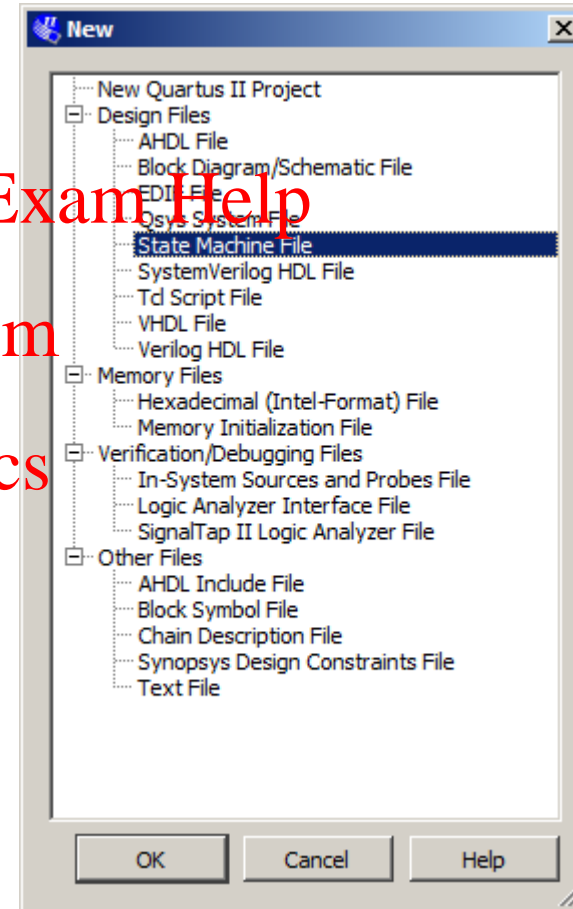- Quartus can generate HDL code from the entered state machine
- Create a new state machine file
- Then use the state machine wizard for entering your design



State Machine Wizard

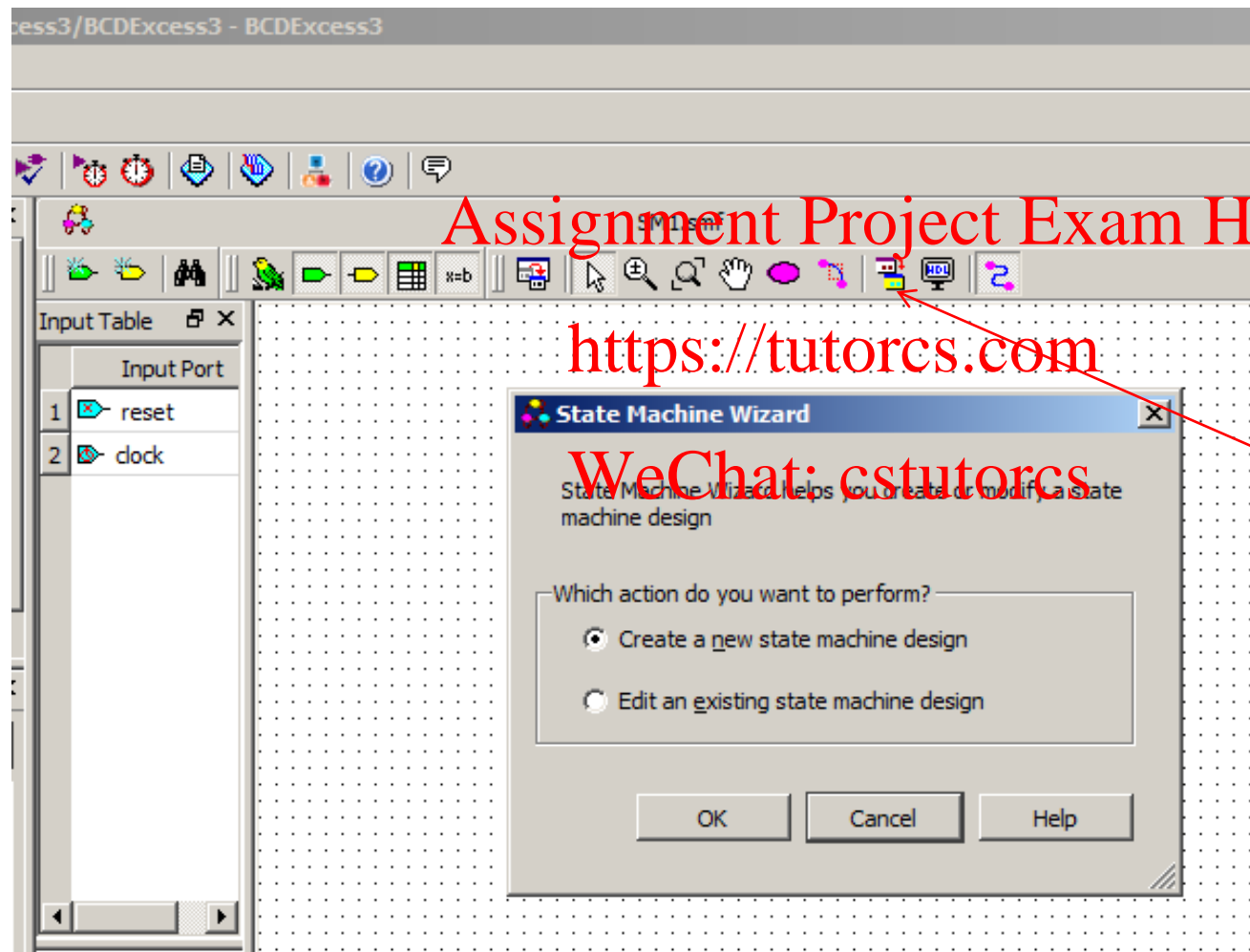


Assignment Project Exam Help

<https://tutorcs.com>


WeChat: cstutorcs

State Machine
Wizard

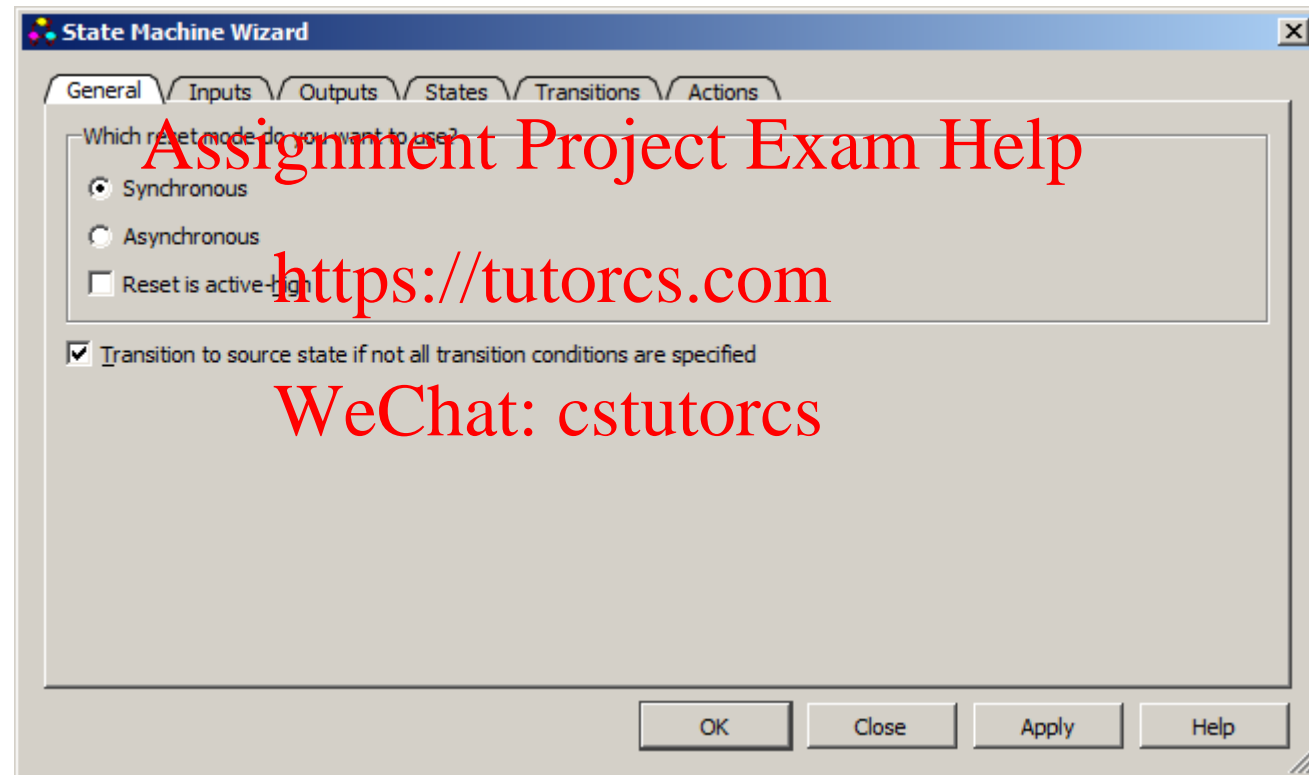
Choose the type of Reset and default states




Define inputs

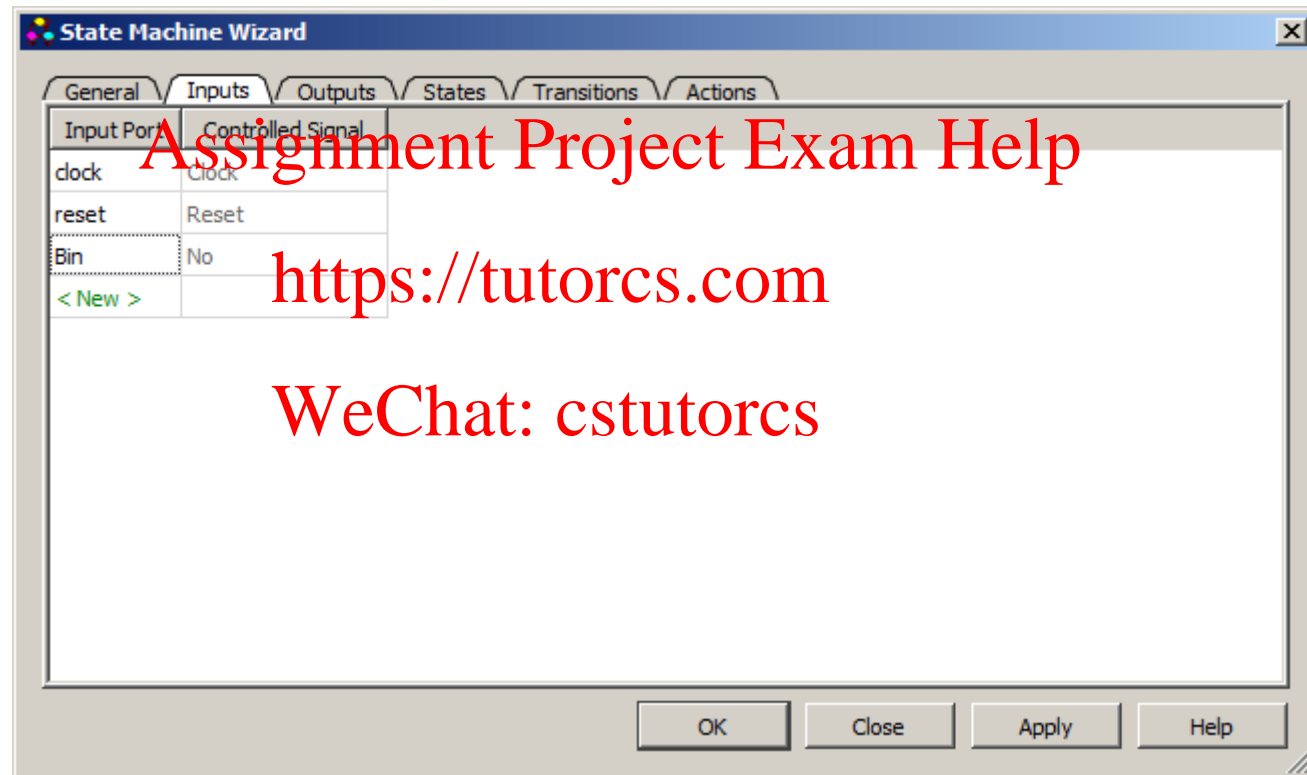


Define outputs

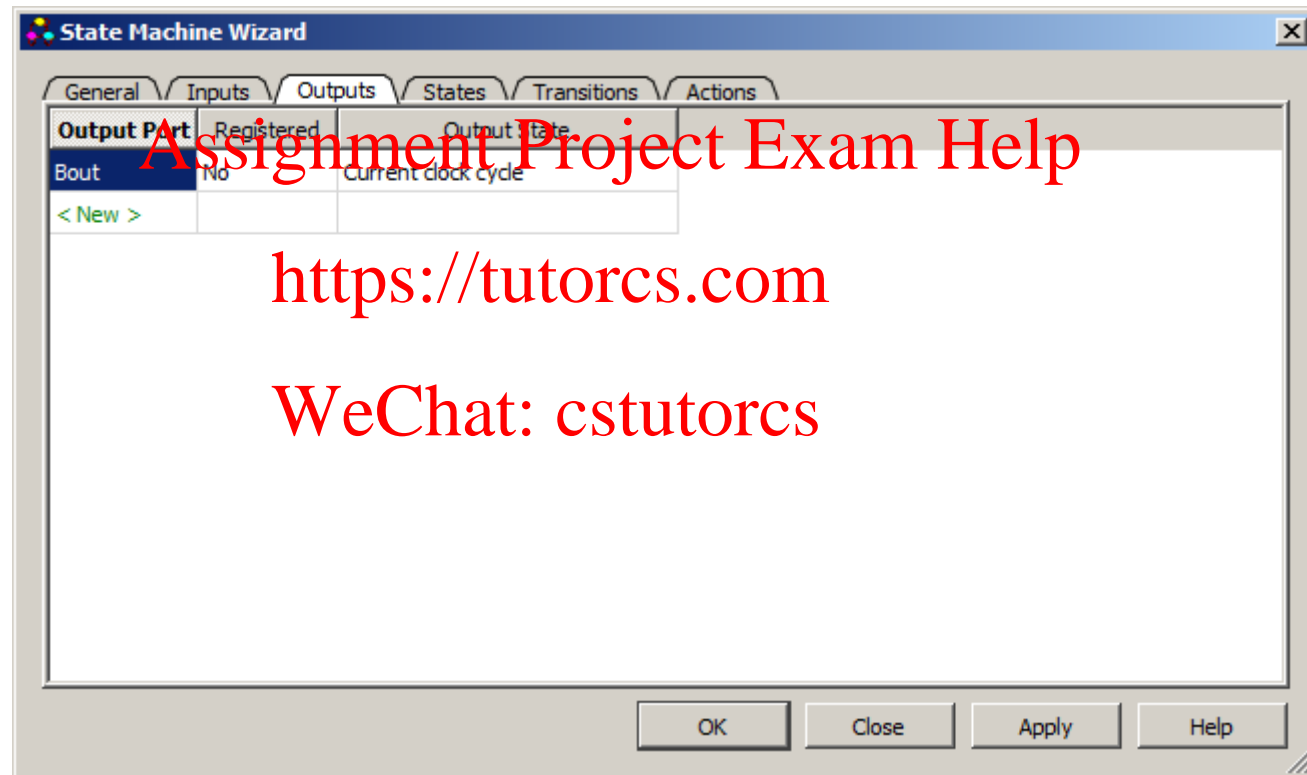


Define the states

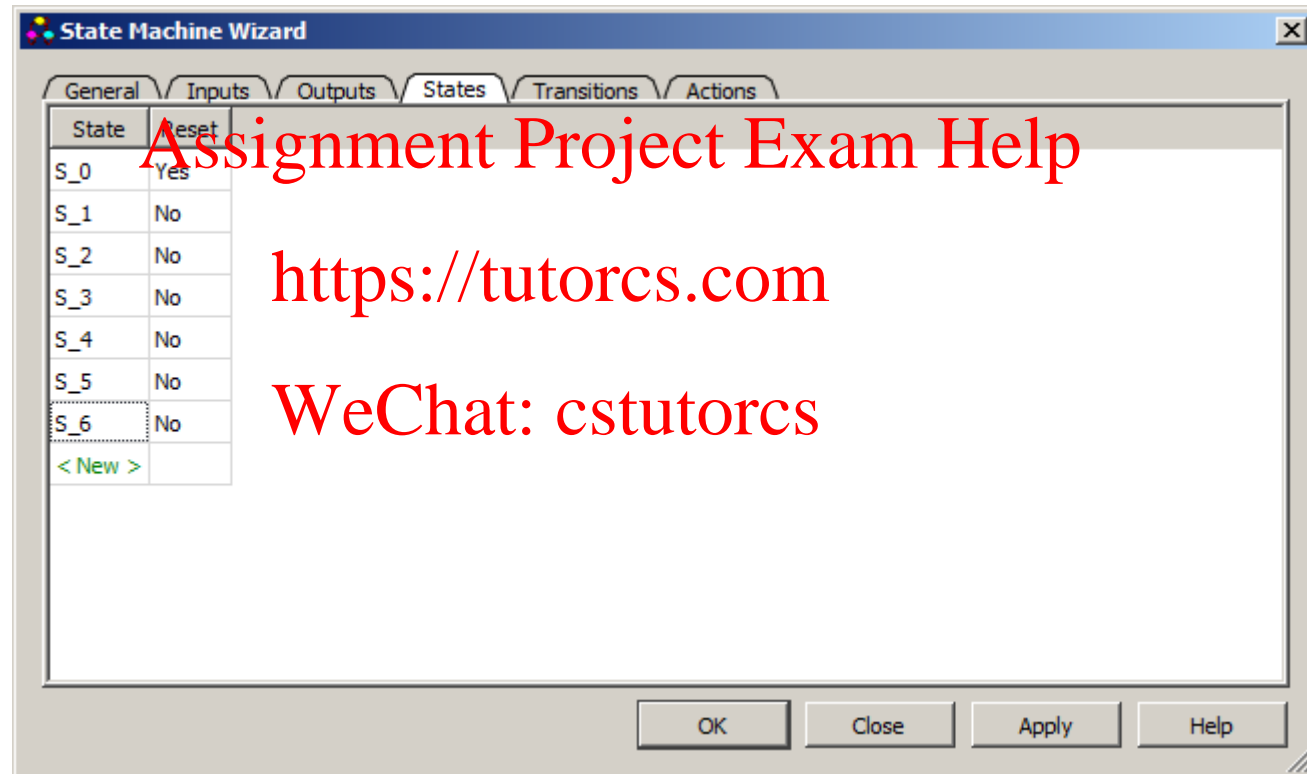


Define the transitions

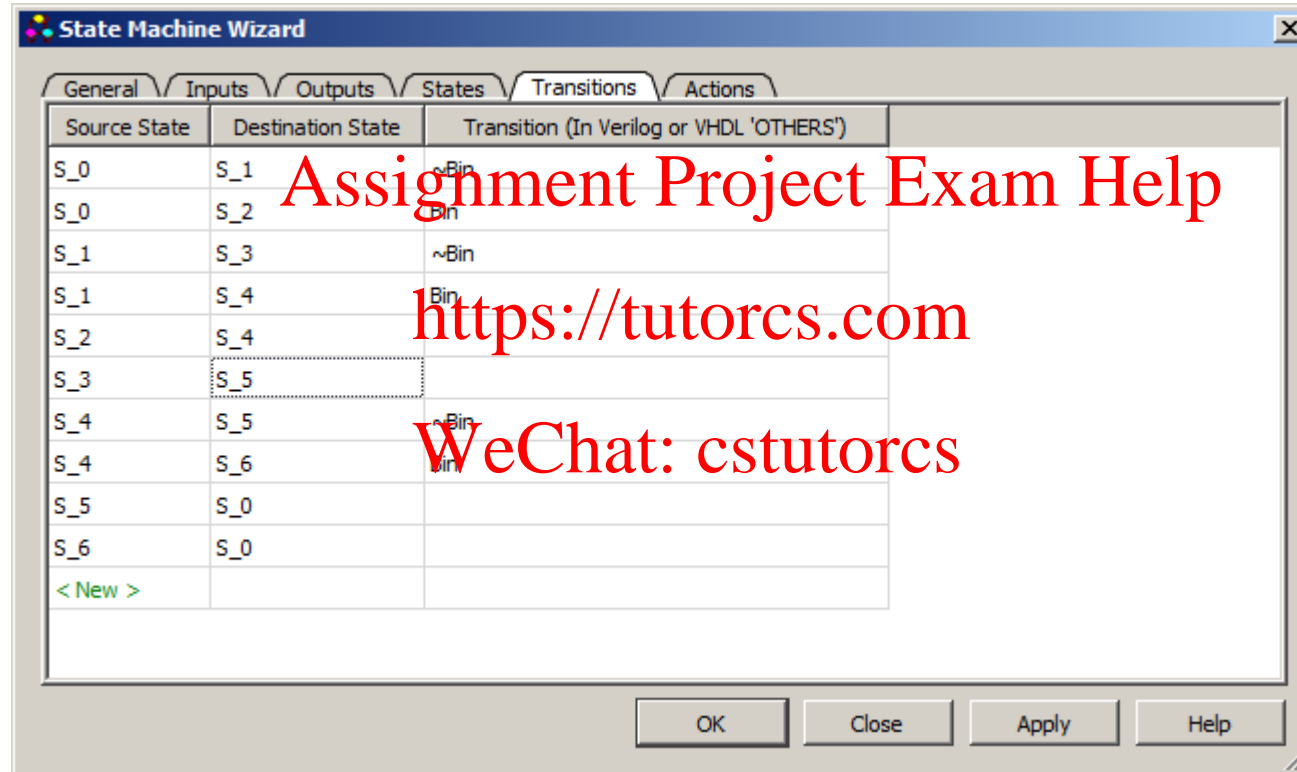


Define the Actions (outputs)

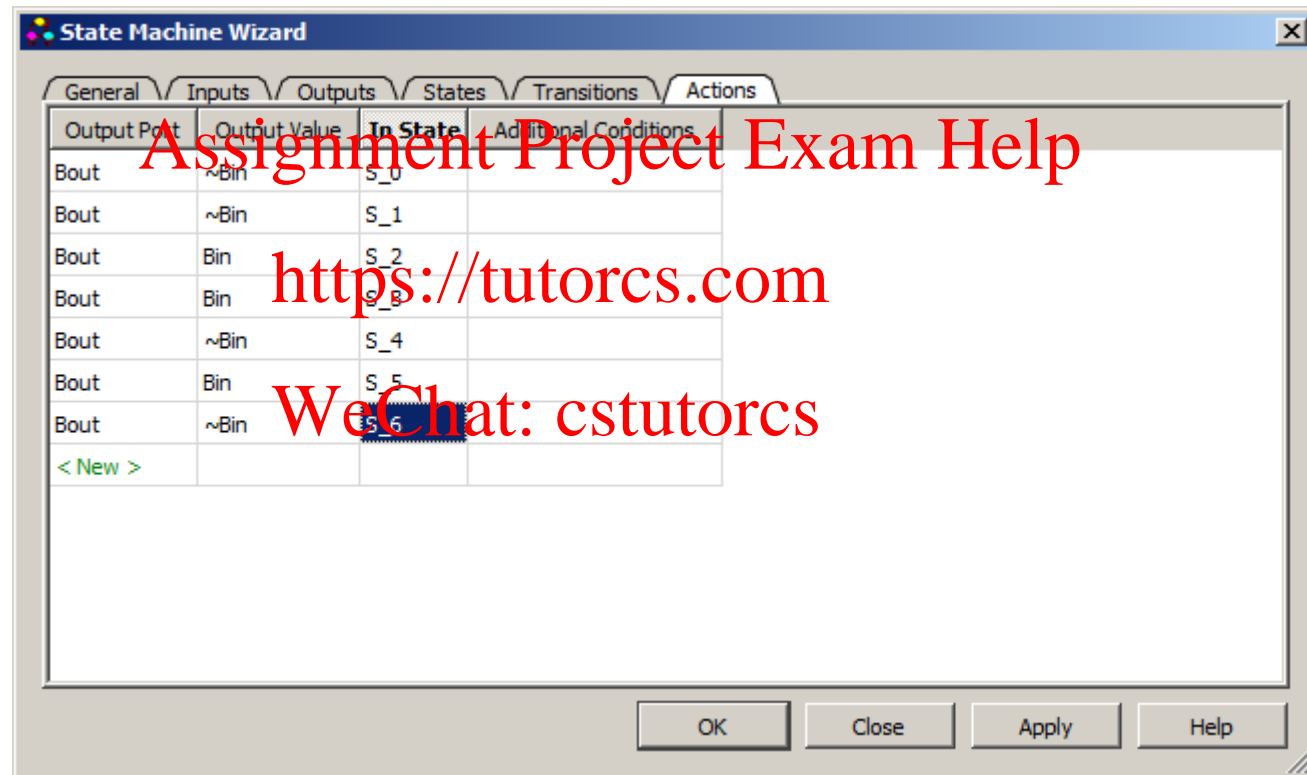

Check the generated state diagram

 

 Save the state machine file and generate a HDL file



Check the generated Verilog file

```
22 module BCDExcess3 (  
23     clock, reset, Bin,  
24     Bout);  
25  
26     input clock;  
27     input reset;  
28     input Bin;  
29     tri0 reset;  
30     tri0 Bin;  
31     output Bout;  
32     reg Bout;  
33     reg [6:0] fstate;  
34     reg [6:0] reg_fstate;  
35     parameter S_0=0,S_1=1,S_2=2,S_3=3,S_4=4,S_5=5,S_6=6;  
36  
37     always @(posedge clock)  
38     begin  
39         if (clock) begin  
40             fstate <= reg_fstate;  
41         end  
42     end  
43  
44     always @(fstate or reset or Bin)  
45     begin  
46         if (~reset) begin  
47             reg_fstate <= S_0;  
48             Bout <= 1'b0;  
49         end  
50         else begin  
51             Bout <= 1'b0;  
52             case (fstate)  
53                 S_0: begin
```

Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs

```

43
44 always @(fstate or reset or Bin)
45 begin
46     if (~reset) begin
47         reg_fstate <= S_0;
48         Bout <= 1'b0;
49     end
50     else begin
51         Bout <= 1'b0;
52         case (fstate)
53             S_0: begin
54                 if (~(Bin))
55                     reg_fstate <= S_1;
56                 else if (Bin)
57                     reg_fstate <= S_2;
58                 // Inserting 'else' block to prevent latch inference
59                 else
60                     reg_fstate <= S_0;
61             end
62             S_1: begin
63                 if (~(Bin))
64                     reg_fstate <= S_0;
65                 else if (Bin)
66                     reg_fstate <= S_4;
67                 // Inserting 'else' block to prevent latch inference
68                 else
69                     reg_fstate <= S_1;
70             end
71             S_2: begin
72                 Bout <= ~(Bin);
73             end
74             S_3: begin
75                 reg_fstate <= S_4;
76             end
77             S_4: begin
78                 Bout <= Bin;
79             end
80             S_5: begin

```

Assignment Project Exam Help

<https://tutorcs.com>

WeChat: estutorcs

```

80      S_3: begin
81          reg_fstate <= S_5;
82
83          Bout <= Bin;
84      end
85      S_4: begin
86          if ~(Bin)
87              reg_fstate <= S_5;
88          else if (Bin)
89              reg_fstate <= S_6;
90          // Inserting 'else' block to prevent latch inference
91          else
92              reg_fstate <= S_4;
93          Bout <= ~(Bin);
94      end
95      S_5: begin
96          reg_fstate <= S_0;
97
98          Bout <= Bin;
99      end
100      S_6: begin
101          reg_fstate <= S_0;
102
103          Bout <= ~(Bin);
104      end
105      default: begin
106          Bout <= 1'bx;
107          $display ("Reach undefined state");
108      end
109  endcase
110  end
111  end
112  endmodule // BCDEExcess3
113
114


```

Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs

Simulate the system

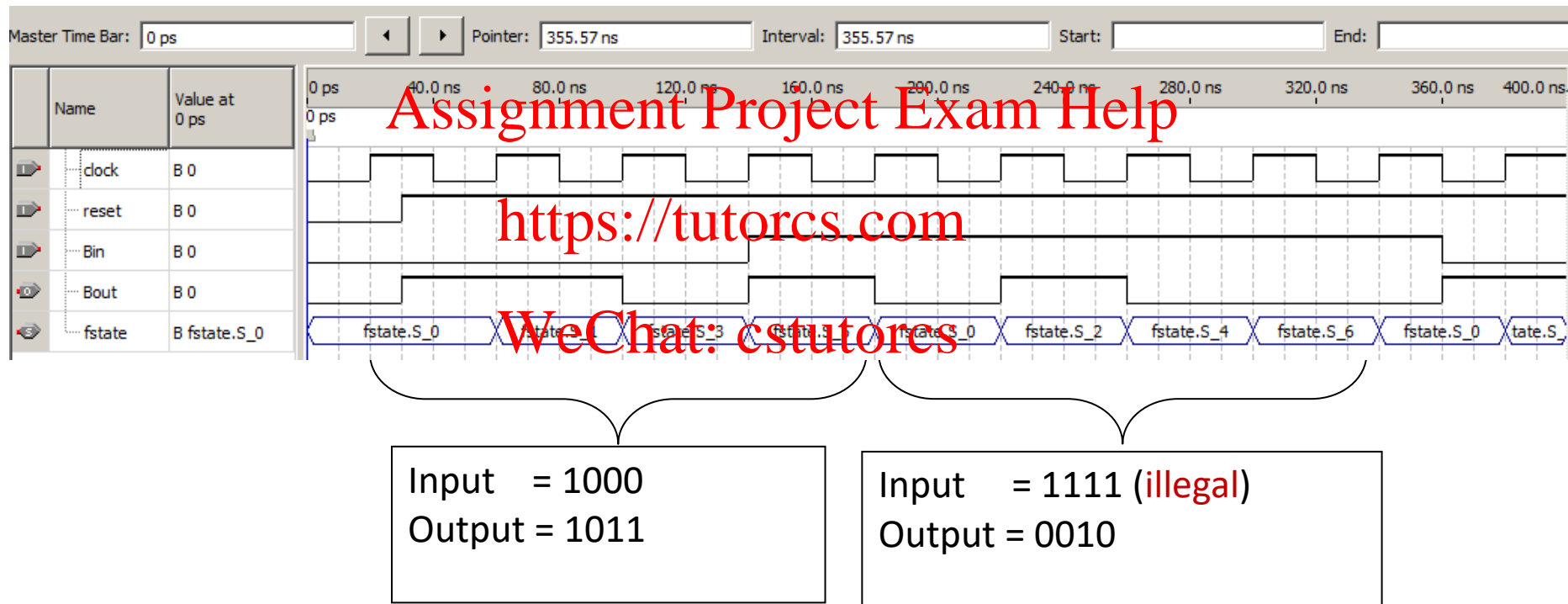

Notice the illegal output is different from the first design.