

# Digital System Design

## ELEC373/473

Assignment Project Exam Help




<https://tutorcs.com>

WeChat: cstutorcs

Algorithmic State Machines (ASMs)  
(Implementation – Classical Method)
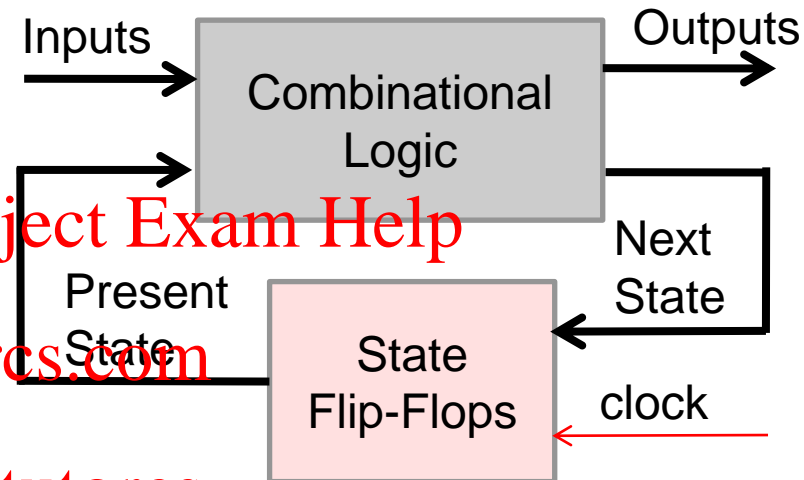
# Controller Structure


- All sequential circuits can be divided into a combinational block and a storage element block implemented by Flip-Flops.




- There are two “classes” of state machines:
  - Moore type outputs are a combinational function of only “Present State” signals.
  - Mealy type outputs are a combinational function of both “Present State” and “Input” signals.
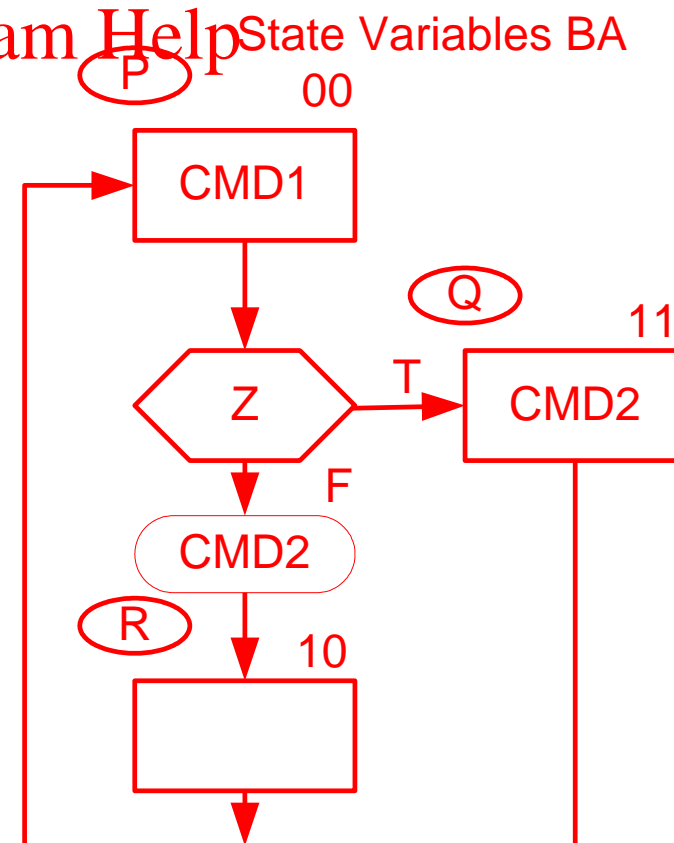
# Traditional Design Implementation


- Use flip-flops as state memory (either D, T, or J-K types)
- There are two ways to represent the present state in flip-flop memory
  1. Assign a unique binary number to each state (**Encoding Method**).
  2. Assign one flip-flop to each state (**One Hot Method**).
- Using the **Encoding method**, two state variables are required for encoding 3 states.
- The state assignment is arbitrary.
- Given the present state we need to compute the new state code to load into the state flip flops.



# Process Model

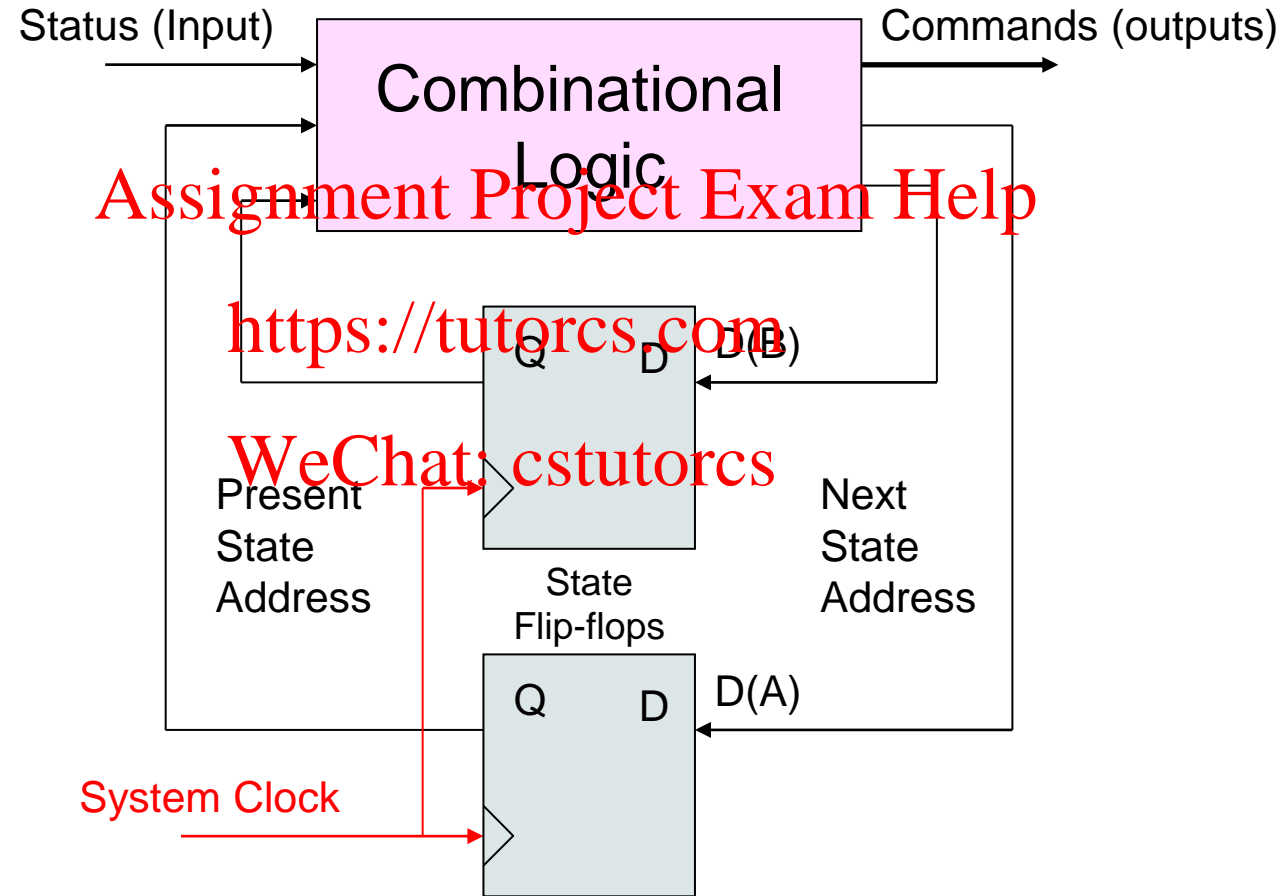

# State Transition Table

 

CMD1 =

CMD2 =

D(B) =

D(A) =


Present State	Input	Next State	Outputs	
(state) BA	Z	D(B)D(A)	CMD1	CMD2
(P) 00				
(Q) 11				
(R) 10				
(?) 01				

BA \ Z	0	1
00		
01		
11		
10		

BA \ Z	0	1
00		
01		
11		
10		


BA \ Z	0	1
00		
01		
11		
10		

# State Transition Table

 


Present State	Input	Next State	Outputs	
(state)BA	Z	D(B)D(A)	CMD1	CMD2
(P) 00	0	-	-	-
(P) 00	1	-	-	-
(Q) 11	0	-	-	-
(R) 10	-	-	-	-
(?) 01	-	-	-	-

# State Transition Table

 

Present State	Input	Next State	Outputs	
(state)BA	Z	D(B)D(A)	CMD1	CMD2
(P) 00	0	(R) 10		
(P) 00	1			
(Q) 11	0			
(R) 10	-			
(?) 01	-	-	-	-


# State Transition Table

 

Present State	Input	Next State	Outputs	
(state)BA	Z	D(B)D(A)	CMD1	CMD2
(P) 00	0	(R) 10	1	-
(P) 00	1	-	-	-
(Q) 11	-	-	-	-
(R) 10	-	-	-	-
(?) 01	-	-	-	-



# State Transition Table

 


Present State	Input	Next State	Outputs	
(state)BA	Z	D(B)D(A)	CMD1	CMD2
(P) 00	0	(R) 10	1	1
(P) 00	1	-	-	-
(Q) 11	-	-	-	-
(R) 10	-	-	-	-
(?) 01	-	-	-	-

Assignment Project Exam Help

<https://tutorcs.com>


WeChat: cstutorcs

# State Transition Table

 


Present State	Input	Next State	Outputs	
(state)BA	Z	D(B)D(A)	CMD1	CMD2
(P) 00	0	(R) 10	1	1
(P) 00	1	(Q) 11		
(Q) 11	-	-	-	-
(R) 10	-	-	-	-
(?) 01	-	-	-	-

# State Transition Table

 


Present State	Input	Next State	Outputs	
(state) BA	Z	D(B)D(A)	CMD1	CMD2
(P) 00	0	(R) 10	1	1
(P) 00	1	(Q) 11	1	
(Q) 11	-	-	-	-
(R) 10	-	-	-	-
(?) 01	-	-	-	-

# State Transition Table

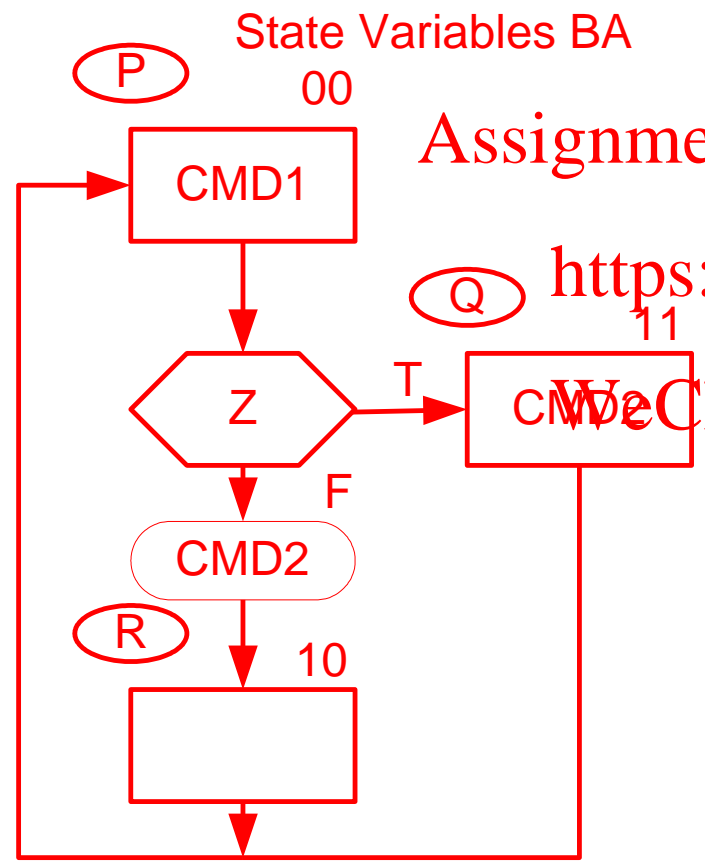


Present State	Input	Next State	Outputs	
(state)BA	Z	D(B)D(A)	CMD1	CMD2
(P) 00	0	(R) 10	1	1
(P) 00	1	(Q) 11	1	0
(Q) 11	-	-	-	-
(R) 10	-	-	-	-
(?) 01	-	-	-	-

# State Transition Table

 


Present State	Input	Next State	Outputs	
(state)BA	Z	D(B)D(A)	CMD1	CMD2
(P) 00	0	(R) 10	1	1
(P) 00	1	(Q) 11	1	0
(Q) 11	-	(P) 00	-	-
(R) 10	-	-	-	-
(?) 01	-	-	-	-

# State Transition Table

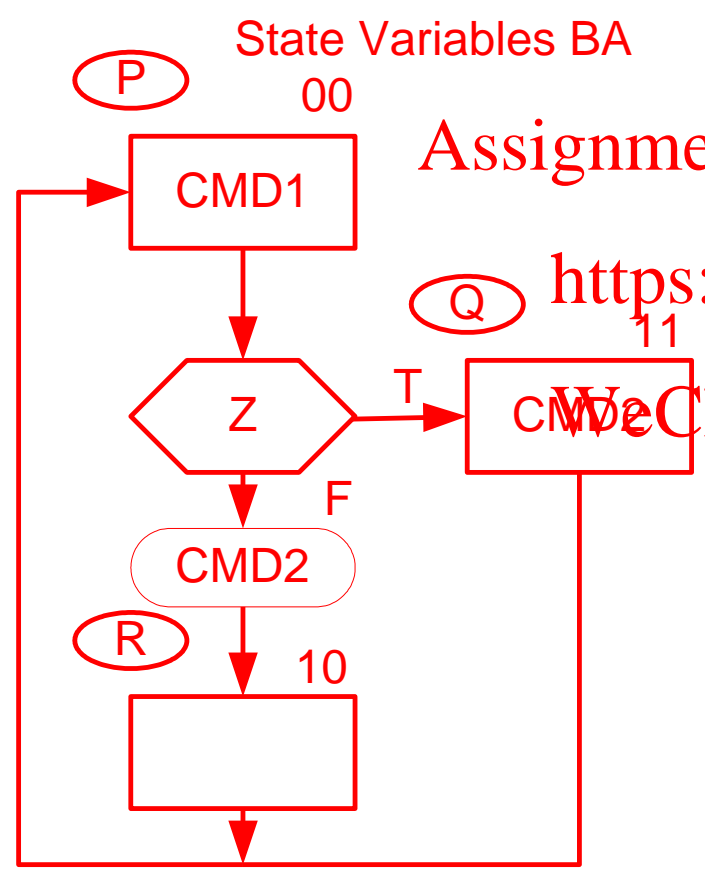


Present State	Input	Next State	Outputs	
(state)BA	Z	D(B)D(A)	CMD1	CMD2
(P) 00	0	(R) 10	1	1
(P) 00	1	(Q) 11	1	0
(Q) 11	-	(P) 00	0	-
(R) 10	-	-	-	-
(?) 01	-	-	-	-

# State Transition Table

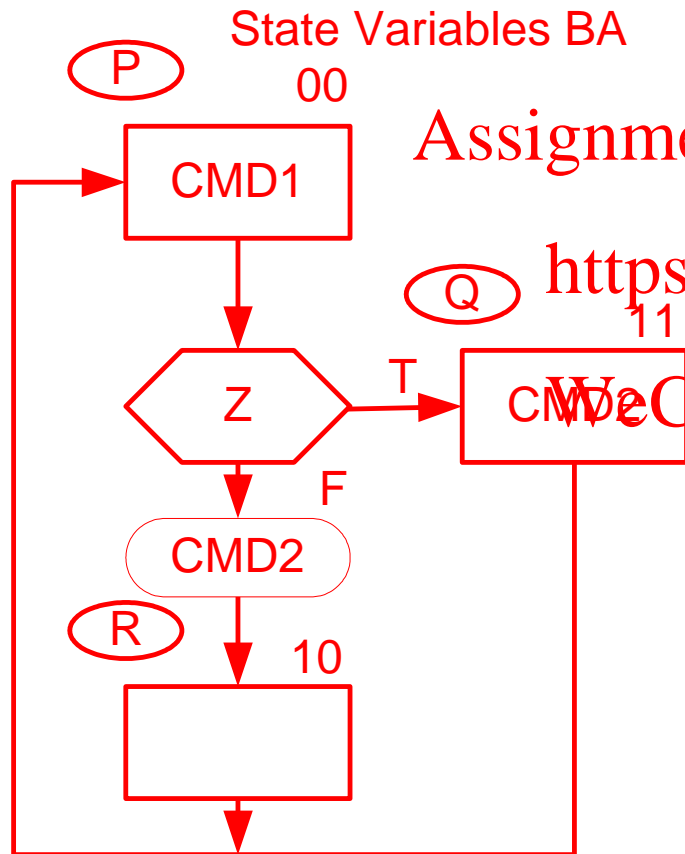

Present State	Input	Next State	Outputs	
(state)BA	Z	D(B)D(A)	CMD1	CMD2
(P) 00	0	(R) 10	1	1
(P) 00	1	(Q) 11	1	0
(Q) 11	0	(P) 00	0	1
(R) 10	-	-	-	-
(?) 01	-	-	-	-


# State Transition Table

 

Present State	Input	Next State	Outputs	
(state)BA	Z	D(B)D(A)	CMD1	CMD2
(P) 00	0	(R) 10	1	1
(P) 00	1	(Q) 11	1	0
(Q) 11	0	(P) 00	0	1
(R) 10	-	(P) 00	-	-
(?) 01	-	-	-	-




# State Transition Table

 


Present State	Input	Next State	Outputs	
(state)BA	Z	D(B)D(A)	CMD1	CMD2
(F) 00	0	(R) 00	1	1
(P) 00	1	(Q) 11	1	0
(Q) 11	0	(P) 00	0	1
(R) 10	-	(P) 00	0	
(?) 01	-	-	-	-

# State Transition Table

 

Present State	Input	Next State	Outputs	
(state)BA	Z	D(B)D(A)	CMD1	CMD2
(P) 00	0	(R) 10	1	1
(P) 00	1	(Q) 11	1	0
(Q) 11	0	(P) 00	0	1
(R) 10	-	(P) 00	0	0
(?) 01	-	-	-	-

# State Transition Table

 

Present State	Input	Next State	Outputs	
(state)BA	Z	D(B)D(A)	CMD1	CMD2
(P) 00	0	(R) 10	1	1
(P) 00	1	(Q) 11	1	0
(Q) 11	0	(P) 00	0	1
(R) 10	-	(P) 00	0	0
(?) 01	-	-	-	-

BA \ Z	0	1
00		
01		
11		
10		

BA \ Z	0	1
00		
01		
11		
10		

BA \ Z	0	1
00		
01		
11		
10		


CMD1 =

CMD2 =

D(B) =

D(A) =

# State Transition Table

 

Present State	Input	Next State	Outputs	
(state) BA	Z	D(B)D(A)	CMD1	CMD2
(P) 00	0	(R) 10	1	1
(P) 00	1	(Q) 11	1	0
(Q) 11	0	(P) 00	0	1
(R) 10	-	(P) 00	0	0
(?) 01	-	-	-	-

BA \ Z	0	1
00		
01		
11		
10		

CMD2 =

BA \ Z	0	1
00		
01		
11		
10		


D(B) =

BA \ Z	0	1
00	0	
01		
11		
10		

D(A) =

CMD1 =

# State Transition Table

 

Present State	Input	Next State	Outputs	
(state)BA	Z	D(B)D(A)	CMD1	CMD2
(P) 00	0	(R) 10	1	1
(P) 00	1	(Q) 11	1	0
(Q) 11	0	(P) 00	0	1
(R) 10	-	(P) 00	0	0
(?) 01	-	-	-	-

BA \ Z	0	1
00		
01		
11		
10		

BA \ Z	0	1
00		
01		
11		
10		

BA \ Z	0	1
00	0	1
01		
11		
10		


CMD1 =

CMD2 =

D(B) =

D(A) =

# State Transition Table

 

Present State	Input	Next State	Outputs	
(state)BA	Z	D(B)D(A)	CMD1	CMD2
(P) 00	0	(R) 10	1	1
(P) 00	1	(Q) 11	1	0
(Q) 11	0	(P) 00	0	1
(R) 10	-	(P) 00	0	0
(?) 01	-	-	-	-

z	0	1
BA		
00		
01		
11		
10		

z	0	1
BA		
00		
01		
11		
10		

z	0	1
BA		
00	0	1
01	X	X
11		
10		


CMD1 =

CMD2 =

D(B) =

D(A) =

# State Transition Table

 

Present State	Input	Next State	Outputs	
(state) BA	Z	D(B)D(A)	CMD1	CMD2
(P) 00	0	(R) 10	1	1
(P) 00	1	(Q) 11	1	0
(Q) 11	-	(P) 00	0	1
(R) 10	-	(P) 00	0	0
(?) 01	-	-	-	-

z BA	0	1
00		
01		
11		
10		

CMD2 =

z BA	0	1
00		
01		
11		
10		


D(B) =

z BA	0	1
00	0	1
01	X	X
11	0	0
10	0	0

D(A) =

CMD1 =

# State Transition Table

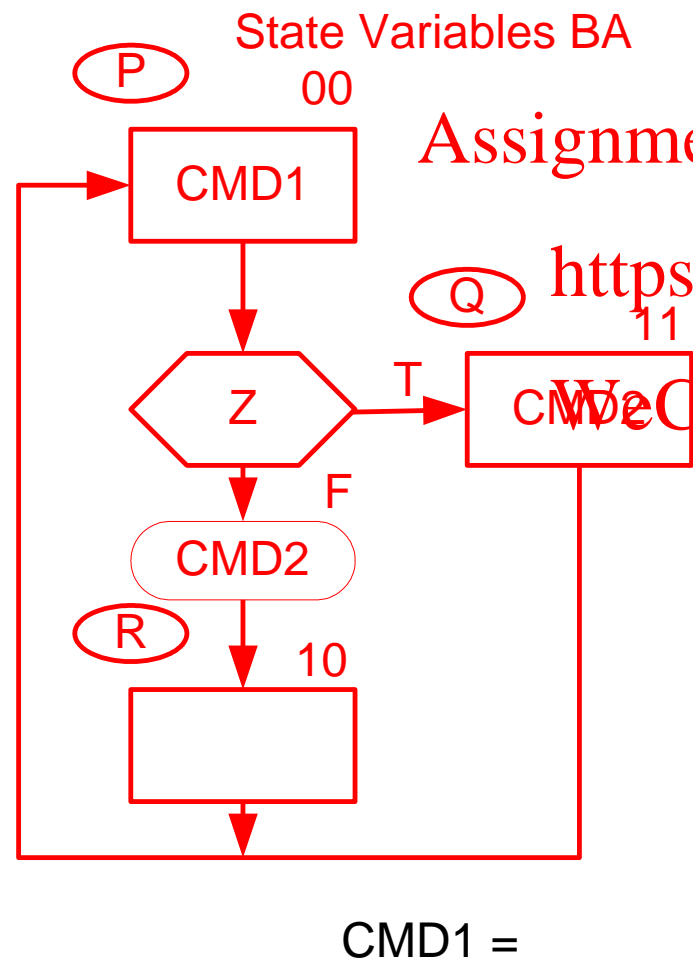

Present State	Input	Next State	Outputs	
(state)BA	Z	D(B)D(A)	CMD1	CMD2
(P) 00	0	(R) 10	1	1
(P) 00	1	(Q) 11	1	0
(Q) 11	-	(P) 00	0	1
(R) 10	-	(P) 00	0	0
(?) 01	-	-	-	-

z	0	1
BA		
00		
01		
11		
10		

CMD2 =

z	0	1
BA		
00		
01		
11		
10		


D(B) =

z	0	1
BA		
00	0	1
01	X	X
11	0	0
10	0	0

D(A) =



# State Transition Table

 

CMD1 =

CMD2 =

D(B) =

D(A) = B'Z


Present State	Input	Next State	Outputs	
(state)BA	Z	D(B)D(A)	CMD1	CMD2
(P) 00	0	(R) 10	1	1
(P) 00	1	(Q) 11	1	0
(Q) 11	0	(P) 00	0	1
(R) 10	-	(P) 00	0	0
(?) 01	-	-	-	-

z BA	0	1
00		
01		
11		
10		

z BA	0	1
00		
01		
11		
10		

z BA	0	1
00	0	1
01	X	X
11	0	0
10	0	0

# State Transition Table

 

CMD1 =

CMD2 =

D(B) =

D(A) = B'Z


Present State	Input	Next State	Outputs	
(state)BA	Z	D(B)D(A)	CMD1	CMD2
(P) 00	0	(R) 10	1	1
(P) 00	1	(Q) 11	1	0
(Q) 11	-	(P) 00	0	1
(R) 10	-	(P) 00	0	0
(?) 01	-	-	-	-

z BA	0	1
00		
01		
11		
10		

z BA	0	1
00	1	1
01		
11		
10		

z BA	0	1
00	0	1
01	X	X
11	0	0
10	0	0

# State Transition Table

 

CMD1 =

CMD2 =

D(B) =

D(A) = B'Z


Present State	Input	Next State	Outputs	
(state) BA	Z	D(B)D(A)	CMD1	CMD2
(P) 00	0	(R) 10	1	1
(P) 00	1	(Q) 11	1	0
(Q) 11	-	(P) 00	0	1
(R) 10	-	(P) 00	0	0
(?) 01	-	-	-	-

z BA	0	1
00		
01		
11		
10		

z BA	0	1
00	1	1
01	X	X
11		
10		

z BA	0	1
00	0	1
01	X	X
11	0	0
10	0	0

# State Transition Table

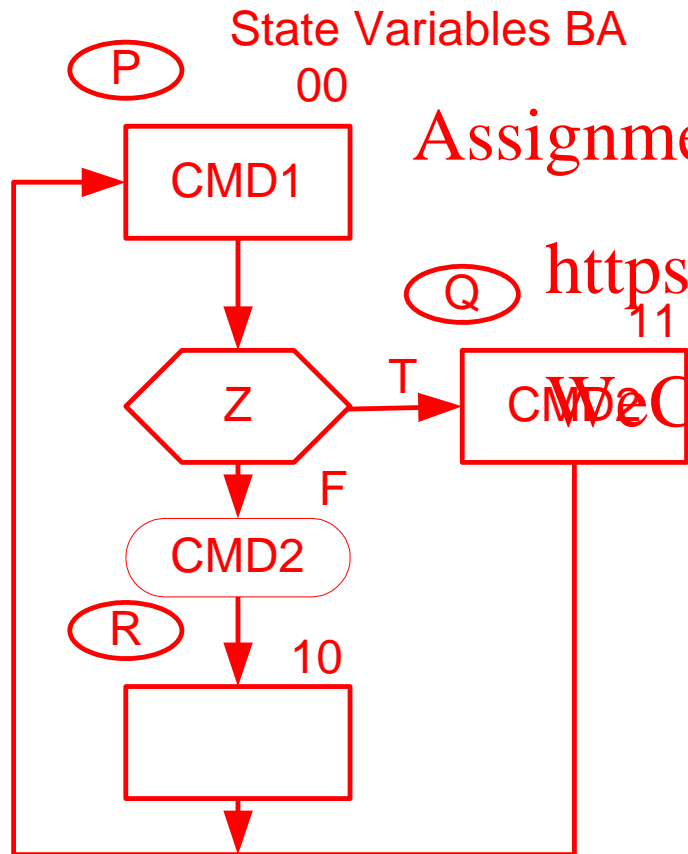

CMD1 =

CMD2 =

D(B) =

D(A) = B'Z


Present State	Input	Next State	Outputs	
(state) BA	Z	D(B)D(A)	CMD1	CMD2
(P) 00	0	(R) 10	1	1
(P) 00	1	(Q) 11	1	0
(Q) 11	-	(P) 00	0	1
(R) 10	-	(P) 00	0	0
(?) 01	-	-	-	-

BA \ Z	0	1
00		
01		
11		
10		

BA \ Z	0	1
00	1	1
01	X	X
11	0	0
10	0	0

BA \ Z	0	1
00	0	1
01	X	X
11	0	0
10	0	0

# State Transition Table

 

CMD1 =

CMD2 =

z \ BA	0	1
00		
01		
11		
10		

z \ BA	0	1
00	1	1
01	X	X
11	0	0
10	0	0


D(B) =

z \ BA	0	1
00	0	1
01	X	X
11	0	0
10	0	0

D(A) = B'Z

Present State	Input	Next State	Outputs	
(state) BA	Z	D(B)D(A)	CMD1	CMD2
(P) 00	0	(R) 10	1	1
(P) 00	1	(Q) 11	1	0
(Q) 11	0	(P) 00	0	1
(R) 10	-	(P) 00	0	0
(?) 01	-	-	-	-

# State Transition Table

 

CMD1 =

Present State	Input	Next State	Outputs	
(state) BA	Z	D(B)D(A)	CMD1	CMD2
(P) 00	0	(R) 10	1	1
(P) 00	1	(Q) 11	1	0
(Q) 11	-	(P) 00	0	1
(R) 10	-	(P) 00	0	0
(?) 01	-	-	-	-

BA \ Z	Z	
	0	1
00		
01		
11		
10		

CMD2 =


BA \ Z	Z	
	0	1
00	1	1
01	X	X
11	0	0
10	0	0

$D(B) = B'$

BA \ Z	Z	
	0	1
00	0	1
01	X	X
11	0	0
10	0	0

$D(A) = B'Z$

# State Transition Table

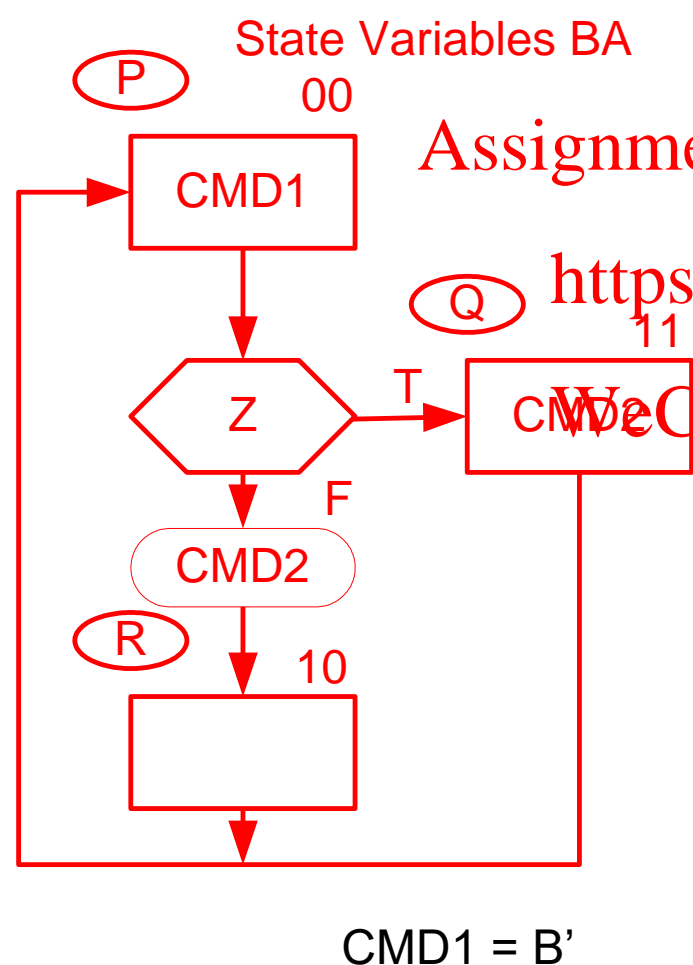

Present State	Input	Next State	Outputs	
(state)BA	Z	D(B)D(A)	CMD1	CMD2
(P) 00	0	(R) 10	1	1
(P) 00	1	(Q) 11	1	0
(Q) 11	-	(P) 00	0	1
(R) 10	-	(P) 00	0	0
(?) 01	-	-	-	-

z	0	1
BA		
00		
01		
11		
10		

CMD2 =


z	0	1
BA		
00	1	1
01	X	X
11	0	0
10	0	0

D(B) = B'

z	0	1
BA		
00	0	1
01	X	X
11	0	0
10	0	0

D(A) = B'Z

# State Transition Table

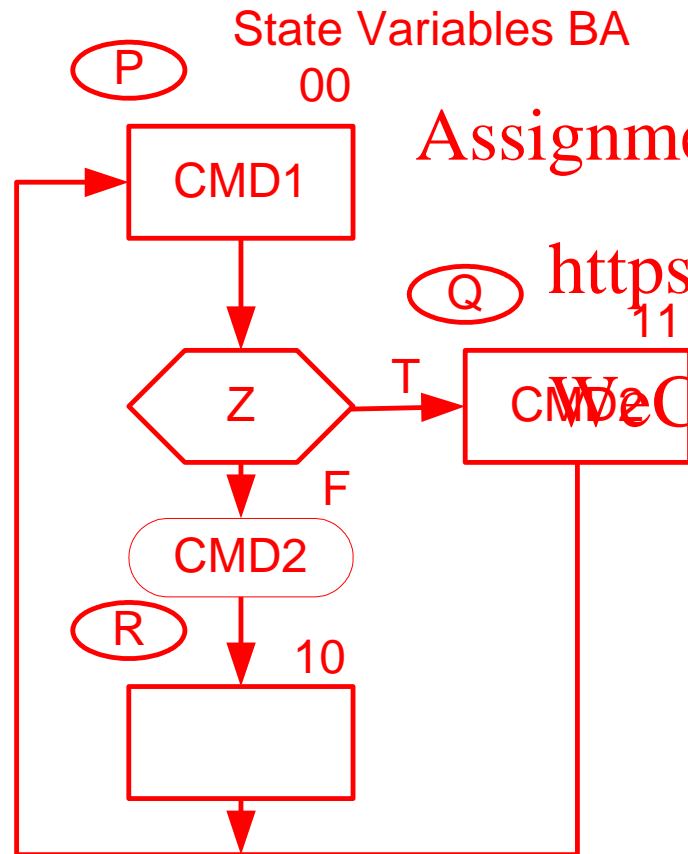

CMD1 = B'

Present State	Input	Next State	Outputs	
(state) BA	Z	D(B)D(A)	CMD1	CMD2
(P) 00	0	(R) 10	1	1
(P) 00	1	(Q) 11	1	0
(Q) 11	-	(P) 00	0	1
(R) 10	-	(P) 00	0	0
(?) 01	-	-	-	-

z	0	1
BA		
00	1	
01		
11		
10		

CMD2 =

z	0	1
BA		
00	1	1
01	X	X
11	0	0
10	0	0


D(B) = B'

z	0	1
BA		
00	0	1
01	X	X
11	0	0
10	0	0

D(A) = B'Z



# State Transition Table

 

CMD1 = B'

Present State	Input	Next State	Outputs	
(state) BA	Z	D(B)D(A)	CMD1	CMD2
(P) 00	0	(R) 10	1	1
(P) 00	1	(Q) 11	1	0
(Q) 11	-	(P) 00	0	1
(R) 10	-	(P) 00	0	0
(?) 01	-	-	-	-

z BA	0	1
00	1	0
01		
11		
10		

CMD2 =


z BA	0	1
00	1	1
01	X	X
11	0	0
10	0	0

D(B) = B'

z BA	0	1
00	0	1
01	X	X
11	0	0
10	0	0

D(A) = B'Z

# State Transition Table

 

Present State	Input	Next State	Outputs	
(state)BA	Z	D(B)D(A)	CMD1	CMD2
(P) 00	0	(R) 10	1	1
(P) 00	1	(Q) 11	1	0
(Q) 11	-	(P) 00	0	1
(R) 10	-	(P) 00	0	0
(?) 01	-	-	-	-

	Z	0	1
BA			
00		1	0
01		X	X
11			
10			

CMD2 =


	Z	0	1
BA			
00		1	1
01		X	X
11		0	0
10		0	0

D(B) = B'

	Z	0	1
BA			
00		0	1
01		X	X
11		0	0
10		0	0

D(A) = B'Z

# State Transition Table

 

CMD1 = B'

Present State	Input	Next State	Outputs	
(state) BA	Z	D(B)D(A)	CMD1	CMD2
(P) 00	0	(R) 10	1	1
(P) 00	1	(Q) 11	1	0
(Q) 11	-	(P) 00	0	1
(R) 10	-	(P) 00	0	0
(?) 01	-	-	-	-

BA \ Z	Z	
	0	1
00	1	0
01	X	X
11	1	1
10		

CMD2 =


BA \ Z	Z	
	0	1
00	1	1
01	X	X
11	0	0
10	0	0

D(B) = B'

BA \ Z	Z	
	0	1
00	0	1
01	X	X
11	0	0
10	0	0

D(A) = B'Z

# State Transition Table

 

CMD1 = B'

Present State	Input	Next State	Outputs	
(state) BA	Z	D(B)D(A)	CMD1	CMD2
(P) 00	0	(R) 10	1	1
(P) 00	1	(Q) 11	1	0
(Q) 11	-	(P) 00	0	1
(R) 10	-	(P) 00	0	0
(?) 01	-	-	-	-

BA \ Z	Z	
	0	1
00	1	0
01	X	X
11	1	1
10	0	0

CMD2 =


BA \ Z	Z	
	0	1
00	1	1
01	X	X
11	0	0
10	0	0

D(B) = B'

BA \ Z	Z	
	0	1
00	0	1
01	X	X
11	0	0
10	0	0

D(A) = B'Z

# State Transition Table

 

Present State	Input	Next State	Outputs	
(state)BA	Z	D(B)D(A)	CMD1	CMD2
(P) 00	0	(R) 10	1	1
(P) 00	1	(Q) 11	1	0
(Q) 11	-	(P) 00	0	1
(R) 10	-	(P) 00	0	0
(?) 01	-	-	-	-

z	0	1
BA		
00	1	0
01	X	X
11	1	1
10	0	0

CMD2 =


z	0	1
BA		
00	1	1
01	X	X
11	0	0
10	0	0

D(B) = B'

z	0	1
BA		
00	0	1
01	X	X
11	0	0
10	0	0

D(A) = B'Z

# State Transition Table

 

CMD1 = B'

Present State	Input	Next State	Outputs	
(state) BA	Z	D(B)D(A)	CMD1	CMD2
(P) 00	0	(R) 10	1	1
(P) 00	1	(Q) 11	1	0
(Q) 11	-	(P) 00	0	1
(R) 10	-	(P) 00	0	0
(?) 01	-	-	-	-

z	0	1
BA		
00	1	0
01	X	X
11	1	1
10	0	0

CMD2 =


z	0	1
BA		
00	1	1
01	X	X
11	0	0
10	0	0

D(B) = B'

z	0	1
BA		
00	0	1
01	X	X
11	0	0
10	0	0

D(A) = B'Z

# State Transition Table

 

$$\text{CMD1} = B'$$

Present State	Input	Next State	Outputs	
(state) BA	Z	D(B)D(A)	CMD1	CMD2
(P) 00	0	(R) 10	1	1
(P) 00	1	(Q) 11	1	0
(Q) 11	-	(P) 00	0	1
(R) 10	-	(P) 00	0	0
(?) 01	-	-	-	-

z	0	1
BA		
00	1	0
01	X	X
11	1	1
10	0	0

$$\text{CMD2} = A + B'Z$$

z	0	1
BA		
00	1	1
01	X	X
11	0	0
10	0	0

$$D(B) = B'$$

z	0	1
BA		
00	0	1
01	X	X
11	0	0
10	0	0

$$D(A) = B'Z$$

# Check for unused states

- In the last example we didn't design for the unused state BA=01
- It is good practice to check what would happen if the system booted or "jumped" into the unused state
- As  $D(A) = B'Z$ 
  - If  $Z = 1$  then  $D(A) = 1$
  - If  $Z = 0$  then  $D(A) = 0$
- As  $D(B) = B'$ 
  - $D(B) = 1$
- Therefore the next state(s) are
  - If  $Z = 1$  BA=11 (State Q)
  - If  $Z = 0$  BA=10 (State R)
- Hence even if the system enters the unused state (BA = 01) it will exit it.


Assignment Project Exam Help

<https://tutorcs.com>


WeChat: cstutorcs



# ASM Implementation

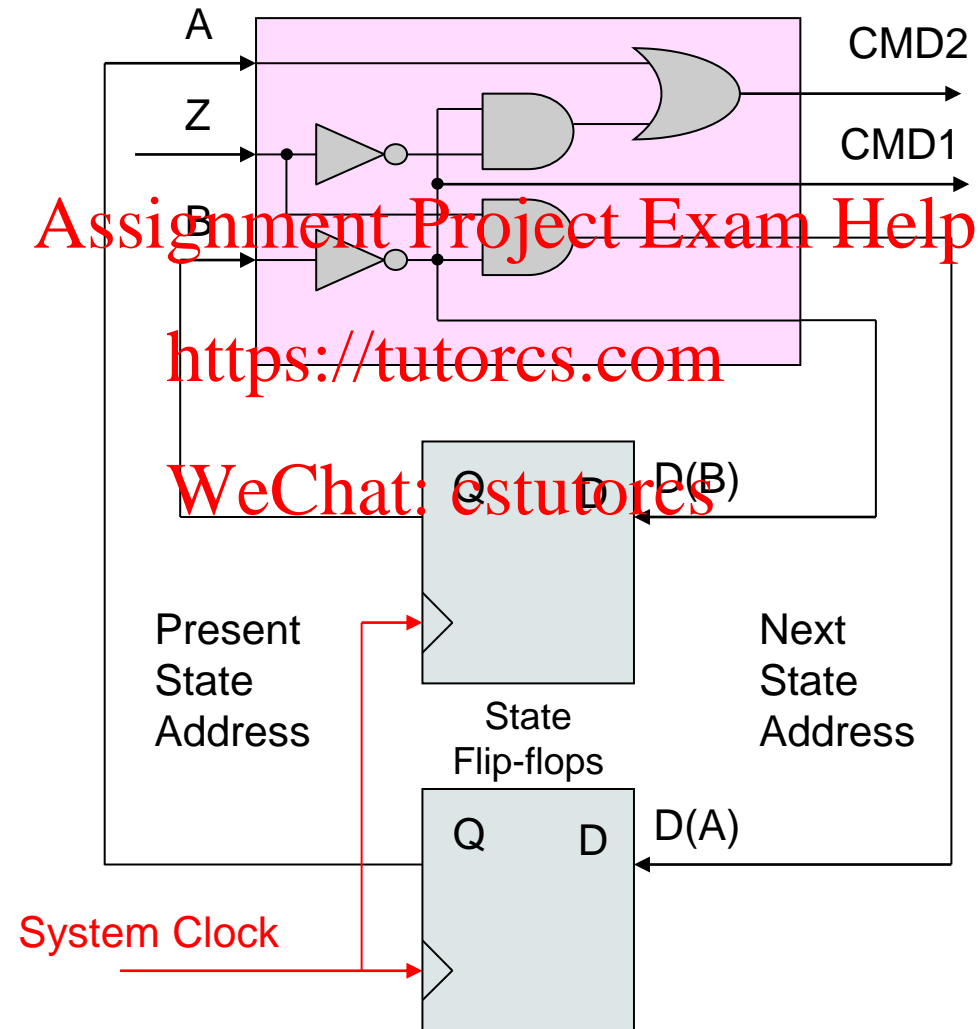

# Altera State Machine Implementation

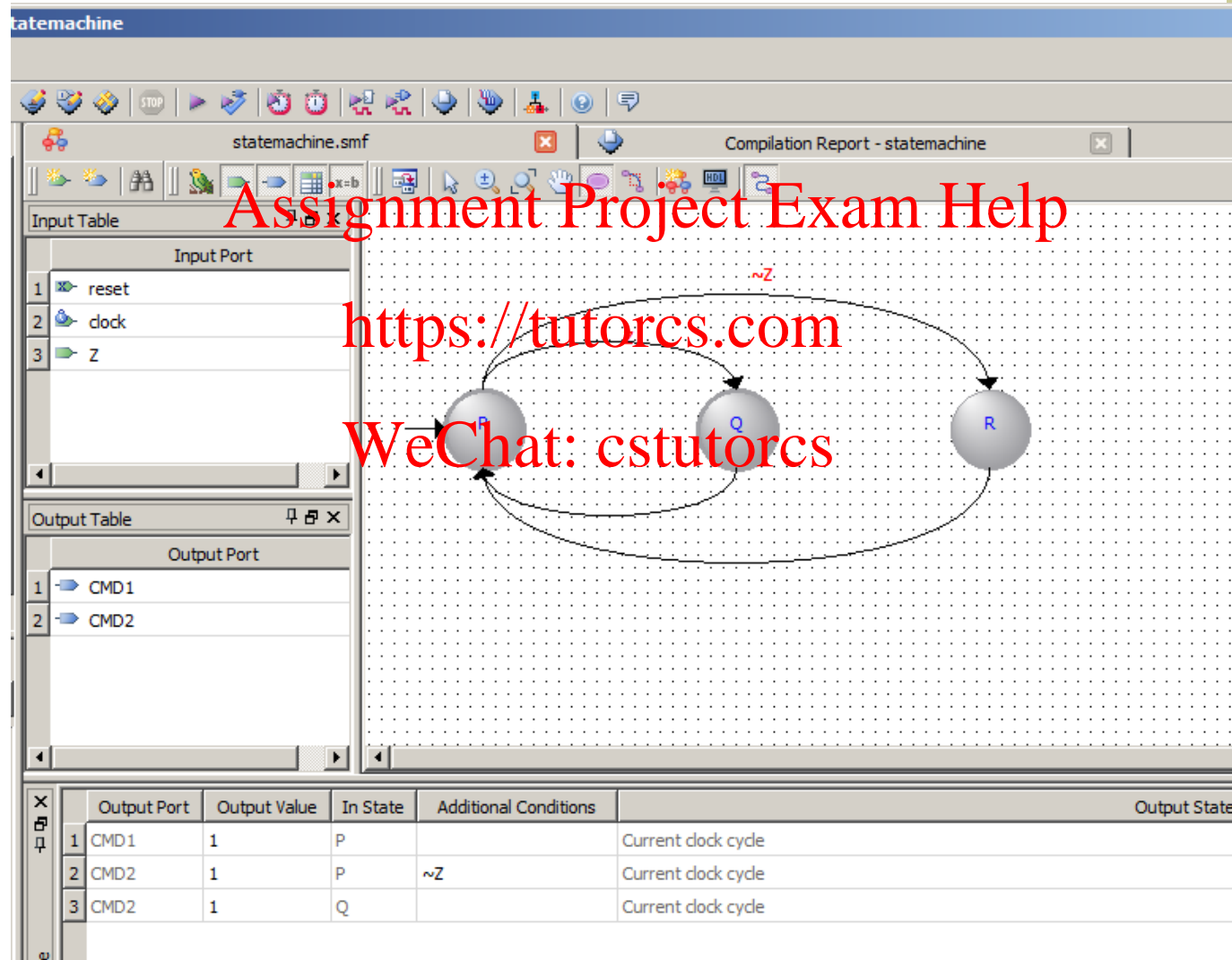

# Verilog Generated by State Machine Wizard

```
22 module statemachine (  
23     reset, clock, Z,  
24     CMD1, CMD2);  
25  
26     input reset;  
27     input clock;  
28     input Z;  
29     tri0 reset;  
30     tri0 Z;  
31     output CMD1;  
32     output CMD2;  
33     reg CMD1;  
34     reg CMD2;  
35     reg [2:0] fstate;  
36     reg [2:0] reg_fstate;  
37     parameter P=0, Q=1, R=2;  
38  
39     always @(posedge clock)  
40     begin  
41         if (clock) begin  
42             fstate <= reg_fstate;  
43         end  
44     end  
45
```

Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs

```
46     always @(fstate or reset or Z)  
47     begin  
48         if (reset) begin  
49             reg_fstate <= P;  
50             CMD1 <= 1'b0;  
51             CMD2 <= 1'b0;  
52         end  
53         else begin  
54             CMD1 <= 1'b0;  
55             CMD2 <= 1'b0;  
56             case (fstate)  
57                 P: begin  
58                     if (Z)  
59                         reg_fstate <= Q;  
60                     else if (~Z)  
61                         reg_fstate <= R;  
62                     // Inserting 'else' block to prevent latch inference  
63                     else  
64                         reg_fstate <= P;  
65                 end  
66                 if (~Z)  
67                     CMD2 <= 1'b1;  
68                 // Inserting 'else' block to prevent latch inference  
69                 else  
70                     CMD2 <= 1'b0;  
71  
72                 CMD1 <= 1'b1;  
73             end  
74             Q: begin  
75                 reg_fstate <= P;  
76  
77                 CMD2 <= 1'b1;  
78             end  
79             R: begin  
80                 reg_fstate <= P;  
81             end  
82             default: begin  
83                 CMD1 <= 1'bx;  
84                 CMD2 <= 1'bx;  
85                 $display ("Reach undefined state");  
86             end  
87         endcase  
88     end  
89 end  
90 endmodule // statemachine  
91
```

# Better Verilog


```
1 module statemachine( cmd1, cmd2, clk, reset_n, z);
2   input    clk;
3   input    reset_n;
4   input    z;
5   output   cmd1, cmd2;
6
7   reg [1:0] p_state, n_state;
8   reg      cmd1, cmd2;
9
10  parameter S_P=2'b00, S_Q=2'b01, S_R=2'b10, S_Q=2'b11;
11
12  always @ (posedge clk, negedge reset_n)
13    if (reset_n == 0) p_state <= S_P;
14    else p_state <= n_state;
15
16  always @ (p_state, z)
17  begin
18    cmd1 = 1'b0;
19    cmd2 = 1'b0;
20    n_state = p_state;
21    case (p_state)
22      S_P: begin
23        cmd1 = 1'b1;
24        if (z)
25          n_state = S_Q;
26        else
27          begin
28            cmd2 = 1'b1;
29            n_state = S_R;
30          end
31        end
32      S_R: begin
33        n_state = S_P;
34      end
35      S_Q: begin
36        cmd2 = 1'b1;
37        n_state = S_P;
38      end
39    endcase
40  end
41 endmodule
```

p\_state is the output of the state flip-flops  
n\_state is what will be loaded into the state  
flip-flops on the next active clock edge

Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs

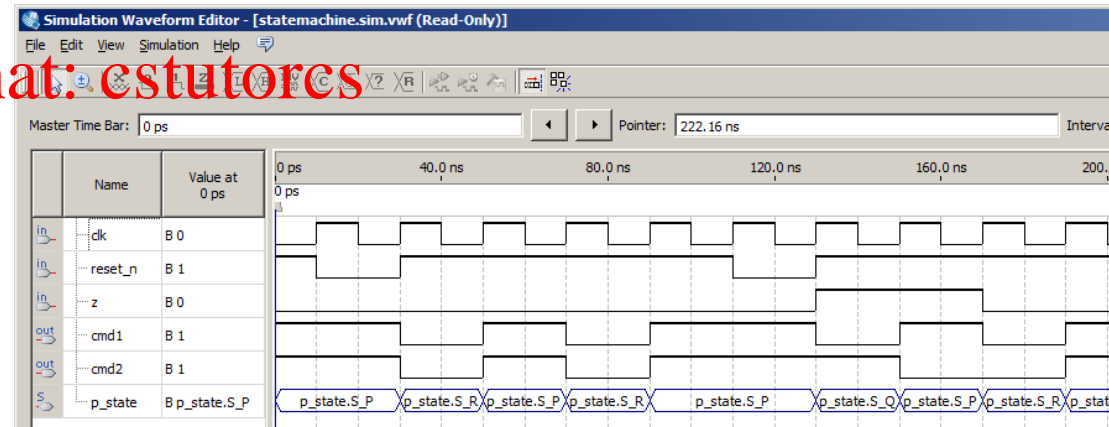

Note simulator only shows states when  
“Quartus II Simulator” selected under  
“Simulation/Options”