



UNIVERSITY OF  
LIVERPOOL

# Digital Systems Design

## ELEC373/473

Assignment/Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs

## Counters Again


Prof J.S. Smith  
Room A515;  
E-mail: [j.s.smith@liv.ac.uk](mailto:j.s.smith@liv.ac.uk)
 
# Decade Counter




Rco = ripple carry out  
True when count =  
max and ent is valid

Counter increments on clock  
active edge when ent & enp =  
True



Cascade counter by connecting rco of lsb to ent of msb  
Use common enp to enable counters

# Decade counter ASM

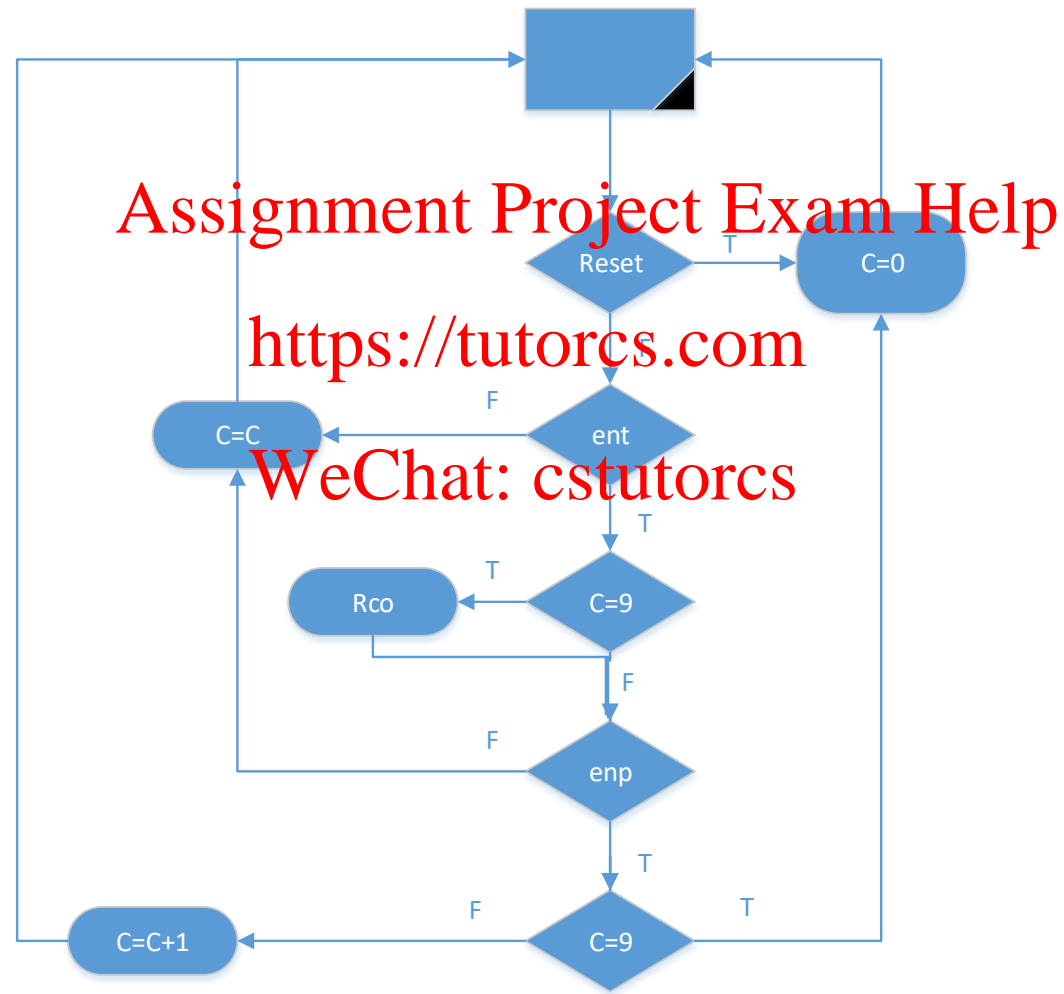

# Decade Counter


```
1  module count10 (input clk, input rst, input enp, input ent, output [3:0] count, output
   reg rco);
2      // standard decade counter with rco
3      // and two enables ent & enp.
4      // ent also enables rco
5      reg [3:0] pstate, nstate; // Present state and Next State
6      assign count = pstate;
7
8      always @(posedge clk)
9      begin
10         if (clk) begin // technically "if (clk)" not needed as only clk in list
11             pstate <= nstate; // load next state into present state at next clock edge
12         end
13     end
14
15     always @(pstate, rst, enp, ent) // could be ",," or "or"
16     begin
17         rco = 1'b0; // default value to stop latch synthesis
18         nstate = pstate; // default assignment to stop latch synthesis
19         if (rst) begin // synchronous active high reset
20             nstate = 4'b0;
21         end
22         else
23         begin
24             if (ent) // enable rco if count = 9 and ent valid
25             begin
26                 if (pstate == 4'b1001)
27                     rco = 1'b1;
28                 if (enp) // count if ent and enp valid
29                     if (pstate == 4'b1001) // if 9 go to 0
30                         nstate = 4'b0000;
31                     else
32                         nstate = pstate + 4'b0001; // otherwise add 1.
33             end
34         end
35     end
36 endmodule // count10
37
```

Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs

# Synthesised design of decade counter

 

WeChat: cstutorcs

Note that rco is cleared by the reset, is that needed?

# Decade Counter - 2


```
1  module count10 (input clk, input rst, input enp, input ent, output [3:0] count, output reg rco);
2  // standard decade counter with 4 bits output
3  // can be cascaded to build larger sequential counters
4  // only counts if ent and enp are valid
5  // produce rco output which should be connected to
6  // ent of the next stage
7
8  reg [3:0] pstate, nstate;
9  assign count = pstate;
10
11  always @(posedge clk)
12  begin
13      if (clk) begin
14          pstate <= nstate;
15      end
16  end
17
18  always @(pstate, rst, enp, ent)
19  begin
20      rco = 1'b0; //default to prevent latch assignment
21      nstate = pstate; //default to prevent latch assignment
22      if (rst)
23      begin
24          nstate = 4'b0;
25          rco = 1'bx;
26      end
27      else
28      begin
29          if (ent)
30          begin
31              if (pstate == 4'b1001)
32                  rco = 1'b1;
33              if (enp)
34                  if (pstate == 4'b1001)
35                      nstate = 4'b0000;
36                  else
37                      nstate = pstate + 4'b0001;
38          end
39      end
40  end
41  endmodule
```

Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs

# Synthesised decade counter (2)

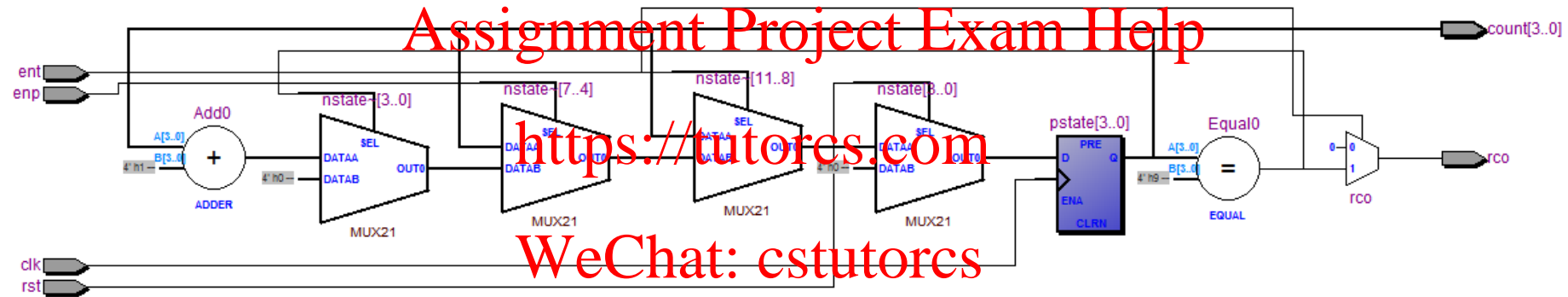

# Decade Counter - 3

```
1  module count10 (input clk, input rst, input enp, input ent, output [3:0] count, output rco);
2  // standard decade counter with 4 bits output
3  // can be cascaded to build larger sequential counters
4  // only counts if ent and enp are valid
5  // produce rco output which should be connected to
6  // ent of the next stage
7
8  reg [3:0] pstate, nstate;
9
10 assign count = pstate;
11 assign rco = (pstate==4'b1001) & ent;
12
13 always @(posedge clk)
14 begin
15     if (clk) begin
16         pstate <= nstate;
17     end
18 end
19
20 always @(pstate, rst, enp, ent)
21 begin
22     nstate = pstate; //default to prevent latches
23     if (rst)
24     begin
25         nstate = 4'b0;
26     end
27     else
28     begin
29         if (ent & enp)
30         begin
31             if (pstate == 4'b1001)
32                 nstate = 4'b0000;
33             else
34                 nstate = pstate + 4'b0001;
35         end
36     end
37 end
38 endmodule
```

Assignment Project Exam Help


Use assign to generate rco

Note rco now not declared as 'reg'  
as it is always being assigned

WeChat: cstutorcs





# Synthesised decade counter (3)

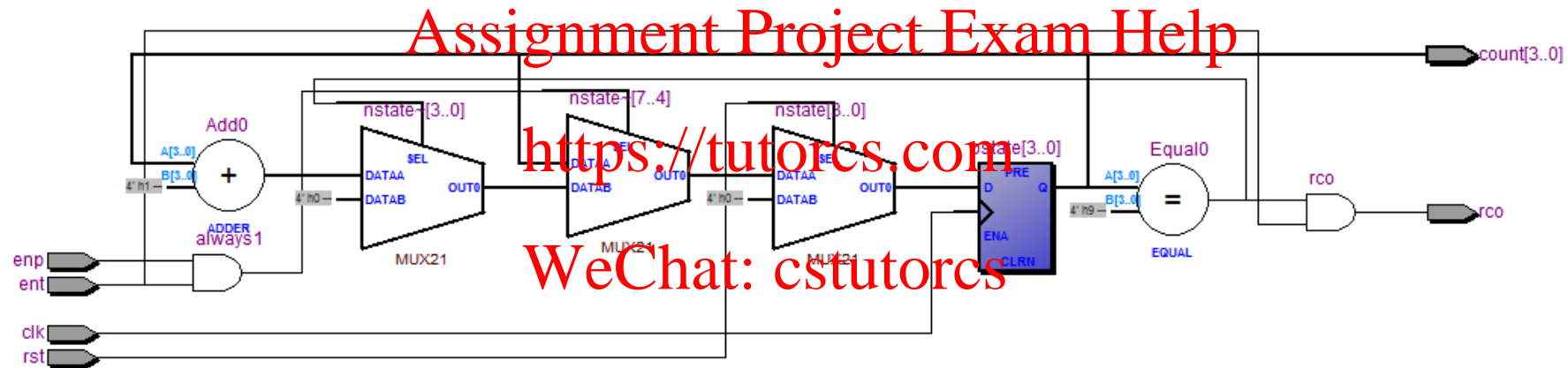

 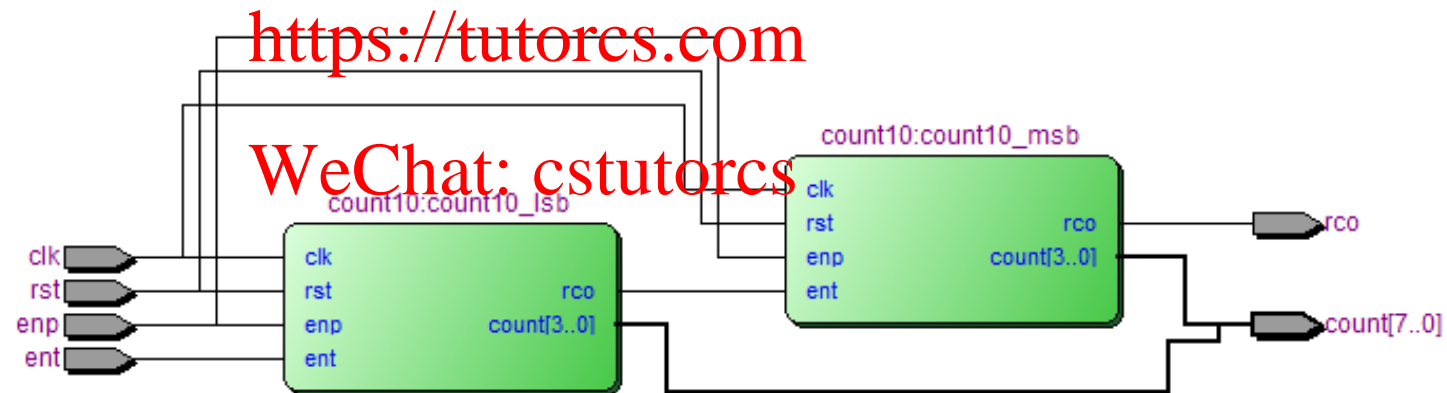
# Hundred Counter

```
1 module count100 (input clk, input rst, input enp, input ent, output[7:0] count, output rco);
2
3     wire rco_int;
4
5     count10 count10_lsb(clk, rst, enp, ent, count[3:0], rco_int);
6     count10 count10_msb(clk, rst, enp, ent, count[7:4], rco);
7
8 endmodule // count100
9
```



# Large Counter (bigpulse)

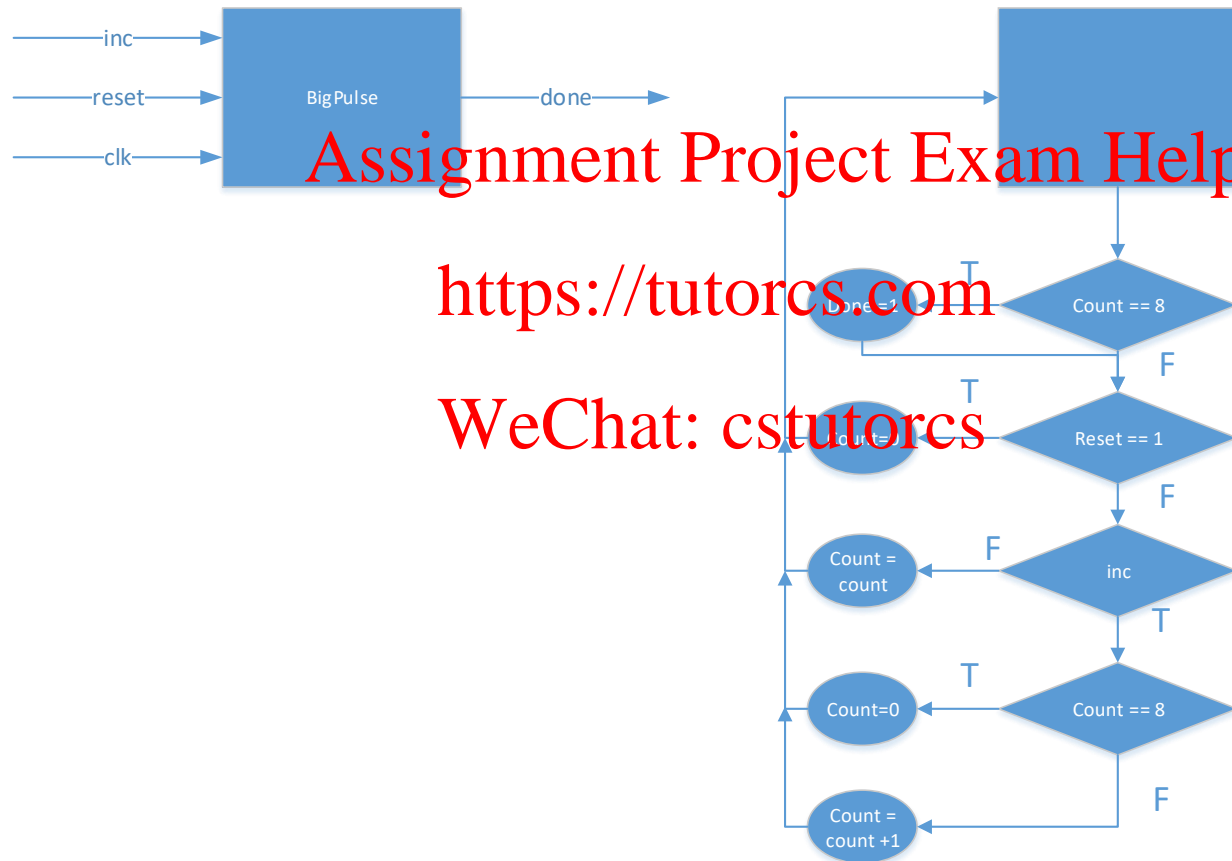

# Verilog for bigpulse


```
1 module bigpulse (input clk, input reset, input inc, output reg done);
2 // a counter that counts up to a big number and generates a pulse when the
3 // count is reached and then resetting to 0
4
5 // assign the variables to hold the present count
6 // and the next count (8 bits for this example)
7 reg [7:0] pcount, ncount;
8
9 // the sequential code to synthesise the latches
10 always @(posedge clk)
11     pcount <= ncount; // load next count into present count
12
13 // the combinational code to increment the count if required
14 // for simulation tests just count to 8
15
16 always @(pcount, reset, inc)
17 begin
18     done = 1'b0; // specify the defaults
19     ncount = pcount; // stops latch synthesis
20     if (pcount == 8'd8) // if c = max
21         done = 1'b1;
22     if (reset) // check for synchronous reset check
23     begin
24         ncount = 8'd0; // if reset clear next count
25         done = 1'bx;
26     end
27     else
28     if (inc) // if enabled
29     if (pcount == 8'd8) // if enabled and c = 8
30         ncount = 8'd0; // set count to 0
31     else
32         ncount = pcount + 8'd1; // else add 1
33     end
34 endmodule // bigcount
35
```

Assignment Project Exam Help


<https://tutorcs.com>

WeChat: cstutorcs

# RTL View for bigpulse

 

WeChat: cstutorcs

 

# Alternate reset implementation


```
1 module bigpulse (input clk, input reset, input inc, output reg done);
2 // a counter that counts up to a big number and generates a pulse when the
3 // count is reached and then resetting to 0
4
5 // assign the variables to hold the present count
6 // and the next count (8 bits for this example)
7 reg [7:0] pcount, ncount;
8
9 // the sequential code to synthesise the latches
10 always @(posedge clk)
11     if (reset)
12         pcount <= 8'd0;
13     else
14         pcount <= ncount; // load next count into present count
15
16 // the combinational code to increment the count if required
17 // for simulation tests just count to 8
18
19 always @(pcount, reset, inc)
20 begin
21     done = 1'b0; // specify the defaults
22     ncount = pcount; // stops latch synthesis
23     if (pcount == 8'd8) // if c = max
24         done = 1'b1;
25     if (inc) // if enabled
26         if (pcount == 8'd8) // if enabled and c = 8
27             ncount = 8'd0; // set count to 0
28         else
29             ncount = pcount + 8'd1; // else add 1
30     end
31 endmodule // bigcount
32
```

Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs

# New RTL View for bigpulse

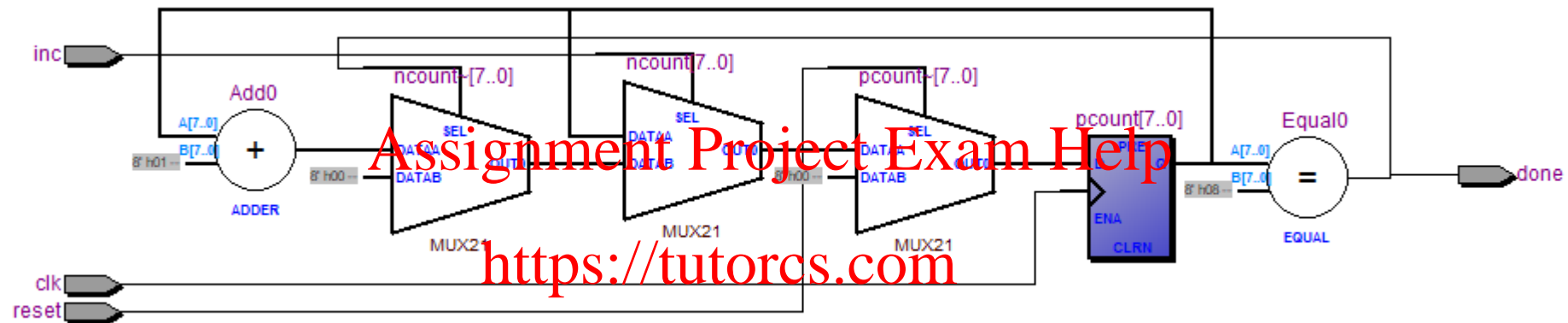

# WeChat: cstutorcs

