

Digital Systems Design

ELEC373/473

Assignment Project Exam Help



<https://tutorcs.com>

WeChat: cstutorcs

Behavioural Modelling

Prof J.S. Smith
Room A515;
E-mail: j.s.smith@liv.ac.uk

Overview of HDLs

- Provides many descriptive styles
 - Structural
 - Register Transfer Level (RTL)
 - Behavioral
- HDL based designs are highly portable and independent of technology.
- HDLs are not like procedural software and cannot run on processors.
- HDLs are a convenient medium for integrating intellectual property (IP) from a variety of sources with a proprietary design.

Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs

Learning Objectives

- Explain the “**always**” and “**initial**” procedures in behavioural modelling.
- Define *blocking* and *nonblocking* procedural assignments.
- Explain conditional statements using “**if**” and “**else**”.
- Describe multiway branching, using “**case**”, “**casex**”, and “**casez**” statements.
- Understand the usage of the *blocking* and *nonblocking* assignments via examples.

Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutors

Why Behavioural Modelling

- Behavioural modelling describes the functionality of a design. It describes
 - **what** the circuit will do
 - **not how** to build it in hardware.
- Designers need to evaluate the tradeoffs of various architectures and algorithms before they implement the optimum one in hardware.
- Behavioural modelling represent the circuit at a **very high level of abstraction**.
- Behavioural modelling provides **flexibility** by allowing part of the design to be modelled at different levels of abstraction.
- Modern synthesis tools are now able to generate RTL circuits from behavioural models:
 - Its “like” using a C compiler rather than working with assemble language (RTL) – But remember its hardware.

Structured Procedures

- *always* and *initial* are the two most basic statements in behavioural modelling.
 - All other behavioural statements can only appear inside these structured procedure statements.
- Verilog is a *concurrent* simulation language.
 - Activity flows in Verilog run in parallel rather than in sequence.
- Each activity flow starts at simulation time 0.
- Each *always* and *initial* statement represent a separate activity flow.
- The *always* and *initial* statements cannot be nested.

always and *initial* statements

- The *always* statement starts at time 0 and executes the statements in a looping fashion.
- The *always* statement is used to model a block of activity that is repeated continuously in a digital circuit.
- The *initial* statement executes exactly once during a *simulation*.
- The *initial* blocks are typically used for initialization, monitoring, waveforms and other processes that must be executed only once during the entire *simulation* run.
 - However the *initial* block in Quartus will set the output values of pins after programming
- The *initial* blocks have no meaning for *synthesis* all initialisation in synthesis is done via the reset signal.
- The statements inside the *always* block are executed sequentially and are “*procedural*” statements.

Procedural Assignments

- Procedural assignments update values of *reg*, *integer*, *real*, or *time variables*.
- The value placed on a *variable* will remain unchanged until another procedural statement updates the *variable*.
- The left-hand side (LHS) of the assignment must be a *variable* and the RHS can be any expression that evaluates to a value.
- The (=) operator is used to specify *blocking* statements.
 - Blocking statements are executed sequentially.
- The (<=) operator is used for *nonblocking* statements.
 - The *nonblocking* assignments allow scheduling of assignments without blocking the execution of the statements that follow in a sequential block.

Verilog Registers

- In digital design, registers represent memory elements.
- Digital registers need a clock to operate and update their state on a certain phase or edge.
- Registers in Verilog should not be confused with hardware registers.
- In Verilog the term register (reg) simply means a variable that can hold its value.
- Verilog registers don't need a clock and don't need to be driven by a net. Values of registers can be changed anytime in a simulation by assigning a new value to the register.

Assignment Project Exam Help

<https://tutorcs.com>


WeChat: cstutorcs

The Sequential always Block

- Edge-triggered circuits are described using a sequential always block


Combinational
 
```
module combinational(a, b, sel, out);  
    input a, b;  
    input sel;  
    output out;  
    reg out;  
    always @ (a or b or sel)  
    begin  
        if (sel) out = a;  
        else out = b;  
    end  
endmodule
```



Sequential
 
```
module sequential(a, b, sel, clk, out);  
    input a, b;  
    input sel, clk;  
    output out;  
    reg out;  
    always @ (posedge clk)  
    begin  
        if (sel) out <= a;  
        else out <= b;  
    end  
endmodule
```



Event Control Statements

- Event Control

- Edge Triggered Event Control
- Level Triggered Event Control

- Edge Triggered Event Control

@ (posedge CLK) //Positive Edge of CLK

Curr_State <= Next_state;

- Level Triggered Event Control

@ (A or B) //change in values of A or B

Out = A & B;

Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs

@ negedge	@ posedge
1 → x	0 → x
1 → z	0 → z
1 → 0	0 → 1
x → 0	x → 1
z → 0	z → 1

Importance of the Sensitivity List

- The use of `posedge` and `negedge` makes an `always` block sequential (edge-triggered)
- Unlike a combinational `always` block, the sensitivity list **does** determine behavior for synthesis!

*D Flip-flop with **synchronous** clear*

```
module dff_sync_clear(d, clearb, clock, q);
input d, clearb, clock;
output q;
reg q;
always @ (posedge clock)
begin
    if (!clearb) q <= 1'b0;
    else q <= d;
end
endmodule
```

always block entered only at
each positive clock edge

*D Flip-flop with **asynchronous** clear*

```
module dff_async_clear(d, clearb, clock, q);
input d, clearb, clock;
output q;
reg q;
always @ (negedge clearb or posedge clock)
begin
    if (!clearb) q <= 1'b0;
    else q <= d;
end
endmodule
```

always block entered immediately
when (active-low) clearb is asserted

Note: The following is **incorrect** syntax: `always @ (clear or negedge clock)`
If one signal in the sensitivity list uses `posedge`/`negedge`, then all signals must.

- Assign any signal or variable from only one `always` block, Be wary of race conditions: `always` blocks execute in parallel

Cyclic Behavioural Models of Flip-flops and Latches

- **Continuous assignments** cannot model an element that has edge-sensitive behaviour, such as a flip-flop.
- Verilog uses a cyclic behaviour to model edge-sensitivity behaviour.
- **Cyclic behaviours** are abstract (they do not use hardware to specify signal values).

<https://tutorcs.com>
WeChat: cstutorcs

```
module dff_behav( q, qbar, data, set, reset, clk);  
input    data, set, reset, clk;  
output  q, q_bar;  
reg     q;  
assign  q_bar = ~q;  
always @ (posedge clk) // Flip-flop with synchronous set/reset  
    begin  
        if (reset == 0) q<=0; else if (set == 0) q<=1; else q<= data;  
    end  
endmodule
```

Conditional Statement

- The *conditional* statement (or *if-else* statement) is used to make a decision as to whether a statement is executed or not.
- **if** (**expression**) **statement_or_null**
 [**else** **statement_or_null**]
 - If the expression evaluates to **true** the first statement shall be executed.
 - If it evaluates to **false** (has a **zero** value or the value is **x** or **z**), the first statement shall not execute.
 - If there is an **else** statement and the expression is **false**, the **else** **statement** shall be executed.

Conditional Statement (cont.)

```
if (index > 0)
    if (rega > regb)
        result = rega;
    else
        result = regb;
```

Assignment Project Exam Help

<https://tutorcs.com>


WeChat: cstutorcs

else applies to preceding **if** as both **ifs** do not have the optional **else**.

```
if (index > 0)      begin
    if (rega > regb)
        result = rega;
    end
else result = regb;
```

begin-end block statement shall be used to force the proper association. Now **else** applies to the first **if**.


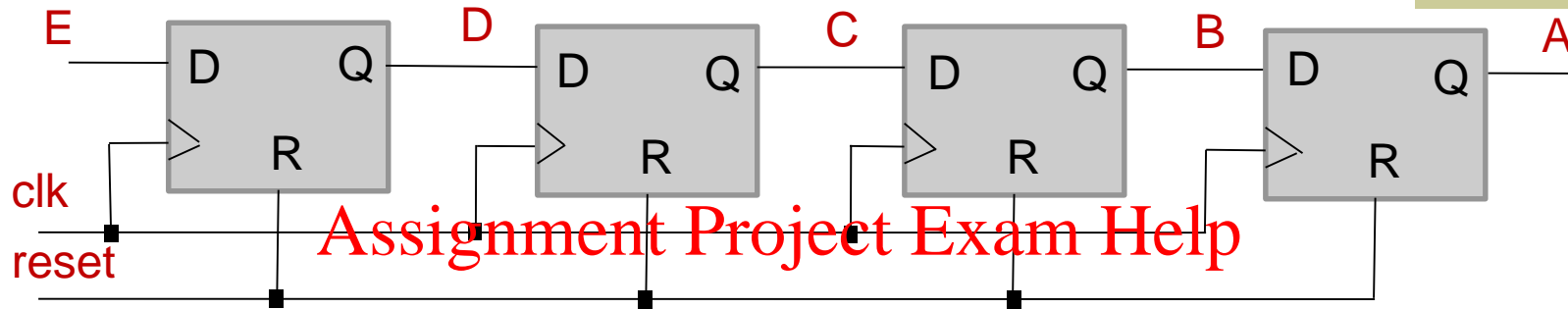
Shift Register Model using Blocking Assignment



```
module ShiftRegister(A, E, reset, clk);  
  input  E, reset, clk;  
  output A;  
  reg    A, B, C, D;  
  always @ (posedge clk or posedge reset)  
  begin  
    if (reset) begin A=0; B=0; C=0; D=0; end  
    else begin A=B; B=C; C=D; D=E; end  
  end  
endmodule
```

The list of statements are
executed in sequential order.
Blocking assignments.


Simulation and Synthesis

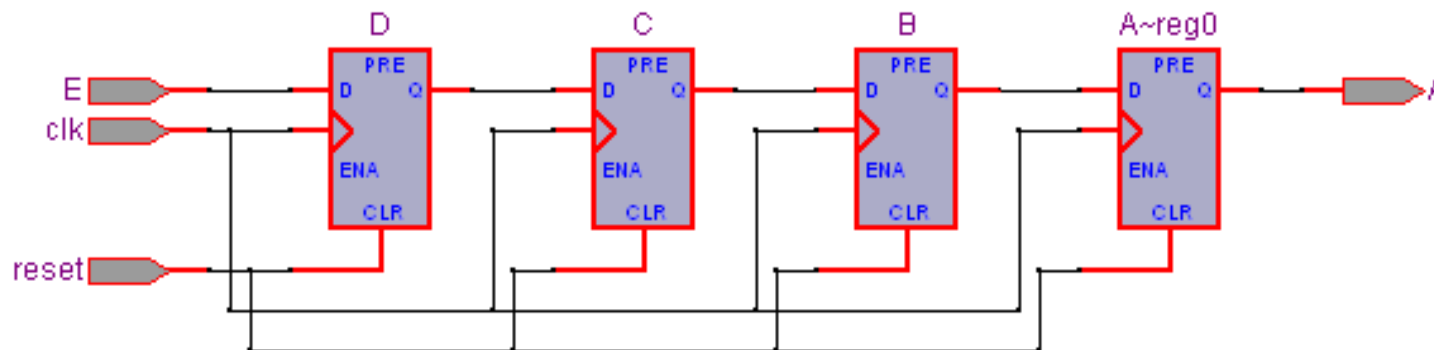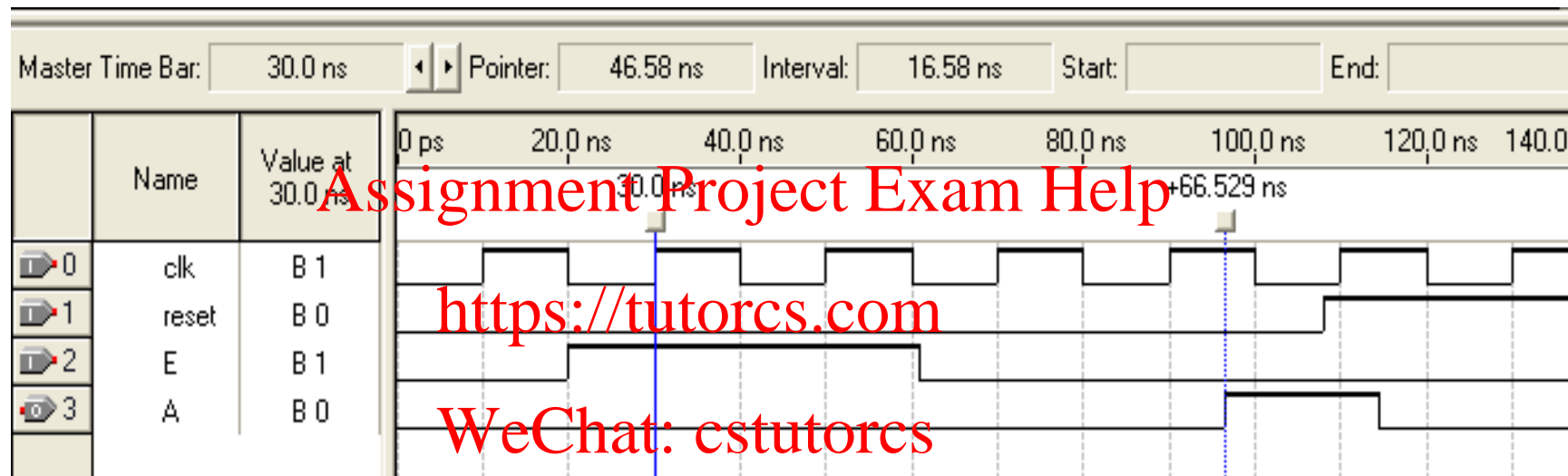

Order of Execution in Blocking Assignments

```
module ShiftRegister( A, E, reset, clk);  
input  E, reset, clk;  
output A;  
reg    A, B, C, D;  
always @ (posedge clk or posedge reset)  
begin  
    if (reset) begin A=0; B=0; C=0; D=0; end  
    else begin D=E; C=D; B=C; A=B; end // Equivalent to A=E  
end  
endmodule
```


Only one flip-flop
is synthesised.

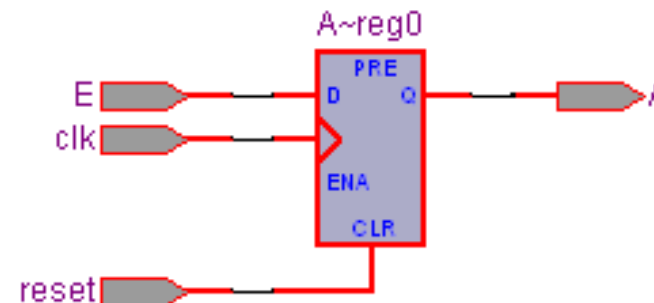

Shift Register using Nonblocking Statements

```
module ShiftRegister( A, E, reset, clk);  
  input  E, reset, clk;  
  output A;  
  reg    A, B, C, D;  
  always @ (posedge clk or posedge reset)  
  begin  
    if (reset) begin A=0; B=0; C=0; D=0; end  
    else begin D<=E; C<=D; B<=C; A<=B; end // The order is unimportant  
  end  
endmodule
```

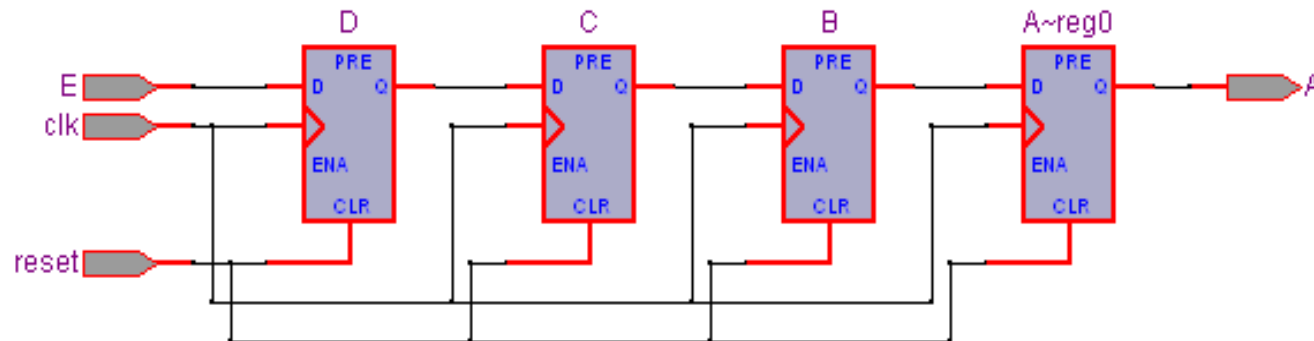All of the variables in the RHS of the nonblocking assignments (\leq) are sampled and held in memory to update the RHS variables concurrently.



Case Statement

- The *case statement* is a multiway decision statement.

- **case** (**expression**)


expression { , **expression** } : **statement_or_null**

| **default** [:] **statement_or_null**

endcase


- The *case item expressions* shall be evaluated and compared with the *case expression* in the exact order in which they are given.
- During the linear search, if a match occurs then the **statement** associated with that case item shall be executed.
- The default **statement** executes if all comparisons fail.
- The default statement is optional.

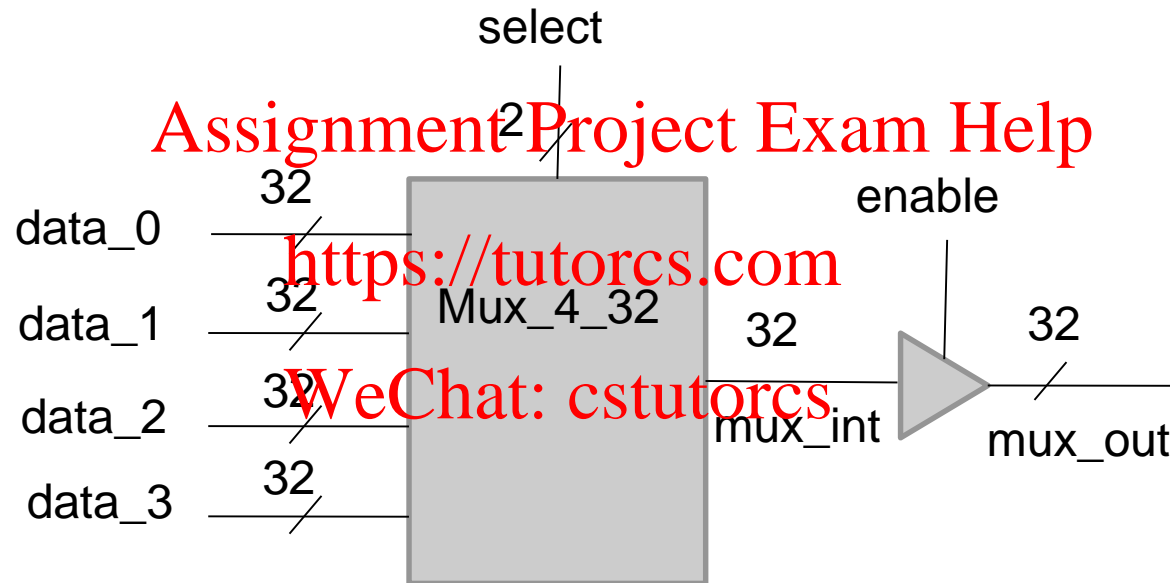4-channel 32-bit Multiplexer with tri-state




Behavioural Model of the 4-channel 32-bit Multiplexer

```
module Mux_4_32_case (mux_out, data_3, data_2, data_1, data_0, select,
    enable);
    output [31:0] mux_out;
    input [31:0] data_3, data_2, data_1, data_0, [1:0] select ;
    input enable;
    reg [31:0] mux_int;
    assign mux_out = enable ? mux_int : 32'bz;
    always @ (data_3 or data_2 or data_1 or data_0 or select)
        case (select)
            0:      mux_int = data_0;
            1:      mux_int = data_1;
            2:      mux_int = data_2;
            3:      mux_int = data_3;
            default mux_int = 32'bx;
        endcase
endmodule
```

 

Synthesised Design

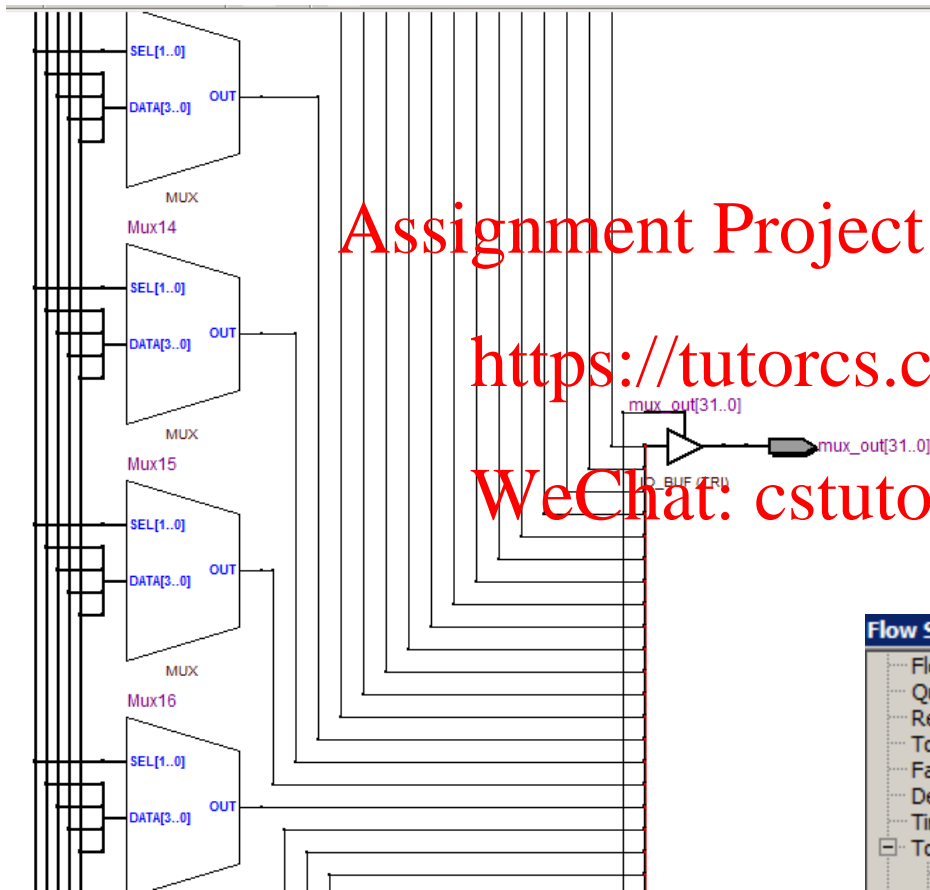

Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs

Flow Summary	
Flow Status	Successful - Mon Oct 10 10:19:23 2011
Quartus II 64-Bit Version	11.0 Build 208 07/03/2011 SP 1 SJ Full Version
Revision Name	Mux_4_32_case
Top-level Entity Name	Mux_4_32_case
Family	Cyclone II
Device	EP2C35F672C6
Timing Models	Final
Total logic elements	64 / 33,216 (< 1 %)
Total combinational functions	64 / 33,216 (< 1 %)
Dedicated logic registers	0 / 33,216 (0 %)
Total registers	0
Total pins	163 / 475 (34 %)
Total virtual pins	0
Total memory bits	0 / 483,840 (0 %)
Embedded Multiplier 9-bit elements	0 / 70 (0 %)
Total PLLs	0 / 4 (0 %)


Multiplexer Model using Nested Conditional Statements

```
module Mux_4_32_if (mux_out, data_3, data_2, data_1, data_0, select,
    enable);
output [31:0] mux_out;
input [31:0] data_3, data_2, data_1, data_0, [1:0] select ;
input enable;
reg [31:0] mux_int;

assign mux_out = enable ? mux_int : 32'bz;

always @ (data_3 or data_2 or data_1 or data_0 or select)
    if (select ==0) mux_int = data_0; else
        if (select ==1) mux_int = data_1; else
            if (select ==2) mux_int = data_2; else
                if (select ==3) mux_int = data_3; else mux_int = 32'bx;
endmodule
```

Synthesised Design

 

Assignment Project Exam Help


<https://tutorcs.com>

WeChat: cstutorcs

Flow Summary


Flow Status	Successful - Mon Oct 10 10:13:14 2011
Quartus II 64-Bit Version	11.0 Build 208 07/03/2011 SP 1 SJ Full Version
Revision Name	Mux_4_32_if
Top-level Entity Name	Mux_4_32_if
Family	Cyclone II
Device	EP2C35F672C6
Timing Models	Final
Total logic elements	64 / 33,216 (< 1 %)
Total combinational functions	64 / 33,216 (< 1 %)
Dedicated logic registers	0 / 33,216 (0 %)
Total registers	0
Total pins	163 / 475 (34 %)
Total virtual pins	0
Total memory bits	0 / 483,840 (0 %)
Embedded Multiplier 9-bit elements	0 / 70 (0 %)
Total PLLs	0 / 4 (0 %)

Encoder

 

```
module encoder (Code, Data);
output [2:0] Code;
Input [7:0] Data;
reg [2:0] Code;
always @ ( Data )
begin
    if (Data == 8'b00000001 ) Code = 3'b000; else
    if (Data == 8'b00000010 ) Code = 3'b001; else
    if (Data == 8'b00000100 ) Code = 3'b010; else
    if (Data == 8'b00001000 ) Code = 3'b011; else
    if (Data == 8'b00010000 ) Code = 3'b100; else
    if (Data == 8'b00100000 ) Code = 3'b101; else
    if (Data == 8'b01000000 ) Code = 3'b110; else
    if (Data == 8'b10000000 ) Code = 3'b111; else
        Code = 3'bx;
end
endmodule
```

Synthesised design

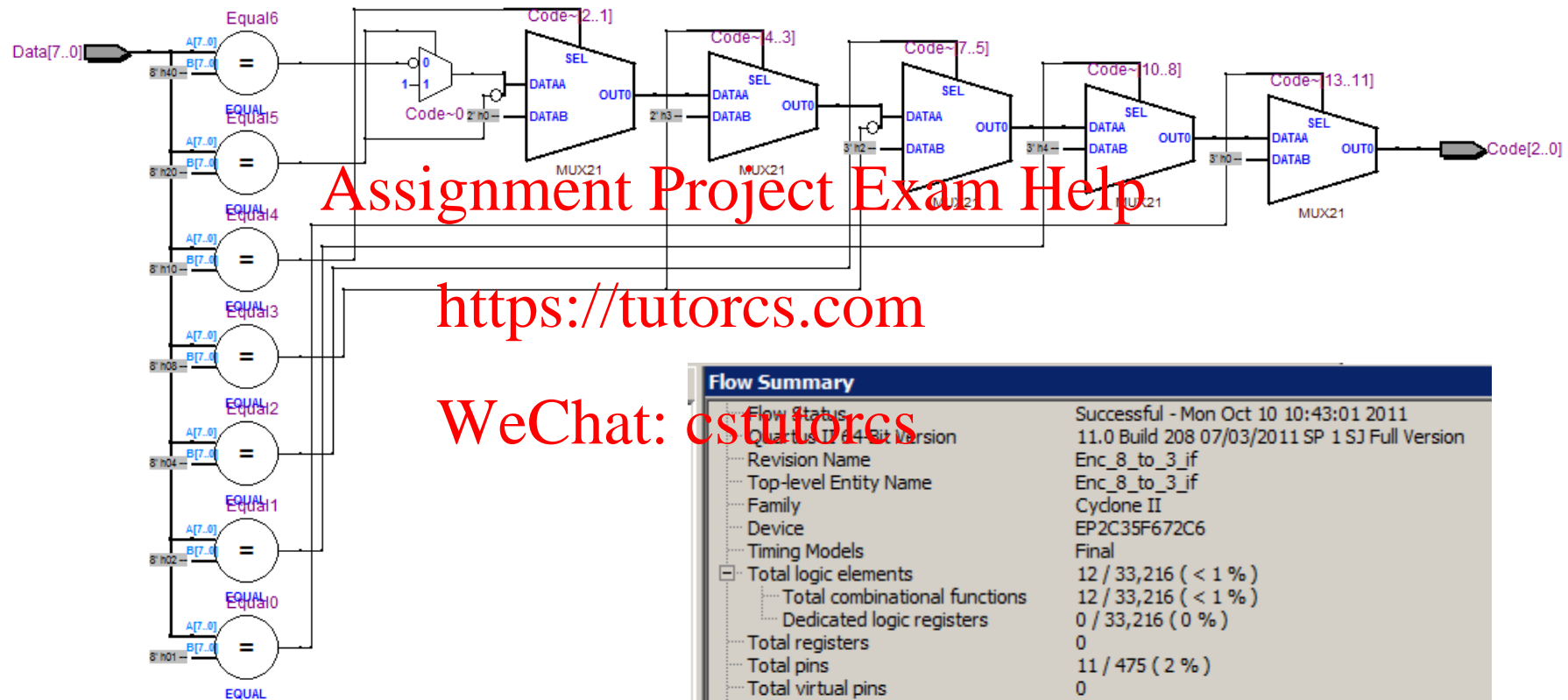


Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs

Flow Summary		
Flow status	Successful - Mon Oct 10 10:43:01 2011	
Quartus II 64-Bit Version	11.0 Build 208 07/03/2011 SP 1 SJ Full Version	
Revision Name	Enc_8_to_3_if	
Top-level Entity Name	Enc_8_to_3_if	
Family	Cyclone II	
Device	EP2C35F672C6	
Timing Models	Final	
Total logic elements	12 / 33,216 (< 1 %)	
Total combinational functions	12 / 33,216 (< 1 %)	
Dedicated logic registers	0 / 33,216 (0 %)	
Total registers	0	
Total pins	11 / 475 (2 %)	
Total virtual pins	0	
Total memory bits	0 / 483,840 (0 %)	
Embedded Multiplier 9-bit elements	0 / 70 (0 %)	
Total PLLs	0 / 4 (0 %)	

Simulation Results

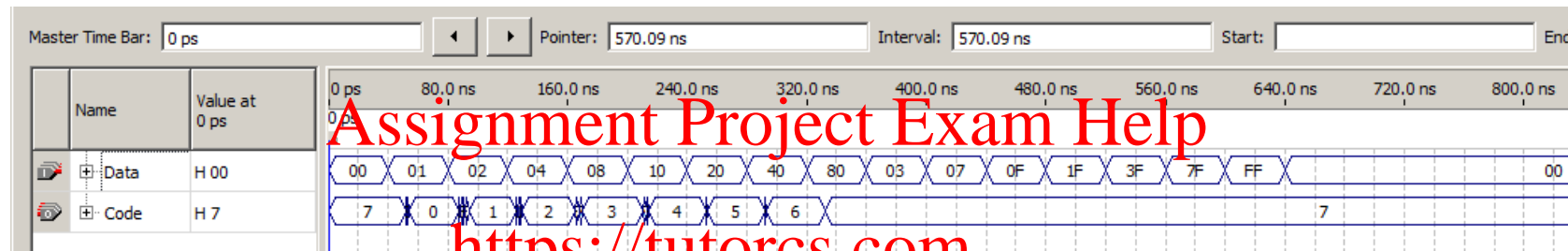


Assignment Project Exam Help

<https://tutorcs.com>


WeChat: cstutorcs

Encoder

 


```
module encoder (Code, Data);
output [2:0] Code;
input [7:0] Data;
reg [2:0] Code;
always @ (Data)
case (Data)
8'b00000001 : Code = 3'b000;
8'b00000010 : Code = 3'b001;
8'b00000100 : Code = 3'b010;
8'b00001000 : Code = 3'b011;
8'b00010000 : Code = 3'b100;
8'b00100000 : Code = 3'b101;
8'b01000000 : Code = 3'b110;
8'b10000000 : Code = 3'b111;
default      Code = 3'bx;
endcase
endmodule
```

Synthesised design

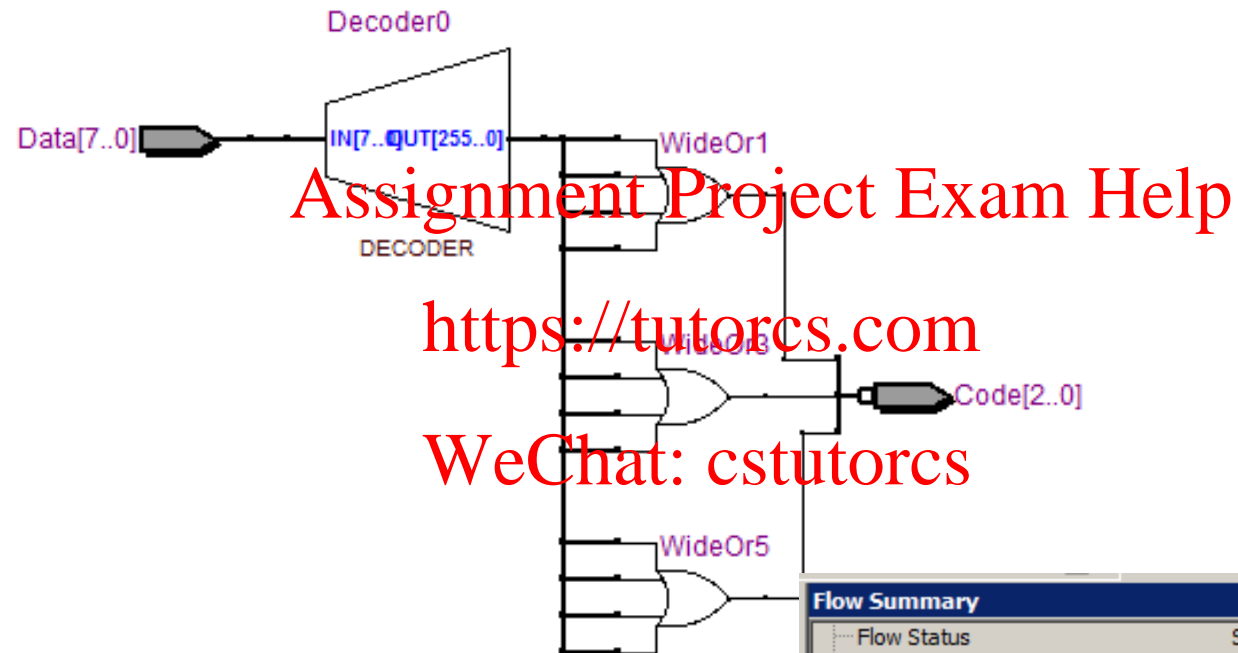

Flow Summary	
Flow Status	Successful - Mon Oct 10 10:39:27 2011
Quartus II 64-Bit Version	11.0 Build 208 07/03/2011 SP 1 SJ Full Version
Revision Name	Enc_8_to_3_case
Top-level Entity Name	Enc_8_to_3_case
Family	Cyclone II
Device	EP2C35F672C6
Timing Models	Final
Total logic elements	8 / 33,216 (< 1 %)
Total combinational functions	8 / 33,216 (< 1 %)
Dedicated logic registers	0 / 33,216 (0 %)
Total registers	0
Total pins	11 / 475 (2 %)
Total virtual pins	0
Total memory bits	0 / 483,840 (0 %)
Embedded Multiplier 9-bit elements	0 / 70 (0 %)
Total PLLs	0 / 4 (0 %)

Simulation Results

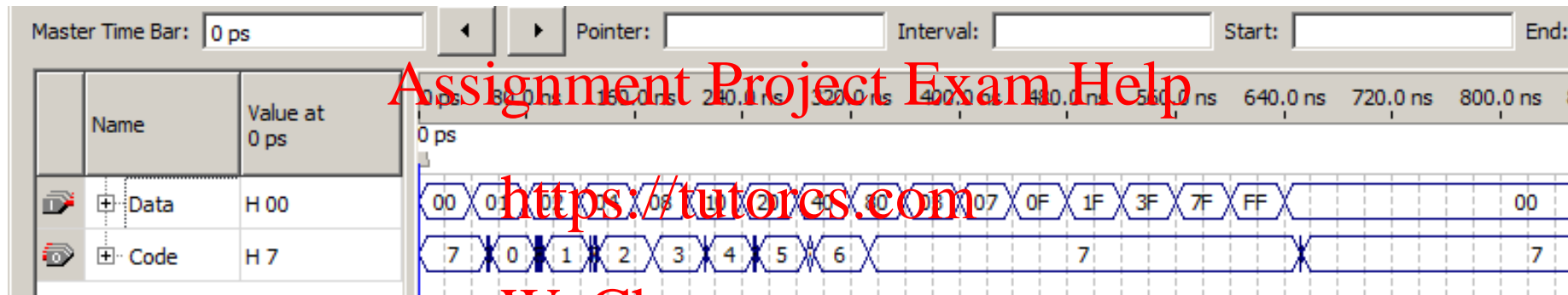

Case Statement with don't-cares

- **casez** treats high-impedance values (z) as don't-cares.
- **casex** treats both high-impedance (z) and unknown (x) values as don't-cares.
- The use of **casex** and **casez** allows comparison of only non-x and non-z positions in the case expression.

reg [7:0] ir;

casez (ir)

8'b1??????? : instruction1(ir); // ? represents the possibility of z

// The instruction1 task is called if the MSB of ir is 1.

8'b01??????? : instruction2(ir);

8'b00010??? : instruction3(ir);

8'b000001?? : instruction4(ir);


endcase

Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs

Priority Encoder

 


```
module encoder (Code, valid_data, Data);
output [2:0] Code;
output valid_data;
input [7:0] Data;
reg [2:0] Code;
assign valid_data = |Data;
always @ (Data)
    casex (Data)
        8'b1xxxxxx : Code = 7;
        8'b01xxxxx : Code = 6;
        8'b001xxxx : Code = 5;
        8'b0001xxx : Code = 4;
        8'b00001xx : Code = 3;
        8'b000001x : Code = 2;
        8'b0000001x : Code = 1;
        8'b00000001 : Code = 0;
        default : Code = 3'bx;
    endcase
endmodule
```

Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs

Synthesised Design

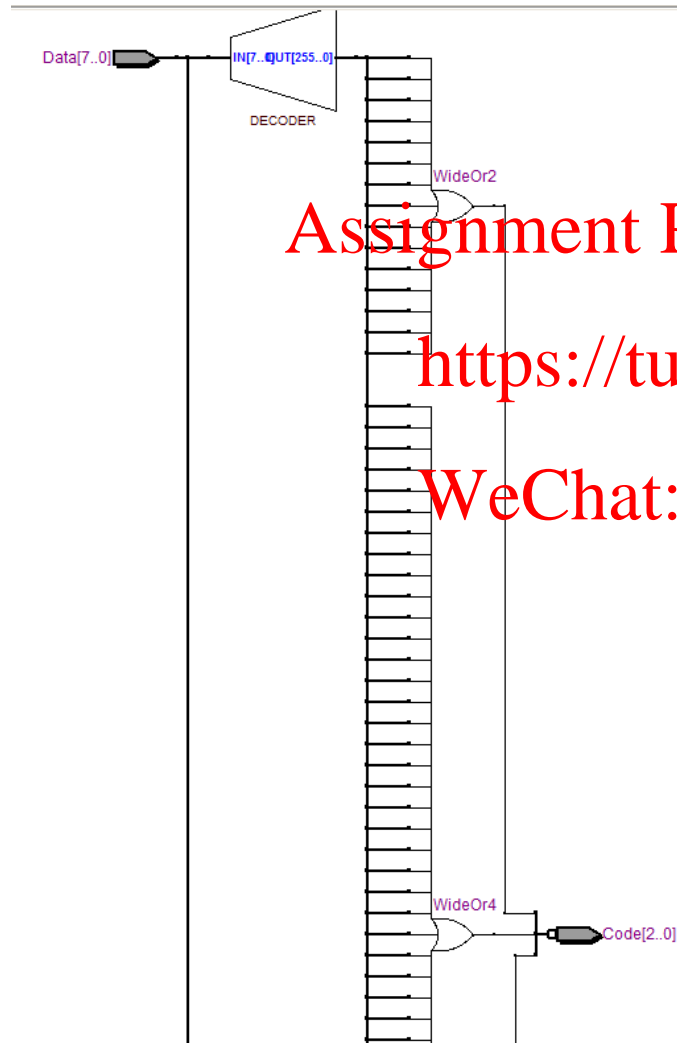


Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs


Flow Summary	
Flow Status	Successful - Mon Oct 10 11:09:02 2011
Quartus II 64-Bit Version	11.0 Build 208 07/03/2011 SP 1 SJ Full Version
Revision Name	PEnc_8_to_3_casex
Top-level Entity Name	PEnc_8_to_3_casex
Family	Cyclone II
Device	EP2C35F672C6
Timing Models	Final
Total logic elements	10 / 33,216 (< 1 %)
Total combinational functions	10 / 33,216 (< 1 %)
Dedicated logic registers	0 / 33,216 (0 %)
Total registers	0
Total pins	12 / 475 (3 %)
Total virtual pins	0
Total memory bits	0 / 483,840 (0 %)
Embedded Multiplier 9-bit elements	0 / 70 (0 %)
Total PLLs	0 / 4 (0 %)

Simulation Results

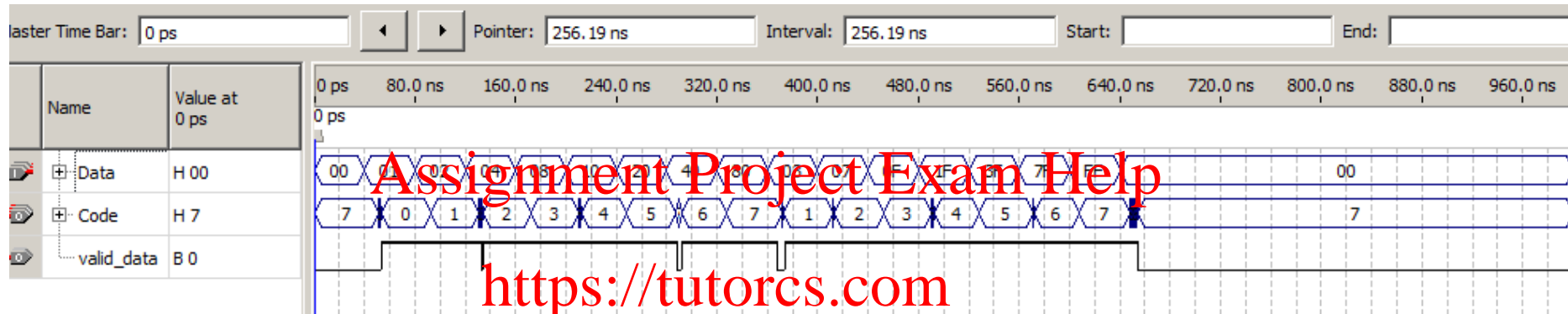


WeChat: cstutorcs

Priority Encoder

 

```
module priority (Code, valid_data, Data);
output [2:0] Code;
output valid_data;
input [7:0] Data;
reg [2:0] Code;
assign valid_data = |Data; // Reduction or operator
always @ ( Data )
begin
    if ( Data [7] ) Code = 7; else
    if ( Data [6] ) Code = 6; else
    if ( Data [5] ) Code = 5; else
    if ( Data [4] ) Code = 4; else
    if ( Data [3] ) Code = 3; else
    if ( Data [2] ) Code = 2; else
    if ( Data [1] ) Code = 1; else
    if ( Data [0] ) Code = 0; else Code = 3'bx;
end
endmodule
```

Synthesised Design

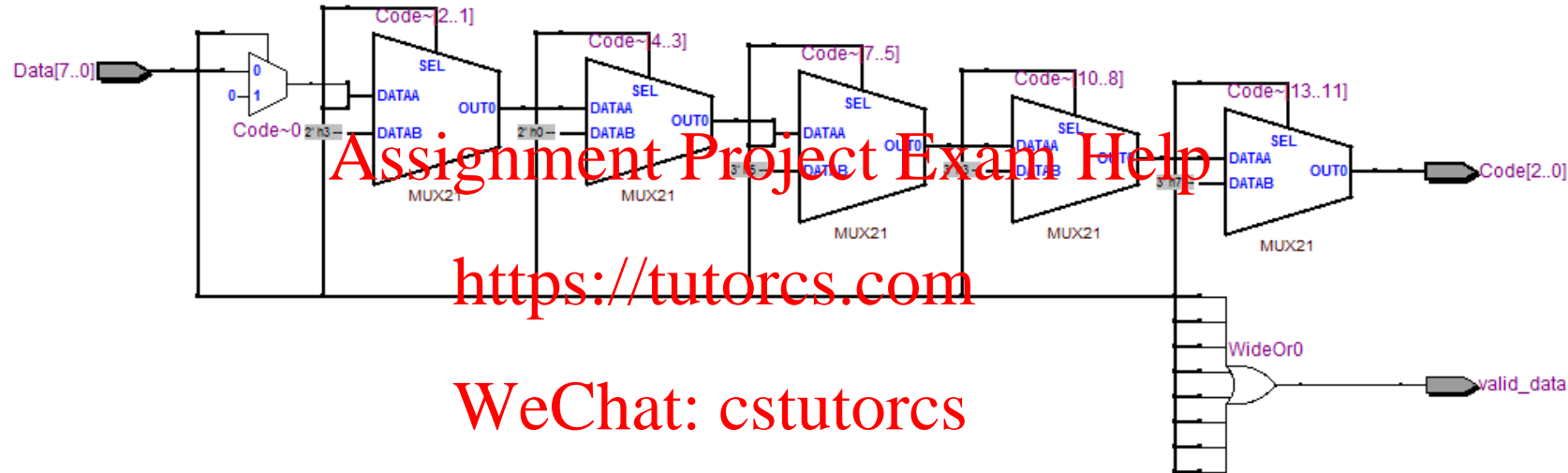

Assignment Project Exam Help


<https://tutorcs.com>

WeChat: cstutorcs

Flow Summary

Flow Status	Successful - Mon Oct 10 11:15:50 2011
Quartus II 64-Bit Version	11.0 Build 208 07/03/2011 SP 1 SJ Full Version
Revision Name	PEnc_8_to_3_if
Top-level Entity Name	PEnc_8_to_3_if
Family	Cyclone II
Device	EP2C35F672C6
Timing Models	Final
Total logic elements	7 / 33,216 (< 1 %)
Total combinational functions	7 / 33,216 (< 1 %)
Dedicated logic registers	0 / 33,216 (0 %)
Total registers	0
Total pins	12 / 475 (3 %)
Total virtual pins	0
Total memory bits	0 / 483,840 (0 %)
Embedded Multiplier 9-bit elements	0 / 70 (0 %)
Total PLLs	0 / 4 (0 %)

Simulation Results

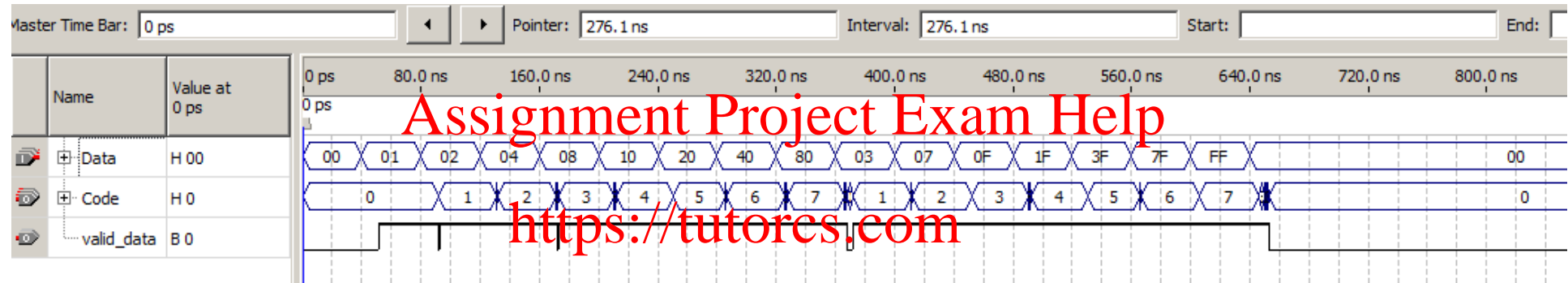

Assignment Project Exam Help

<https://tutores.com>

WeChat: cstutorcs