

Digital Systems Design

Assignment Project Exam Help


<https://tutorcs.com>

WeChat: cstutorcs


Asynchronous inputs
and Synchronisers

Asynchronous Inputs and Races

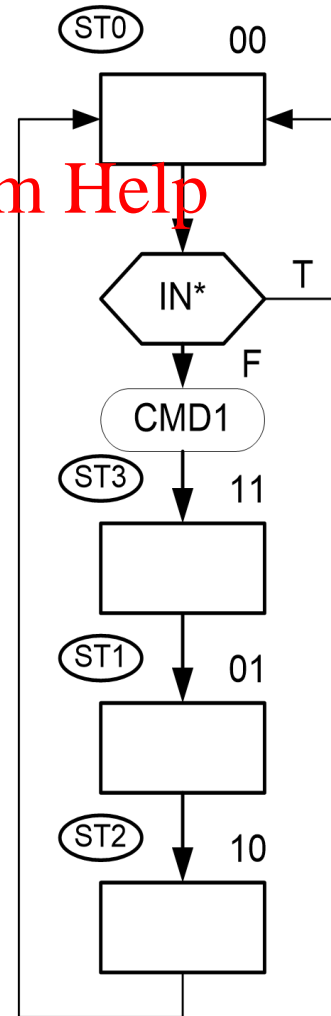- The timing changes of inputs occurring from sources outside our digital circuit are beyond our control.
- Such inputs are asynchronous and they are indicated by adding an asterisk * to their variable name.
- Consider the following:




Process Model

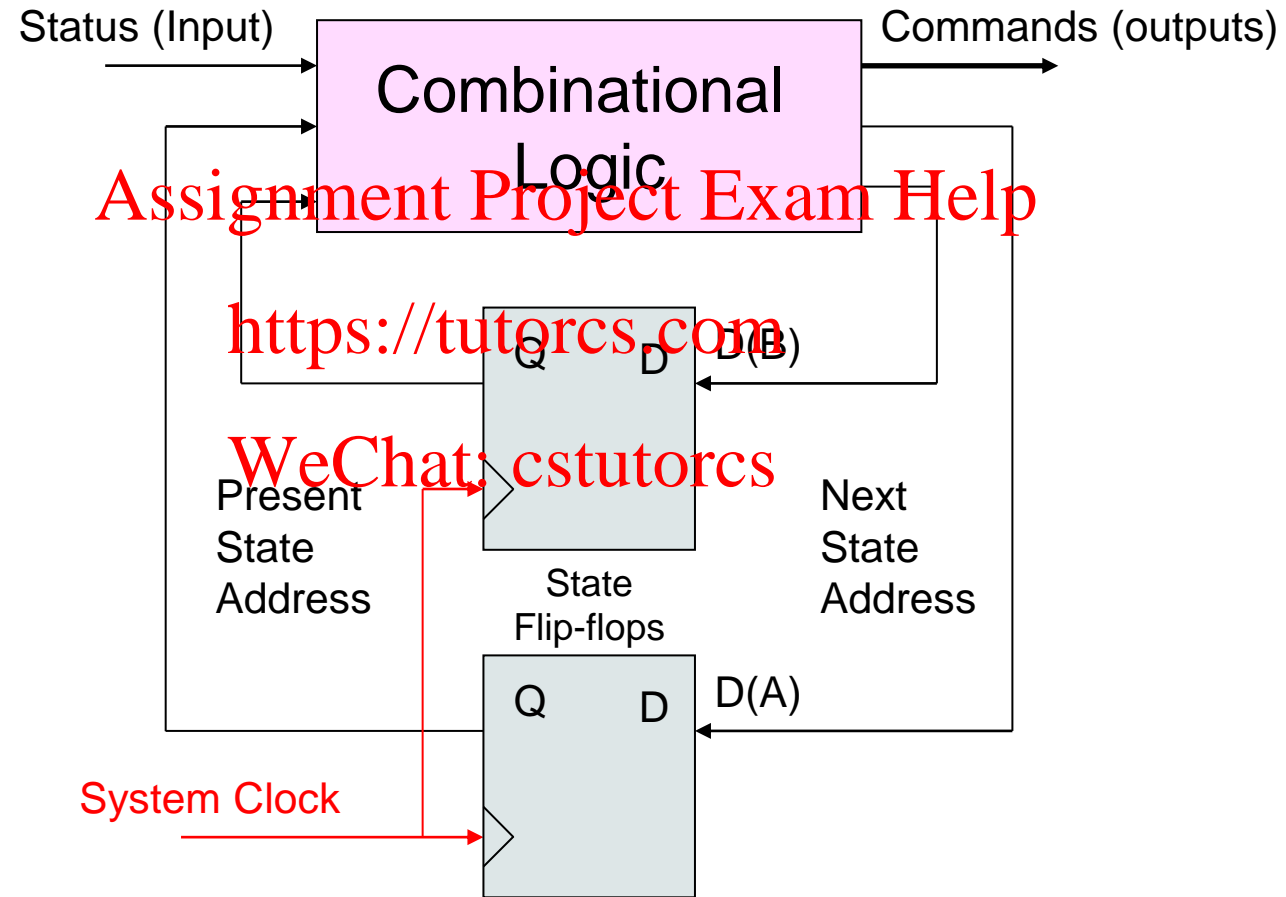


Setup and Hold Times for D Flip-flops

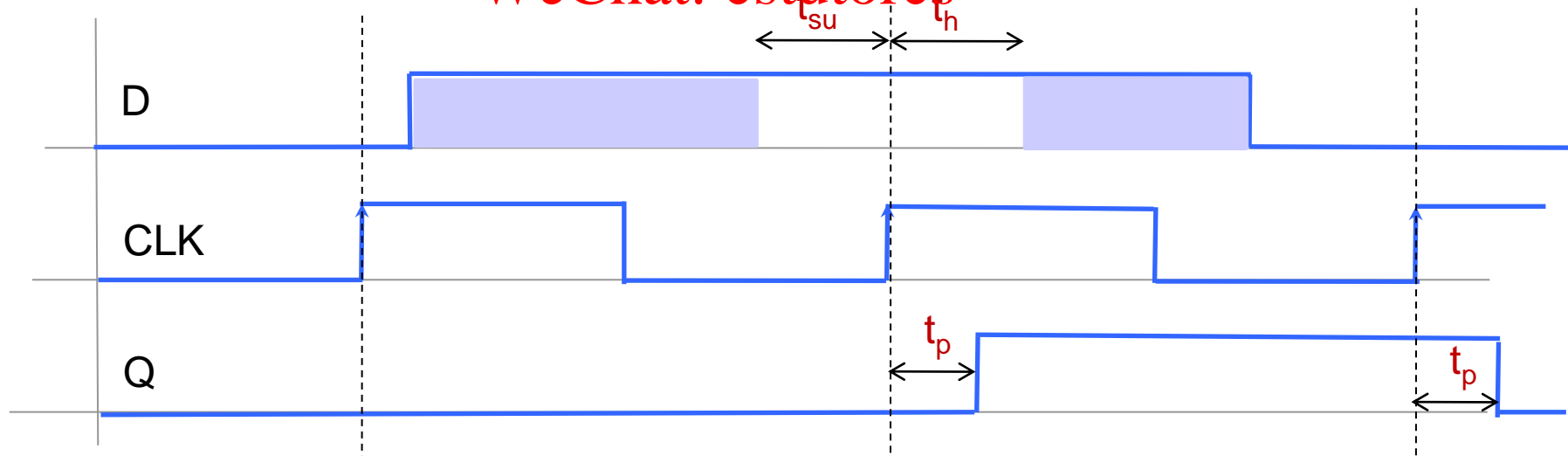- For the proper function of the edge triggered FF
 - D input must be stable for t_{su} time (setup time) before the active edge of the clock.
 - D input must be stable for t_h time (hold time) after the active edge of the clock.




Asynchronous Inputs and Races cont.

- Each bistable requires that its' input be stable for a few nanoseconds prior to the clock edge.
 - If the input changes during the *set-up time* the value of the bistable's output after the clock edge will be unpredictable.
 - i.e. after settling, the output will be either a T or F value, but which is uncertain.
 - If we assume that we are in ST0 and $IN^* = T$, then the inputs to both state bistables is F and the system is preparing to move to ST0. If $IN^* = F$ then the inputs to the bistables will be 11 in preparation to move to ST3.
- However if we have a transition in IN^* during the bistable set-up time or hold time we cannot predict their output.
- The next state could become ST0, ST1, ST2 or ST3.
 - The situation where the next state depends on the exact timing of the bistable input changes, is called a *transition race*.

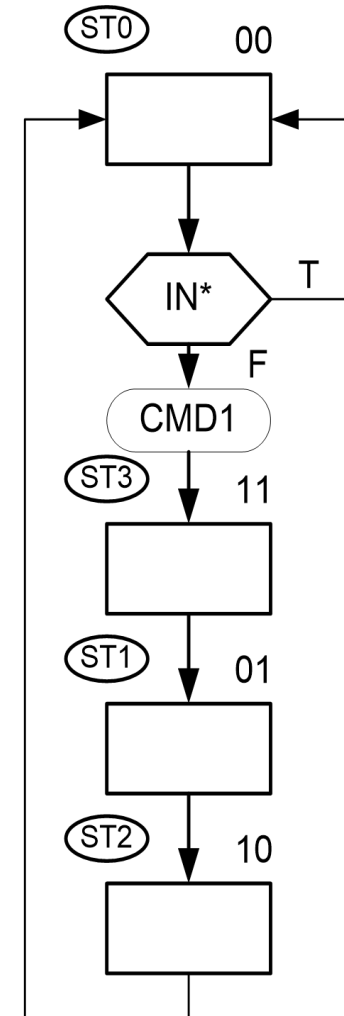


Output Races


- Examining the conditional output CMD1 when IN^* changes (ignoring transition races).
- In state ST0, when IN^* is T, CMD1 is F, whilst when IN^* is F, CMD1 is T.
- A change in IN^* causes an immediate change to CMD1.
- If IN^* changes from T to F in state ST0 time, the output CMD1 will be T for only a short period of the clock time, before the system moves to state ST3.
- This problem can be serious as the output CMD1 may cause problems if it is too short.

 

Output Races cont.

 

 
- This problem is called an *output race* and is the direct result of an ASM output being conditional on an asynchronous input.
- You would only get this problem in **Mealy machines** as in Moore machines the output is only a function of the current state.



Avoiding Races

- There is no way to avoid **output races**, except to avoid conditional outputs that depend on asynchronous inputs.
- We eliminate problems caused by asynchronous inputs by **synchronising** the inputs using a 'D' type flip-flop clocked by the system **block**.
<https://tutorcs.com>
- The ASM uses the **output of the flip-flop** and, as the output changes synchronously with the clock, there will never be a race in the ASM caused by that input.
WeChat: cstutorcs
- Many useful synchronous IC's have asynchronous inputs for setting, clearing or loading.
- The only routine use of asynchronous inputs is a **master clear signal** to be used when power is first applied or when the system 'hangs up'.

Synchroniser Flip-Flop

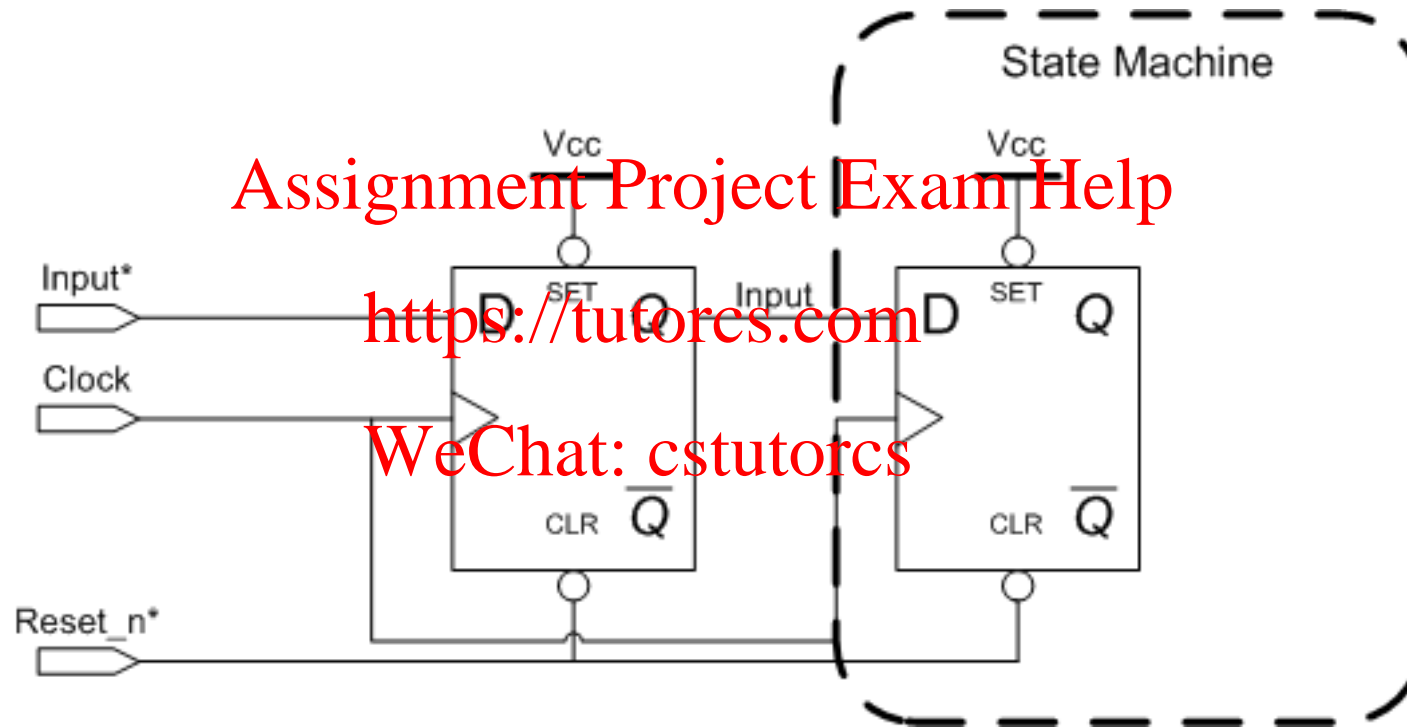

Note that the state machine will now detect the asynchronous “Input*” up to **one clock cycle later** as it is “**delayed**” by the Synchronising D-Type flip-flop.

Do the Asynchronous inputs cause problems in these ASMs?

