

# Digital System Design

## ELEC373/473

Assignment Project Exam Help



<https://tutorcs.com>

WeChat: cstutorcs

Verilog Four-Value Logic  
(HDLs)

# Four-Value Logic

- In Verilog a single bit can have one of four values

- **0** Numeric 0, logical FALSE
- **1** Numeric 1, logical TRUE
- **x** Unknown or ambiguous value
- **z** No value (high impedance)

Assignment Project Exam Help

<https://tutorcs.com>

- Why **x**?


WeChat: cstutorcs

- Could be multiple drivers conflicting on a wire. Strong signals cause short circuit and weak signals cause unexpected results.
- Could be lack of initialization
- In reality there is no 'x' value for a signal, just **0**, **1**, and **z**.


- Why **z**?

- Nothing driving the signal (Tri-states)


# Resolving 4-Value Logic

 


A	B	OUT
0	0	
0	1	
1	1	
0	x	
0	z	
1	x	
1	z	

 

A	B	OUT
0	0	
0	1	
1	1	
0	x	
0	z	
1	x	
1	z	

 

S	A	T	B	OUT
0	0		z	
0	1		x	
0	x		1	
0	z		0	
1	0		1	
1	0		z	
1	1		z	
1	x		z	
1	z		0	

 


A	0	1	x	z
OUT				

Assignment Project Exam Help


<https://tutorcs.com>

WeChat: cstutorcs


# Resolving 4-Value Logic

 


A	B	OUT
0	0	
0	1	
1	1	
0	x	
0	z	
1	x	
1	z	

 

A	B	OUT
0	0	
0	1	
1	1	
0	x	
0	z	
1	x	
1	z	

 

S	A	T	B	OUT
0	0			
0	1			
0	x			
0	z			
1	0			
1	1			
1	x			
1	z			

 


A	0	1	x	z
OUT	1	0	x	x

Assignment Project Exam Help


<https://tutorcs.com>

WeChat: cstutorcs


# Resolving 4-Value Logic

 


A	B	OUT
0	0	0
0	1	1
1	1	1
0	x	x
0	z	x
1	x	1
1	z	1

 

A	B	OUT
0	0	0
0	1	0
1	1	1
0	x	0
0	z	0
1	x	0
1	z	0

 

S	A	T	B	OUT
0	0			
0	1			
0	x			
0	z			
1	0			
1	0			
1	1			
1	x			
1	z			

 


A	0	1	x	z
OUT	1	0	x	x

Assignment Project Exam Help


<https://tutorcs.com>

WeChat: cstutorcs


# Resolving 4-Value Logic

 


A	B	OUT
0	0	0
0	1	1
1	1	1
0	x	x
0	z	x
1	x	1
1	z	1

 

A	B	OUT
0	0	0
0	1	0
1	1	1
0	x	0
0	z	0
1	x	x
1	z	x

 

S	A	T	B	OUT
0	0		z	
0	1		x	
0	x		1	
0	z		0	
1	0		1	
1	0		z	
1	1		z	
1	x		z	
1	z		0	

 


A	0	1	x	z
OUT	1	0	x	x

Assignment Project Exam Help


<https://tutorcs.com>

WeChat: cstutorcs


# Resolving 4-Value Logic

 


A	B	OUT
0	0	0
0	1	1
1	1	1
0	x	x
0	z	x
1	x	1
1	z	1

 

A	B	OUT
0	0	0
0	1	0
1	1	1
0	x	0
0	z	0
1	x	x
1	z	x

 

S	A	T	B	OUT
0	0	z	z	
0	1	z	x	
0	x	z	1	
0	z	z	0	
1	0	0	1	
1	0	0	z	
1	1	1	z	
1	x	x	z	
1	z	x	0	

 


A	0	1	x	z
OUT	1	0	x	x

Assignment Project Exam Help


<https://tutorcs.com>

WeChat: cstutorcs


# Resolving 4-Value Logic

 


A	B	OUT
0	0	0
0	1	1
1	1	1
0	x	x
0	z	x
1	x	1
1	z	1

 

A	B	OUT
0	0	0
0	1	0
1	1	1
0	x	0
0	z	0
1	x	x
1	z	x

 

S	A	T	B	OUT
0	0	z	z	z
0	1	z	x	x
0	x	z	1	1
0	z	z	0	0
1	0	0	1	x
1	0	0	z	0
1	1	1	z	1
1	x	x	z	x
1	z	x	0	x

 

A	0	1	x	z
OUT	1	0	x	x

Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs



# Verilog Primitives

Table 31—Built-in gates and switches

n_input gates	n_output gates	three-state gates	pull gates	MOS switches	bidirectional switches
and	buf	bufif0	pulldown	nmos	rtran
nand	not	bufif1	pullup	nmos	rtranif0
nor		notif0		pmos	rtranif1
or		notif1		rcmos	tran
xnor				rnmos	tranif0
xor				rpmos	tranif1


- The first three columns of primitives are supported by Quartus package.
- *MOS switches, bidirectional switches, and pull gates* are not supported by Quartus.

# Three-State Gates

		Control						Control					
		<b>bufif0</b>	0	1	x	z			<b>notif1</b>	0	1	x	z
<i>i</i> <i>n</i> <i>p</i> <i>u</i> <i>t</i>	0						<i>i</i> <i>n</i> <i>p</i> <i>u</i> <i>t</i>	0					
	1							1					
	x							x					
	z							z					

Assignment Project Exam Help



<https://tutorcs.com>

 

L means 0 or z  
H means 1 or z

# Three-State Gates (Tri-State Gates)



Control						Control							
		bufif0	0	1	x	z			notif1	0	1	x	z
input	0	0	z	L	L		input	0					
	1	1	z	H	H			1					
	x	x	z	x	x			x					
	z	x	z	x	x			z					

  

L means 0 or z  
H means 1 or z

# Three-State Gates

Control						Control							
		bufif0	0	1	x	z			notif1	0	1	x	z
input	0	0	z	L	L		input	0	z	1	H	H	
	1	1	z	H	H			1	z	0	L	L	
	x	x	z	x	x			x	z	x	x	x	
	z	x	z	x	x			z	z	x	x	x	

  

L means 0 or z  
H means 1 or z