

Digital Systems Design

ELEC373/473

Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs

Synthesis Tips

Extracted from Verilog HDL by M.D. Ciletti

Exploiting Logical Don't-Cares in Synthesis

- The absence of a “**default**” assignment in “case” statements, and incomplete “if” statements will cause latches to be instantiated by a synthesis tool. (Example 1)


WeChat: cstutorcs

Example 1 – Counter & Seven segment decoder

```
1  module Latched_Seven_Seg_Display
2      (Display_L, Display_R, Blanking, Enable, reset, clock);
3
4      output [6:0] Display_L, Display_R;
5      input  Blanking, Enable, reset, clock;
6      reg [6:0] Display_L, Display_R;
7      reg [3:0] count;
8
9      parameter BLANK = 7'b111_1111;
10     parameter ZERO = 7'b000_0001;
11     parameter ONE = 7'b100_1111;
12     parameter TWO = 7'b001_0010;
13     parameter THREE = 7'b000_0110;
14     parameter FOUR = 7'b100_1100;
15     parameter FIVE = 7'b010_0100;
16     parameter SIX = 7'b010_0000;
17     parameter SEVEN = 7'b000_1111;
18     parameter EIGHT = 7'b000_0000;
19     parameter NINE = 7'b000_0100;
```

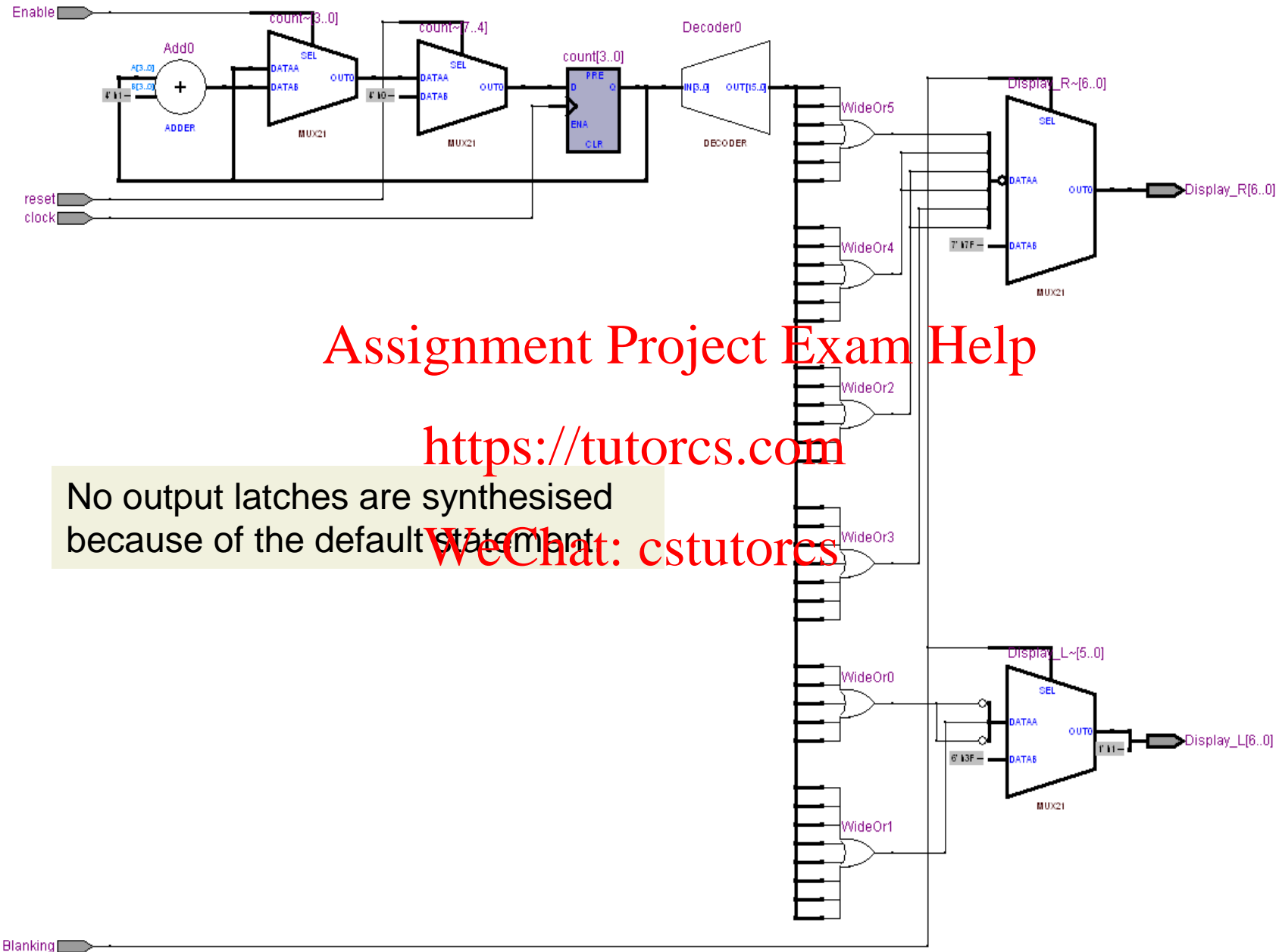Example 1 (cont.)

```
20
21 always @ (posedge clock)
22     if (reset) count<= 0; else if (Enable) count<= count +1;
23 always @ (count or Blanking)
24     if ( Blanking) begin Display_L= BLANK; Display_R= BLANK; end else
25     case (count)
26         0:      begin Display_L= ZERO; Display_R = ZERO;      end
27         2:      begin Display_L= ZERO; Display_R = TWO;      end
28         4:      begin Display_L= ZERO; Display_R = FOUR;      end
29         6:      begin Display_L= ZERO; Display_R = SIX;      end
30         8:      begin Display_L= ZERO; Display_R = EIGHT;     end
31         10:     begin Display_L= ONE; Display_R = ZERO;      end
32         12:     begin Display_L= ONE; Display_R = TWO;      end
33         14:     begin Display_L= ONE; Display_R = FOUR;      end
34         // By removing the default statement 14 latches will be synthesised
35         default begin Display_L= BLANK; Display_R= BLANK; end
36     endcase
37 endmodule
38
```



Assignment Project Exam Help

<https://tutorcs.com>

No output latches are synthesised
because of the default statement.

WeChat: cstutorcs

Don't cares & Tri-State Outputs

- An assignment to “**x**” in a “**case**” or an “**if**” assignment will be treated as a don't-care condition in synthesis. This will be used in logic minimisation. (Example 2)

Assignment Project Exam Help

- If a conditional operator assigns the value “**z**” to the right hand side expression of a continuous assignment in a level sensitive behaviour, the statement will synthesise to a three-state device driven by combinational logic. (Example 2)

<https://tutorcs.com>

WeChat: cstutorcs


Example 2

```
1 module alu_with_z (alu_out, data_a, data_b, enable, opcode);
2
3     input      [2:0]    opcode;
4     input      [3:0]    data_a, data_b;
5     input      enable;
6     output     [3:0]    alu_out;
7
8     reg        [3:0]    alu_reg;
9
10    // Three-state buffers are generated
11    assign alu_out = (enable == 1) ? alu_reg : 4'bz;
12
13    always @ (opcode or data_a or data_b)
14    = case (opcode)
15        3'b001:    alu_reg= data_a | data_b;
16        3'b010:    alu_reg= data_a ^ data_b;
17        3'b110:    alu_reg= ~ data_b;
18        //default:  alu_reg= 4'b0;
19        //with unconstrained default less hardware is generated
20        default:    alu_reg= 4'bx;
21    endcase
22 endmodule
```


Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs

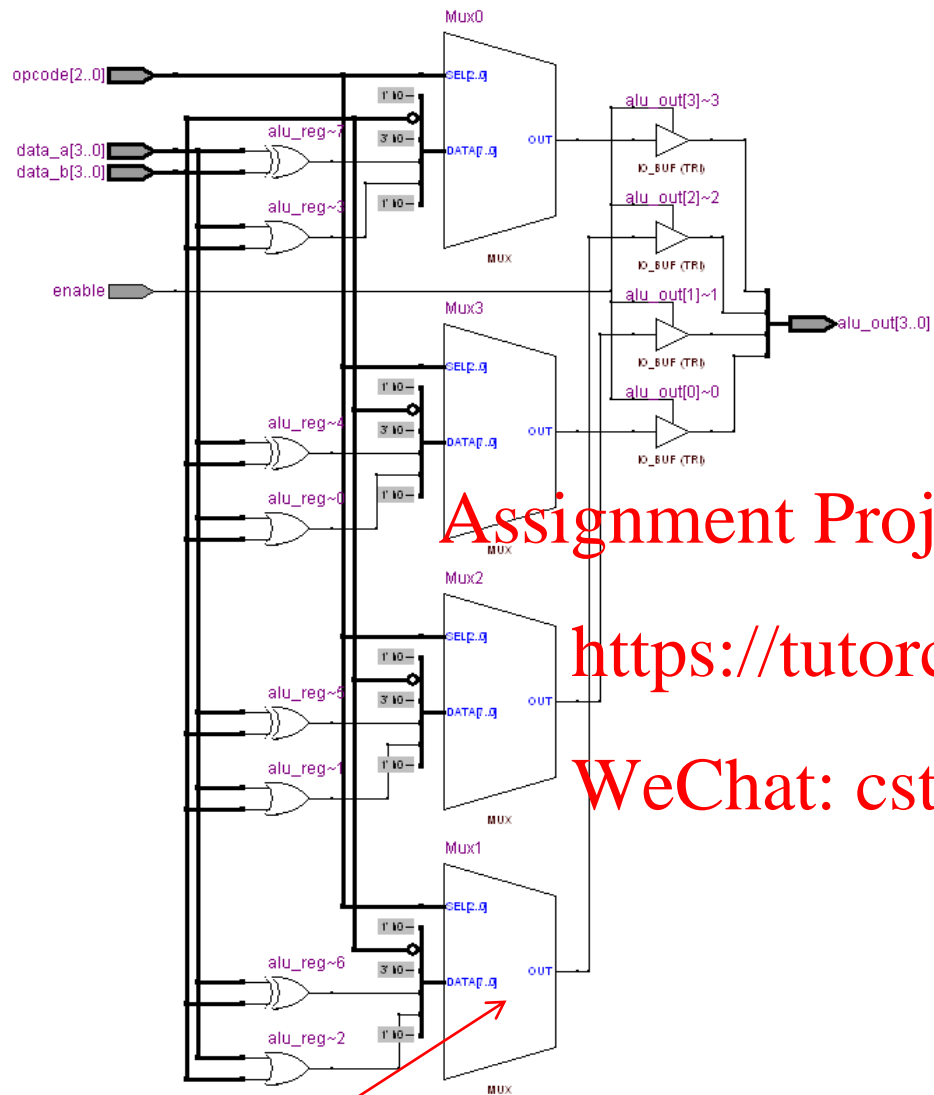

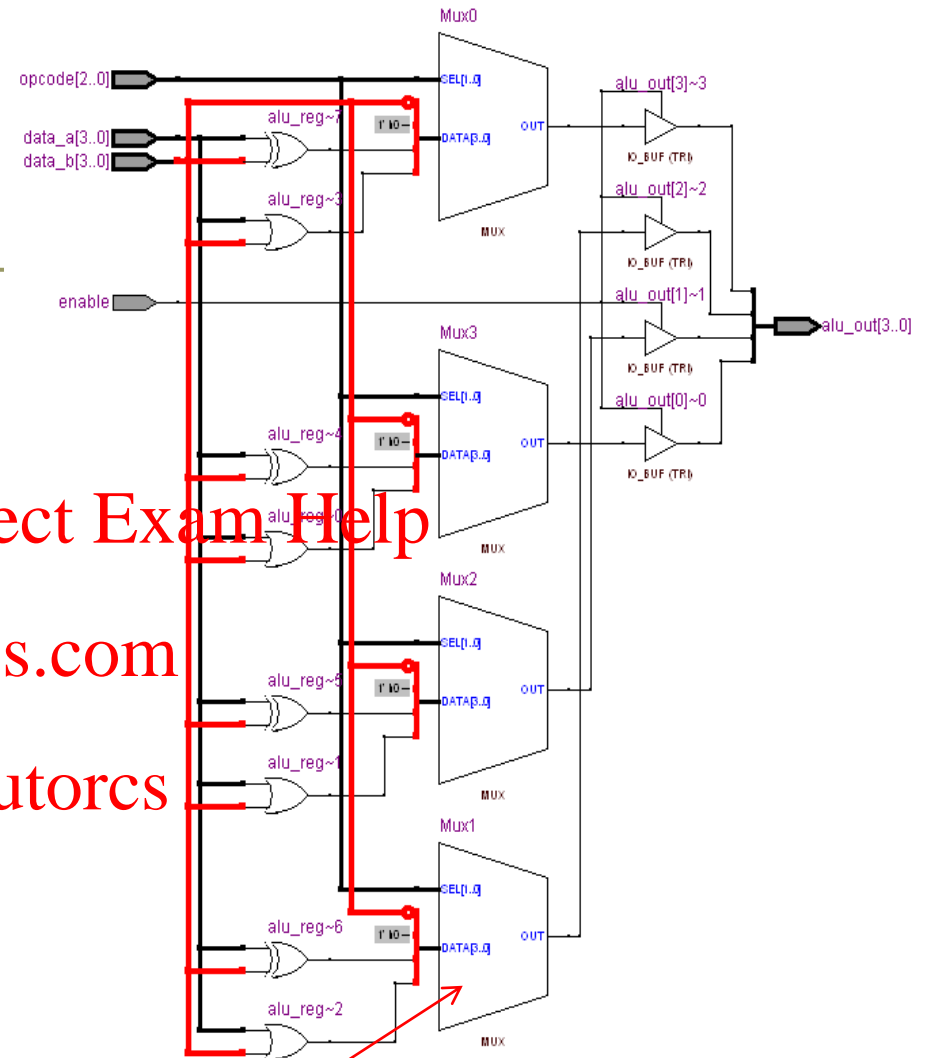Constrained default assignment has used **8-1 multiplexer** blocks for synthesis. **8 Logic Elements** of a Cyclone II device will be used.



Unconstrained default assignment has used **4-1 multiplexer** blocks for synthesis. **4 Logic Elements** of a Cyclone II device will be used.

Assignment Project Exam Help

<https://tutorcs.com>


WeChat: cstutorcs

Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs

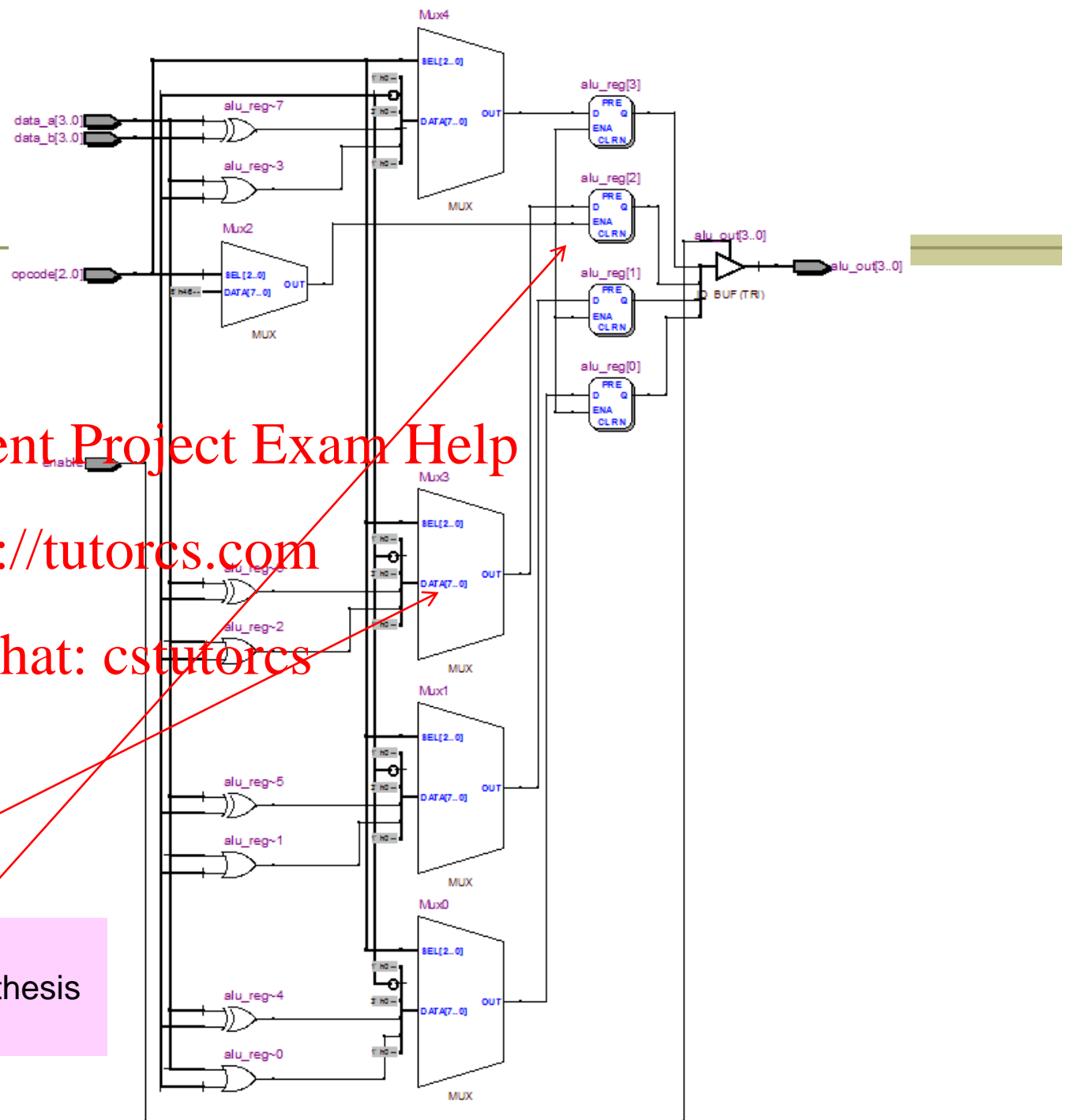With no default assignment has used **8-1 multiplexer** blocks for synthesis and also synthesised latches.



Resource Sharing

- A synthesis tool must recognise whether the physical resources required to implement complex behaviours (e.g. Adders) can be shared.
 - If the data flows within a behaviour do not conflict, the resource can be shared between one or more paths.
- Assignment Project Exam Help

```


module res_share (y_out, sel, data_a, data_b, data_c);
    output [4:0] y_out;
    input [3:0] data_a, data_b, data_c;
    input sel;

    // The synthesis tool couldn't detect the resource sharing
    // assign y_out = sel ? (data_a + data_b) : (data_a + data_c);
    // Forced resource sharing
    assign y_out = data_a + (sel ? data_b : data_c);
endmodule

```

The important design trade off is that the **mux** will use significantly less resources than the adder that it replaces. (Depends on the Architecture)

Forced Resource Sharing

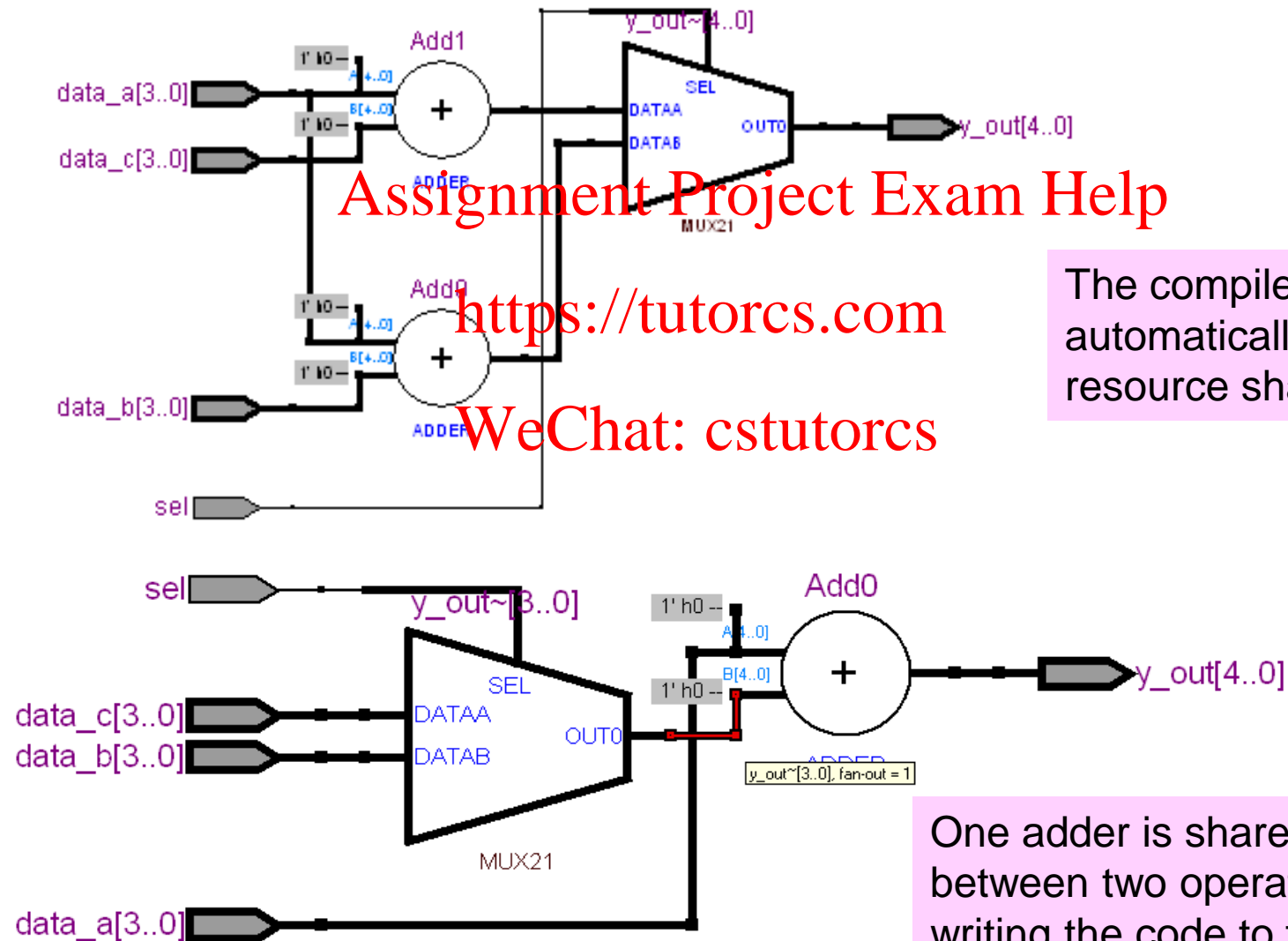

Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs

The compiler did not automatically implement resource sharing.

One adder is shared between two operations by writing the code to force it.

Synthesis of Sequential Logic with Latches

- A set of feedback-free continuous assignments will synthesise into latch free combinational logic.

Assignment Project Exam Help

- A continuous assignment using a conditional operator with feedback will synthesise into a latch

<https://tutorcs.com>

```
assign data_out = ( CS_b ==0) ? (WE_b ==0) ? data_in : data_out : 1'bz;
```

WeChat: cstutorcs

This is better written as

```
assign data_out = ( CS_b ==0) ? ((WE_b ==0) ? data_in : data_out ) : 1'bz;
```

The above assignment synthesises an SRAM cell




Accidental Synthesis of Latches

- A Verilog description of combinational logic must assign values to the outputs for all possible values of the inputs.
- The event control expression must be sensitive to all the inputs otherwise unintentional latches are synthesised.

```
module or4_behav (y, x_in);  
    output y;  
    input [3:0] x_in;  
    reg y;  
    integer k;  
    always @ (x_in) // Only a 4-input OR gate is synthesised  
    // always @ (x_in [3:1]) // If x_in[0] input is excluded from the sensitivity list of the  
    // cyclic behaviour an unintentional latch for x_in[0] is synthesised too.  
    begin: check_for_1  
        y=0;  
        for (k = 0; k <= 3; k = k+1)  
            if (x_in[k] ==1 )  
                begin y=1; disable check_for_1; end  
    end  
endmodule
```

Synthesised Circuits

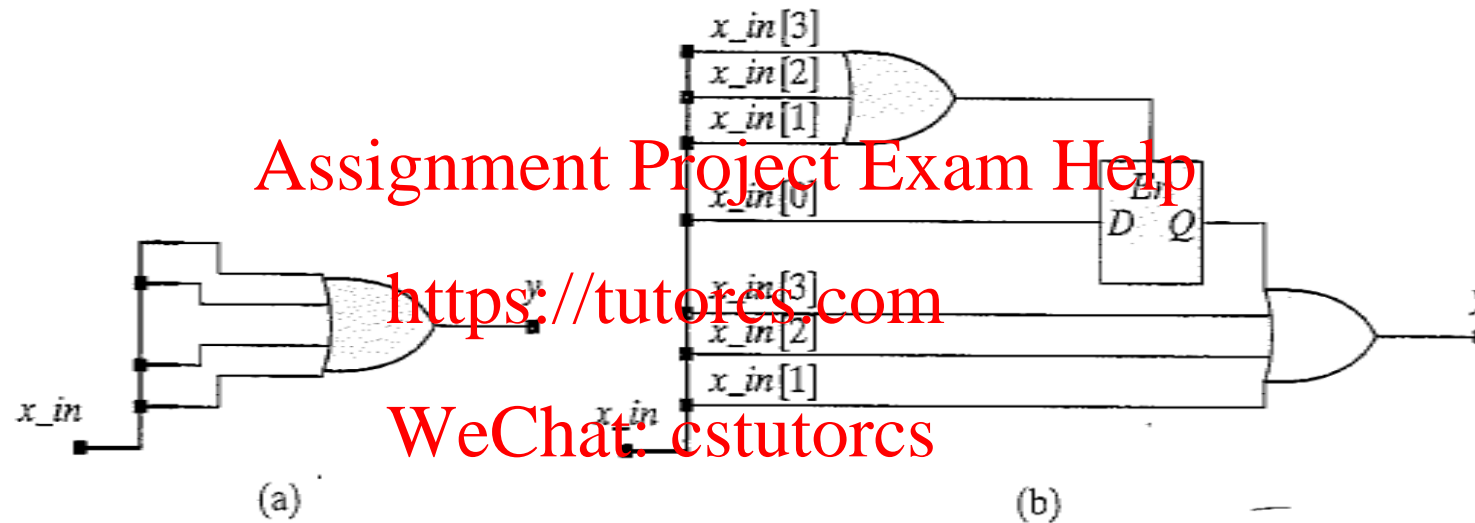

- (a) Circuit synthesised from a level-sensitive cyclic behaviour
- (b) Circuit synthesised from a latch-inducing model

Note: Quartus will actually synthesise circuit (a) for either definition. However not all synthesisers behave the same.


Intentional Synthesis of Latches

- An **if** statement in a level-sensitive behaviour will synthesise to a latch if the statement assigns value to a **register variable** in some, but not all, branches (i.e. the statement is incomplete).

<https://tutorcs.com>
WeChat: tutorcs

```
module latch_if2 (data_out, data_in, latch_enable);  
    output [3:0] data_out;  
    input [3:0] data_in;  
    input latch_enable;  
    reg [3:0] data_out;  
  
    always @ (latch_enable or data_in)  
        if (latch_enable) data_out = data_in; // incompletely specified  
endmodule
```


Synthesised Circuit

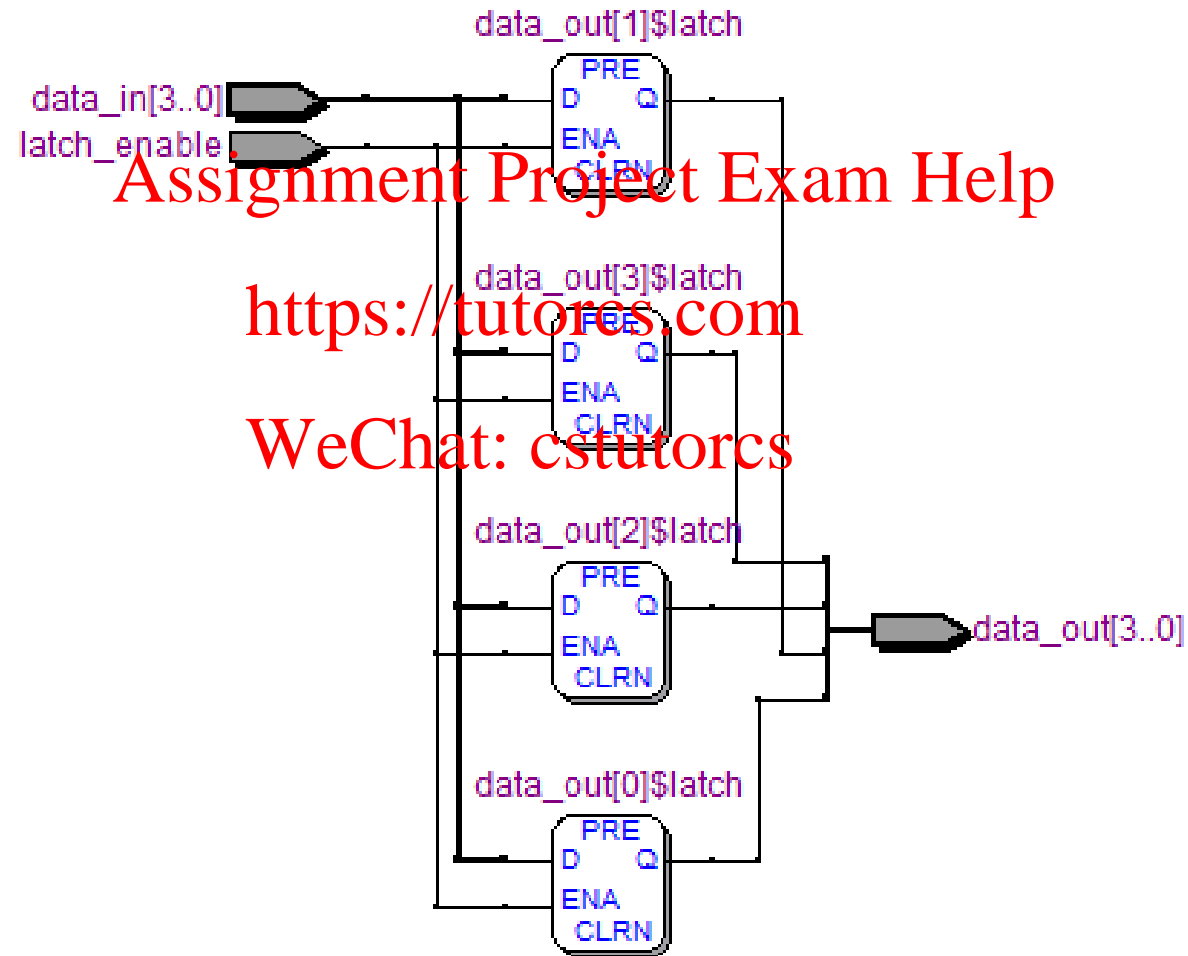

Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs

Synthesis of Loops

- In **static** or **data-independent** loops the number of iterations can be determined by the compiler before simulation.

Assignment Project Exam Help


- In **nonstatic** loops the number of iterations depends on some variable during operation.

<https://tutorcs.com>

WeChat: cstutorcs


- In addition to having a dependency on data, a loop may have a dependency on embedded timing controls.
- Nonstatic loops that do not have internal timing controls are not synthesisable by some tools.

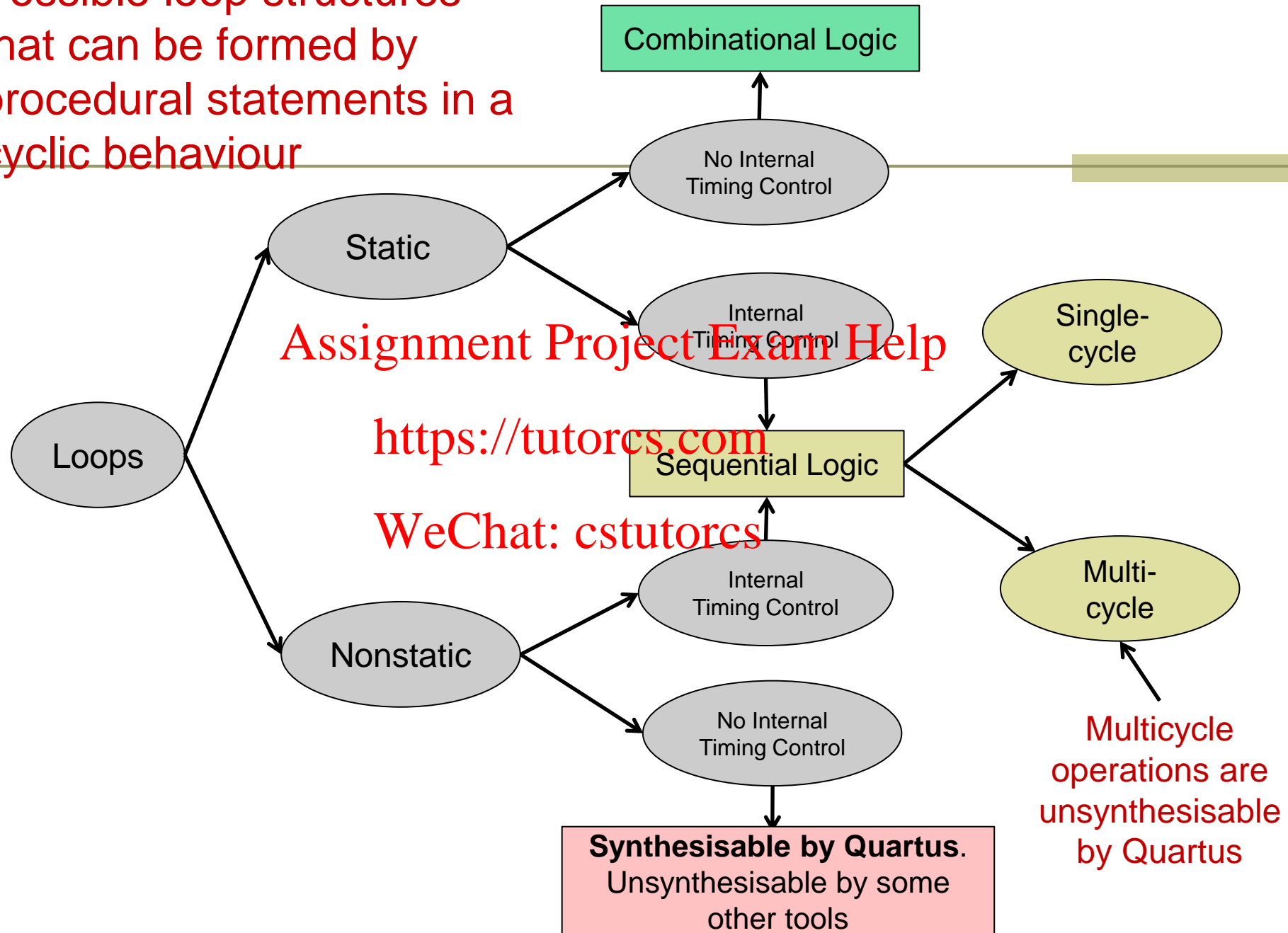Possible loop structures
that can be formed by
procedural statements in a
cyclic behaviour



Static Loops without Embedded Timing Controls
 
```
module for_and_loop_com (out, a,b);  
    output    [3:0]    out;  
    input     [3:0]    a, b;  
    reg       [2:0]    i;  
    reg       [3:0]    out;  
    wire      [3:0]    a, b;  
    always @ (a or b)  
        begin  
            for (i=0; i<=3; i=i+1)  
                out[i] = a[i] & b[i];  
        end  
endmodule
```



The loop does not depend on the data and does not have embedded event controls. Therefore it produces combinational logic.

Example for the next sections

- The following examples all aim to count the number of 1's in a word received in a parallel data format.

Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs

Example count_ones_a

```
1  module count_ones_a( bit_count, data, clk, reset);
2      parameter          data_width = 4;
3      parameter          count_width = 3;
4
5      output  [count_width -1 : 0]  bit_count;
6      input   [data_width -1 : 0]    data;
7      input   clk, reset;
8
9      reg     [count_width -1 : 0]    count;
10     reg     [count_width -1 : 0]    index;
11     reg     [data_width - 1 : 0]    temp;
12
13     always @ (posedge clk)
14         if (reset) begin count = 0; bit_count = 0; end
15         else
16             begin
17                 count = 0;
18                 bit_count = 0;
19                 temp = data;
20                 for ( index = 0; index <= data_width; index = index +1)
21                     begin
22                         count = count + temp[0];
23                         temp = temp >>1;
24                     end
25                 bit_count = count;
26             end
27     endmodule
```

Assignment Project Exam Help


<https://tutorcs.com>

WeChat: cstutorcs

Notes on count_ones_a

- The contents of the register variables index and temp do not have a lifetime outside the cyclic behaviour in which they are assigned a value.
 - Both variables are eliminated by the synthesis tool.
- The only synthesised register is bit_count.
 - Signal bit_count is registered because its value is assigned with an edge sensitive cyclic behaviour. bit_count is also an output port.

WeChat: cstutorcs

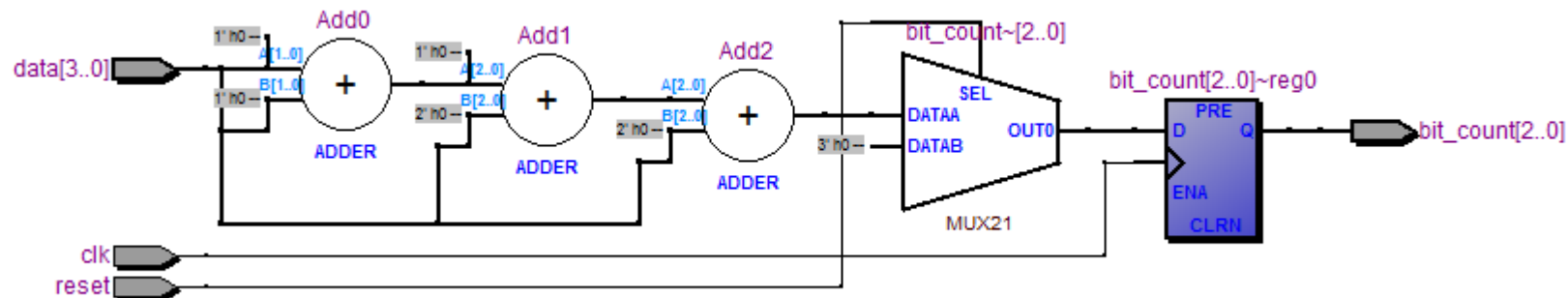

Static Loops with Embedded Timing Controls

```
module count_ones_b2 ( bit_count, data, clk, reset);  
    parameter data_width = 4;  
    parameter count_width = 3;  
    output [count_width - 1 : 0] bit_count;  
    input [data_width - 1 : 0] data;  
    input clk, reset;  
    reg [count_width - 1 : 0] count, bit_count;  
    reg [data_width - 1 : 0] temp;  
    integer index;  
    always begin : machine  
        for ( index = 0; index <= data_width; index = index + 1)  
            begin  
                @ (posedge clk) // embedded timing control  
                if (reset) begin bit_count = 0; disable machine; end  
                else if (index == 0) begin count = 0; bit_count = 0; temp = data; end  
                else if (index < data_width)  
                    begin count = count + temp[0]; temp = temp >> 1; end  
                else bit_count = count + temp[0];  
            end  
        end // machine  
    endmodule
```

Will not synthesise in Quartus: Multiple event control statements are not supported for synthesis

Nonstatic Loops without Embedded Timing Controls

```
module count_ones_c ( bit_count, data, clk, reset);  
    parameter data_width = 4;  
    parameter count_width = 3;  
    output [count_width -1 : 0] bit_count;  
    input [data_width - 1 : 0] data;  
    input clk, reset;  
    reg [count_width -1 : 0] count, bit_count, index;  
    reg [data_width - 1 : 0] temp;  
    always @ (posedge clk)  
        if (reset) begin count = 0; bit_count = 0; end  
        else begin  
            count = 0;    temp = data;  
            for ( index = 0; | temp; index = index +1) begin  
                if (temp[0]) count = count + 1;  
                temp = temp >>1;    end  
            bit_count = count;  
        end  
endmodule
```

Assignment Project Exam Help


<https://tutorcs.com>

WeChat: cstutorcs

This loop's length is data dependent but it was synthesised by Quartus II

Nonstatic Loops without Embedded Timing Controls

Simulation and RTL View

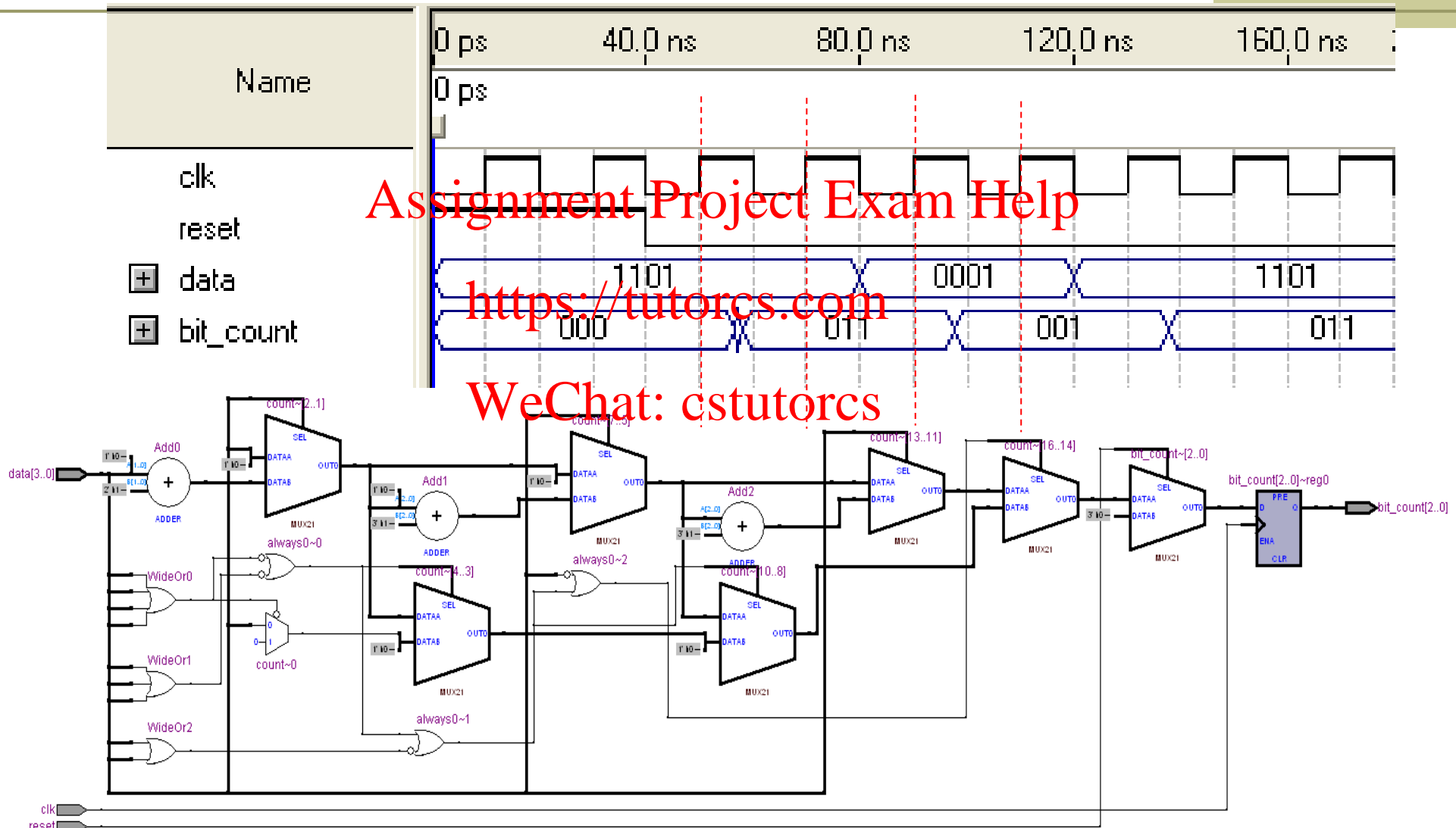

Nonstatic Loops with Embedded Timing Controls

```
module count_ones_d ( bit_count, data, clk, reset);  
  
    parameter data_width = 4;  
    parameter count_width = 3;  
  
    output [count_width - 1 : 0] bit_count;  
    input [data_width - 1 : 0] data;  
    input clk, reset;  
  
    reg [count_width - 1 : 0] count, bit_count;  
    reg [data_width - 1 : 0] temp;
```

Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs

always begin: *wrapper_for_synthesis*

@ (posedge clk)

if (reset) begin count = 0; bit_count = 0; **end**

else begin: *bit_counter*

count = 0;

temp = data;

while (temp) *// nonstatic loop with embedded timing control*

@ (posedge clk)

if (reset)

begin count = 0; **disable** bit_counter; **end**

else

begin count = count + temp [0]; temp = temp >>1; **end**

@ (posedge clk)

if (reset) begin count = 0; **disable** bit_counter; **end**

else bit_count = count;

end *// bit_counter*

// wrapper_for_synthesis

end

endmodule


Multiple event
control statements
are not supported
by Quartus

Assignment Project Exam Help

<https://tutorcs.com>


WeChat: cstutorcs

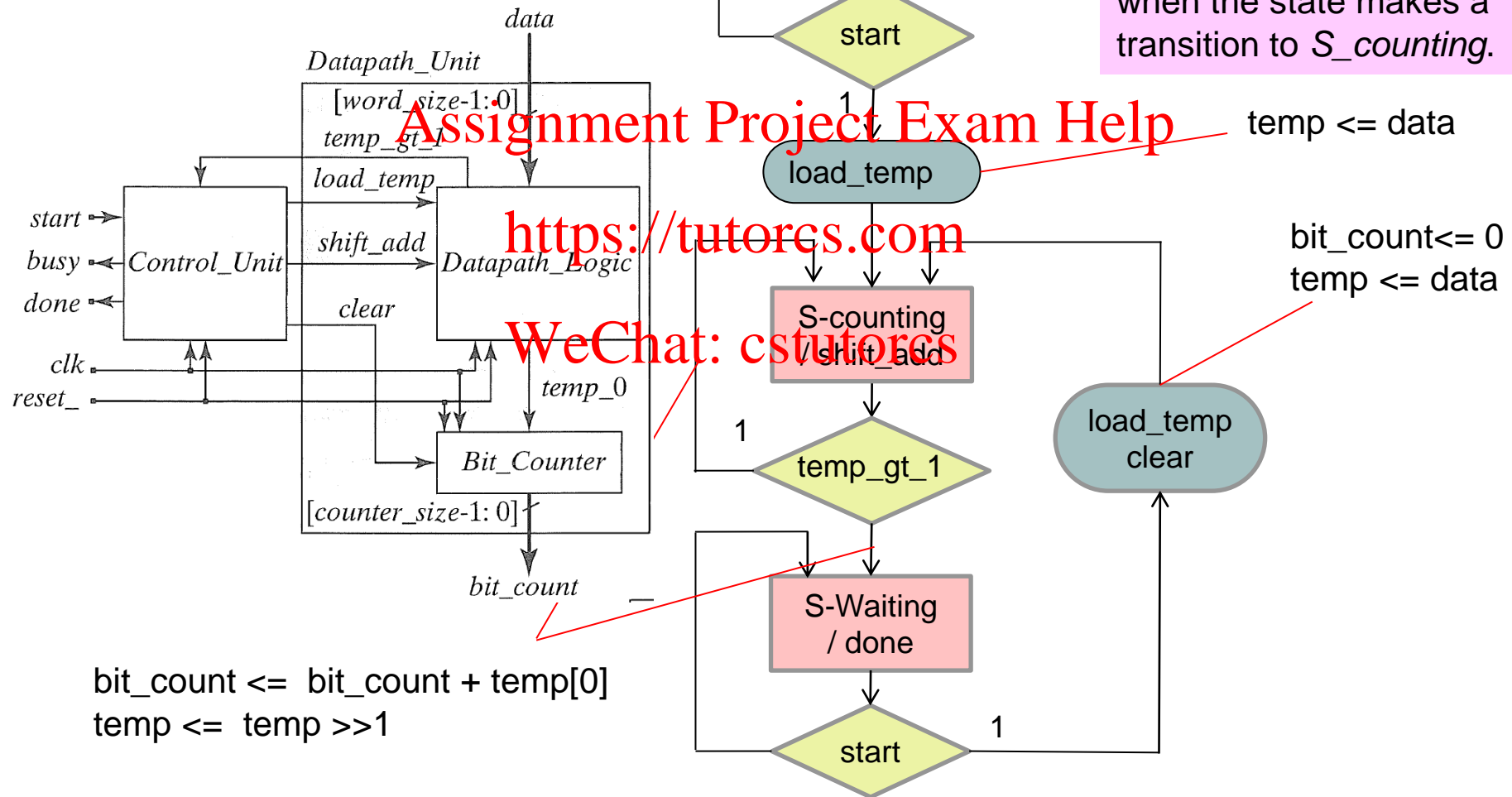ASMD replacement for unsynthesisable loops



Block Diagram of the Loop

Assignment Project Exam Help

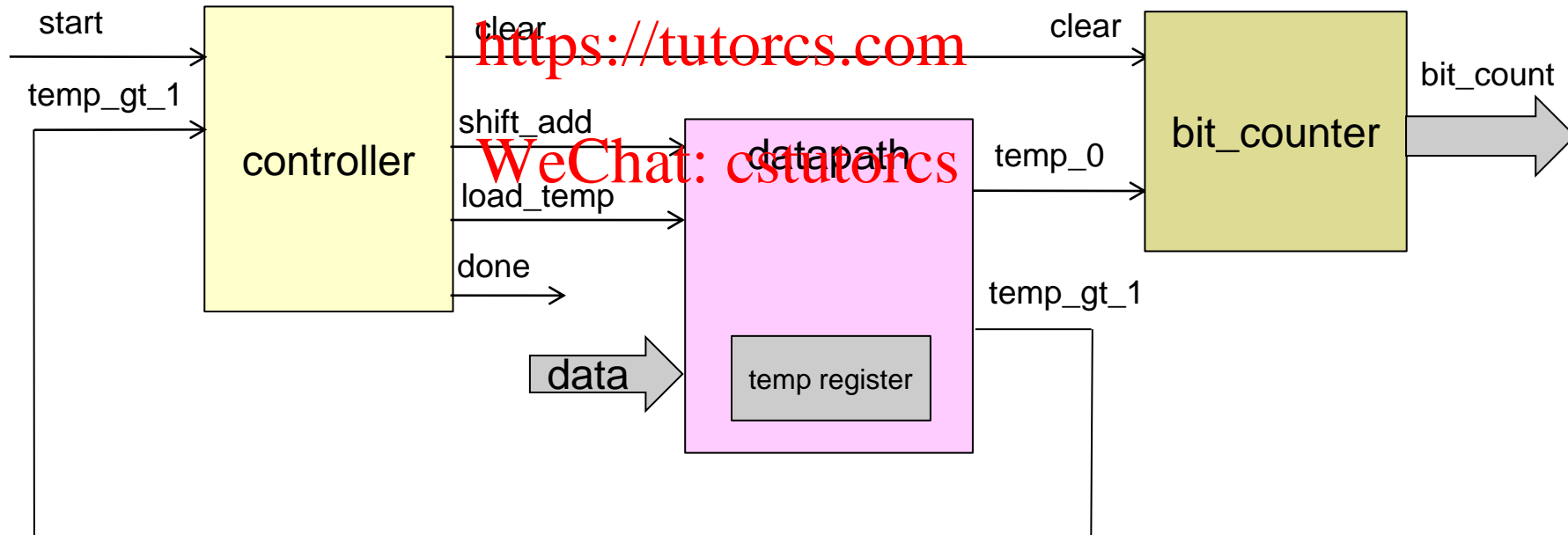

Verilog code

```
module count_ones_SM (bit_count, busy, done, data, start, clk, reset);
    parameter          word_size = 4;
    parameter          counter_size = 3;

    output              [counter_size-1:0]    bit_count;
    output              busy, done;
    input               [word_size-1: 0]      data;
    input               start, clk, reset;

    wire                load_temp, shift_add, clear;
    wire                temp_0, temp_gt_1;


    controller  M0  (load_temp, shift_add, clear, done, start, temp_gt-1, clk, reset);
    datapath    M1  (temp_gt_1, temp_0, data, load_temp, shift_add, clk, reset);
    bit_counter M2  (bit_count, temp_0, clear, clk, reset);
endmodule
```

Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs

Controller Module

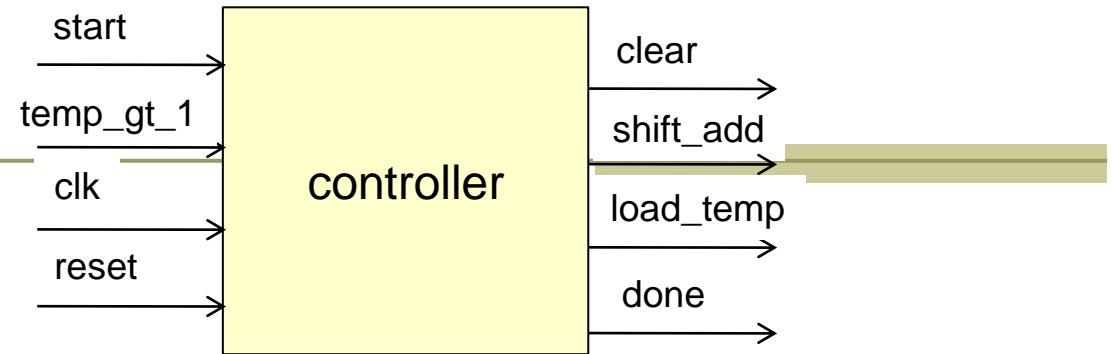

module *controller*
 (load_temp, shift_add, clear, done, start, temp_gt_1, clk, reset);

 parameter state_size = 2;
 parameter S_idle = 0;
 parameter S_counting = 1;
 parameter S_waiting = 2;

 output load_temp, shift_add, clear, done;
 input start, temp_gt_1, clk, reset;

 reg [state_size-1 : 0] state, next_state;
 reg load_temp, shift_add, done, clear;

Assignment Project Exam Help

<https://tutors.com>

WeChat: cstutorcs


```

always @ (posedge clk) // state transitions
    if (reset) state= S_idle; else state <= next_state ;
// next state cyclic behaviour
always @ ( state or start or temp_gt_1 ) begin
    load_temp = 0; shift_add = 0; done = 0;
    clear =0; next_state = S_idle;
    case (state)
        S_idle:      if ( start) begin next_state = S_counting;
                        load_temp = 1; end
        S_counting:  begin
                        shift_add =1;
                        if ( temp_gt_1) next_state = S_counting;
                        else next_state = S_waiting; end
        S_waiting:  begin
                        done =1;
                        if ( start) begin next_state = S_counting;
                                            load_temp=1; clear =1; end
                        else next_state = S_waiting;
                        end
        default:    begin clear =1; next_state = S_idle; end
    endcase
end
endmodule

```

Assignment Project Exam Help


<https://tutorcs.com>

WeChat: cstutorcs

Datapath Module

```
module datapath ( temp_gt_1, temp_0, data, load_temp, shift_add, clk, reset);  
    parameter word_size = 4;  
    output temp_gt_1, temp_0;  
    input load_temp, shift_add, clk, reset;  
    input [word_size-1 : 0] data;  
    reg [word_size-1 : 0] temp;  
    wire temp_gt_1 = (temp > 1);  
    wire temp_0 = temp[0];
```
 
```
    always @ (posedge clk)  
        if (reset) temp <= 0 ;  
        else begin  
            if (load_temp) temp <= data;  
            if (shift_add) temp <= (temp >> 1);  
        end  
endmodule
```




```

module bit_counter ( bit_count, temp_0, clear, clk, reset);
  parameter                                counter_size = 3;
  output      [ counter_size - 1 : 0]      bit_count;
  input        temp_0, clear, clk, reset;

  reg          [ counter_size - 1 : 0]      bit_count;

  always @ (posedge clk)
    if (reset || clear) bit_count <= 0 ;
    else                bit_count <= bit_count + temp_0;
endmodule

```

 

Annotated Simulation

Data is loaded into the temp register in the following clock cycle


It takes 4 clock cycles for calculation of the number of ones because the MSB of the data is 1

For the 0001 data it only takes one clock cycle because after the first shift the content of temp register becomes 0

Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs

 

Synthesising Loops

```
1 module Register_File (Data_out, Read_Addr_in, Shift_Enable, clk, reset_n);
2   parameter WIDTH = 8;
3   parameter DEPTH = 10;
4   output [WIDTH-1:0] Data_out;
5   input [($clog2(DEPTH))-1:0] Read_Addr_in;
6   input Shift_Enable, clk, reset_n;
7
8   reg [WIDTH-1:0] Reg_File [DEPTH-1:0]; // 8bit X 10 word memory
9
10  integer i;
11
12  // Read operation is independent of the clock pulse
13  assign Data_out = Reg_File [ Read_Addr_in ];
14
15  always @ (posedge clk, negedge reset_n)
16    if(reset_n == 0)
17      begin
18        for (i = 0; i <= DEPTH-1; i = i + 1)
19          Reg_File [i] <= i+1;
20        end
21      else if (reset_n == 1'b1 & Shift_Enable == 1'b1)
22        begin
23          for (i = Read_Addr_in; i <= (DEPTH-2); i = i + 1)
24            begin
25              if( i >= Read_Addr_in)
26                Reg_File [i] <= Reg_File [i+1];
27            end
28          Reg_File[DEPTH-1] <= {WIDTH{1'b1}};
29        end
30  endmodule
31
```

Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs

Type	ID	Message
	11104	Parallel Compilation has detected 24 hyper-threaded processors. However, the extra hyper-threaded processors will not be used by default. Parallel Compilatio
	12021	Found 1 design units, including 1 entities, in source file register_file.v
	12127	Elaborating entity "Register_File" for the top level hierarchy
	10230	Verilog HDL assignment warning at Register_File.v(19): truncated value with size 32 to match size of target (8)
	10119	Verilog HDL Loop Statement error at Register_File.v(23): loop with non-constant loop condition must terminate within 250 iterations
	12153	Can't elaborate top-level user hierarchy
		Quartus II 64-Bit Analysis & Synthesis was unsuccessful. 2 errors, 1 warning
	293001	Quartus II Full Compilation was unsuccessful. 4 errors, 1 warning

The error

■ The Error

- Loop with none constant loop condition must terminate within 250 iterations

Assignment Project Exam Help

■ The solution

<https://tutorcs.com>

- Change from

- For (i=variable; i<= variable; i = i+1)

WeChat: cstutorcs

- Do something

- To

- For (i=fixed; i<= fixed; i = i+1)

- If (i > variable) Do something

Revised Verilog code

```
1 module Register_File (Data_out, Read_Addr_in, Shift_Enable, clk, reset_n);
2     parameter WIDTH = 8;
3     parameter DEPTH = 10;
4     output [WIDTH-1:0] Data_out;
5     input [($clog2(DEPTH))-1:0] Read_Addr_in;
6     input Shift_Enable, clk, reset_n;
7
8     reg [WIDTH-1:0] Reg_File [DEPTH-1:0]; // 8bit X 10 word memory
9
10    integer i;
11
12    // Read operation is independent of the clock pulse
13    assign Data_out = Reg_File [ Read_Addr_in ];
14
15    always @ (posedge clk, negedge reset_n)
16        if(reset_n == 0)
17            begin
18                for (i = 0; i <= DEPTH-1; i = i + 1)
19                    Reg_File [i] <= i+1;
20            end
21        else if (reset_n == 1'b1 & Shift_Enable == 1'b1)
22            begin
23                for (i = 0; i <= (DEPTH-2); i = i + 1)
24                    begin
25                        if( i >= Read_Addr_in)
26                            Reg_File [i] <= Reg_File [i+1];
27                    end
28                Reg_File[DEPTH-1] = {WIDTH{1'b1}};
29            end
30 endmodule
31
```

Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs

Simulation

